

Schedule...

Date	Day	Class No.	Title	Chapters	HW Due date	Lab Due date	Exam
6 Oct	Mon	10	Energy Storage	3.7, 4.1		NO LAB	
7 Oct	Tue					NO LAB	
8 Oct	Wed	11	Dynamic Circuits	4.2 – 4.4			
9 Oct	Thu						
10 Oct	Fri		Recitation		HW 4		
11 Oct	Sat						
12 Oct	Sun						
13 Oct	Mon	12	Exam 1 Review				
14 Oct	Tue					LAB 4	EXAM 1

Energy

Moro. 7: 48


48 Wherefore, my beloved brethren, pray unto the Father with all the **energy** of heart, that ye may be filled with this love, which he hath bestowed upon all who are true followers of his Son, Jesus Christ; that ye may become the sons of God; that when he shall appear we shall be like him, for we shall see him as he is; that we may have this hope; that we may be purified even as he is pure. Amen.

Lecture 10 – Energy Storage

Maximum Power Transfer
Capacitors
Inductors

Maximum Power Transfer

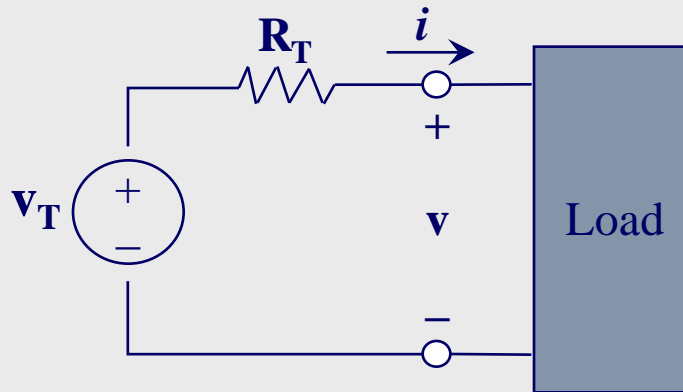- ◆ Equivalent circuit representations are important in power transfer analysis




- ◆ **Ideally** all power from source is absorbed by the load
 - ▲ But some power will be absorbed by internal circuits (represented by R_T)

Maximum Power Transfer

- ◆ Efficiently transferring power from source to load means that internal resistances ($\mathbf{R_T}$) must be minimized

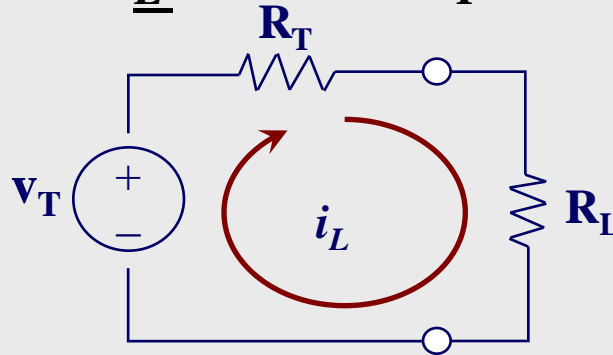
▲ i.e. for a given $\mathbf{R_L}$ we want $\mathbf{R_T}$ as small as possible!



- ◆ For a given $\mathbf{R_T}$ there is a specific $\mathbf{R_L}$ that will maximize power transfer to the load


Maximum Power Transfer

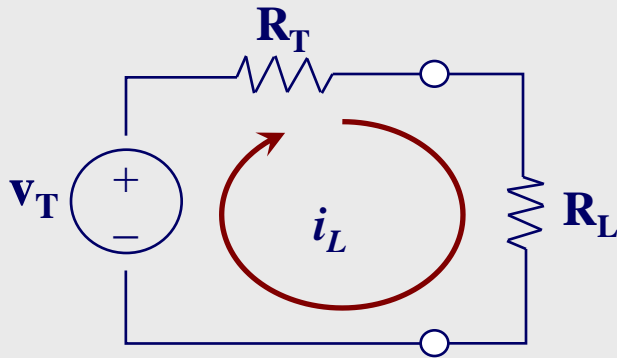◆ Consider the power (P_L) absorbed by the load



Maximum Power Transfer

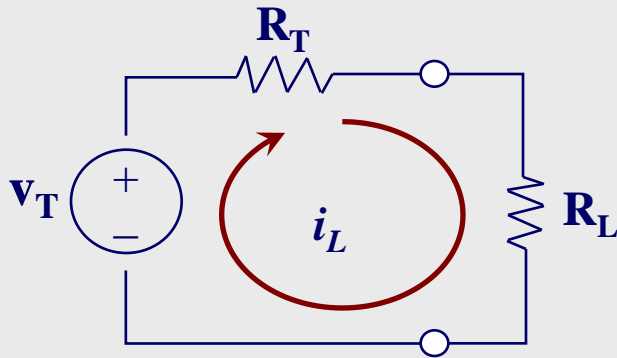- ◆ Consider the power (P_L) absorbed by the load



$$P_L = i_L^2 R_L$$

BUT


$$i_L = \frac{v_T}{R_L + R_T}$$

Therefore

$$P_L = \frac{v_T^2}{(R_L + R_T)^2} R_L$$

Maximum Power Transfer

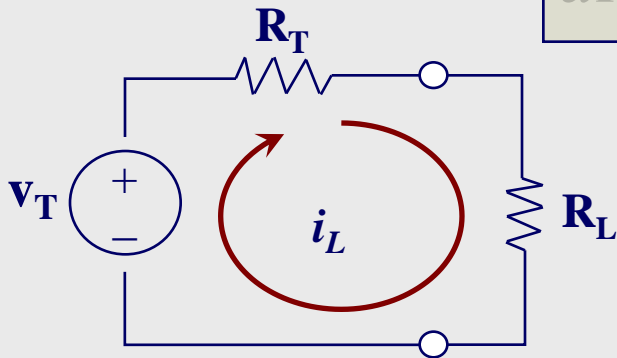- ◆ The **maximum** power transfer can be found by calculating $dP_L/dR_L = 0$



NB: assumes R_T is fixed and R_L is variable

$$\frac{dP_L}{dR_L} = \frac{v_T^2 (R_L + R_T)^{-2} - 2v_T^2 R_L (R_L + R_T)^{-3}}{(R_L + R_T)^4} = 0$$


OR

$$(R_L + R_T)^{-2} - 2R_L (R_L + R_T)^{-3} = 0$$

OR

$$R_L = R_T$$

Maximum Power Transfer

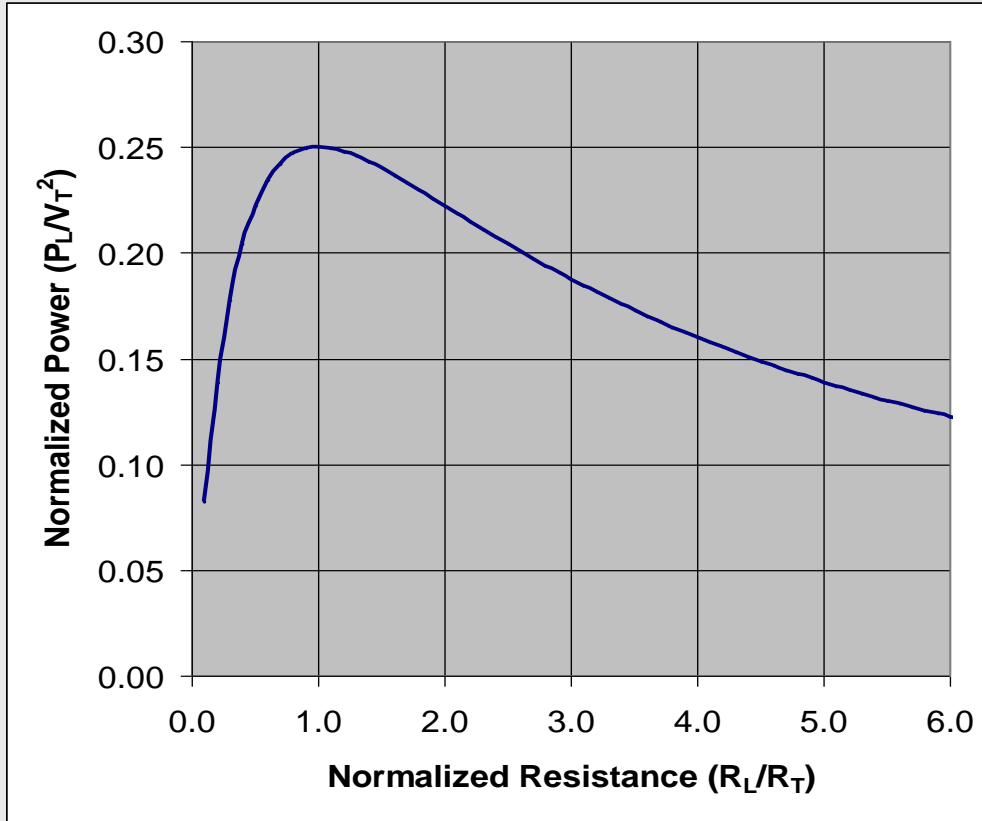


When $R_L < R_T$:
 P_L is lowered since v_L goes down

When $R_L > R_T$:
 P_L is lowered since less current (i_L) flows

To transfer maximum power to the load, the source and load resistors must be **matched** (i.e. $R_T = R_L$). Power is attenuated as R_L departs from R_T

Maximum Power Transfer

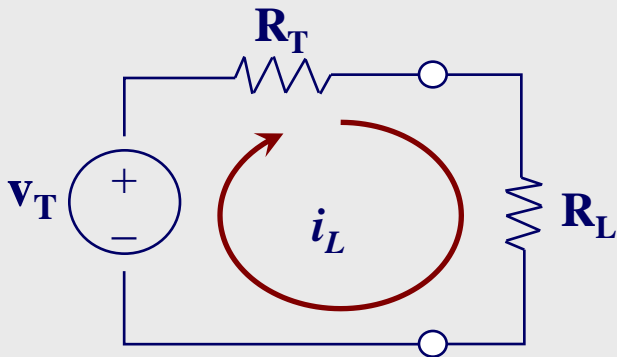Maximum power theorem: maximum power is delivered by a source (represented by its Thévenin equivalent circuit) is attained when the load ($\mathbf{R_L}$) is equal to the Thévenin resistance $\mathbf{R_T}$



$$P_L = \frac{v_T^2}{R_L + R_T} R_L$$

$$P_{LMax} = \frac{v_T^2}{4R_L} = \frac{R_L i_T^2}{4}$$

NB: Substitute ($\mathbf{R_T = R_L}$) to get $\mathbf{P_{LMax}}$

Maximum Power Transfer


Efficiency of power transfer (η): the ratio of the power delivered to the load (P_{out}), to the power supplied by the source (P_{in})

$$\eta = \frac{P_{out}}{P_{in}}$$

NB: $P_{out} = P_L$


Maximum Power Transfer

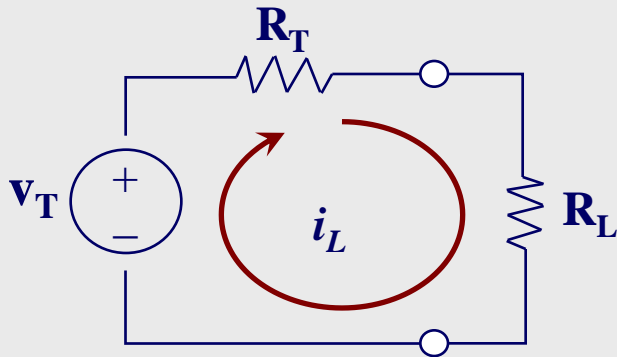Efficiency of power transfer (η): the ratio of the power delivered to the load (P_{out}), to the power supplied by the source (P_{in})



Maximum Power Transfer

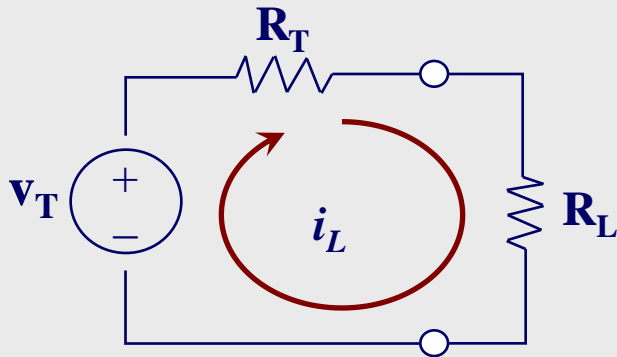Efficiency of power transfer (η): the ratio of the power delivered to the load (P_{out}), to the power supplied by the source (P_{in})




$$P_{in} = i_L v_T$$
$$= v_T \left(\frac{v_T}{R_T + R_L} \right)$$

$$P_{inMax} = \frac{v_T^2}{2R_L}$$
$$= \frac{R_L i_T^2}{2}$$

NB: Substitute ($R_T = R_L$) to get P_{inMax}

Maximum Power Transfer

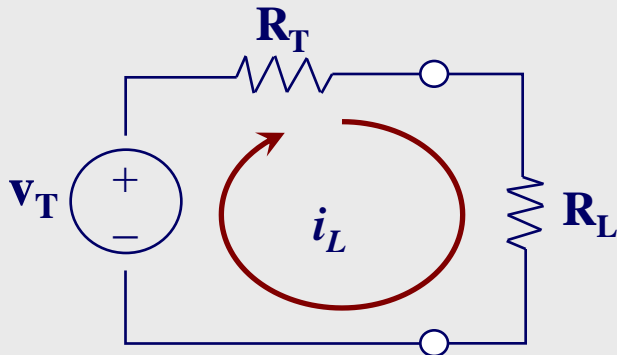Efficiency of power transfer (η): the ratio of the power delivered to the load (P_{out}), to the power supplied by the source (P_{in})




$$\begin{aligned}\eta_{\max} &= \frac{P_{outMax}}{P_{inMax}} \\ &= \frac{v_T^2}{4R_L} \cdot \frac{2R_L}{v_T^2} \\ &= \frac{1}{2}\end{aligned}$$

In other words, **at best**, only 50% efficiency can be achieved

Maximum Power Transfer

◆ **Example 1:** Find the maximum power delivered to R_L

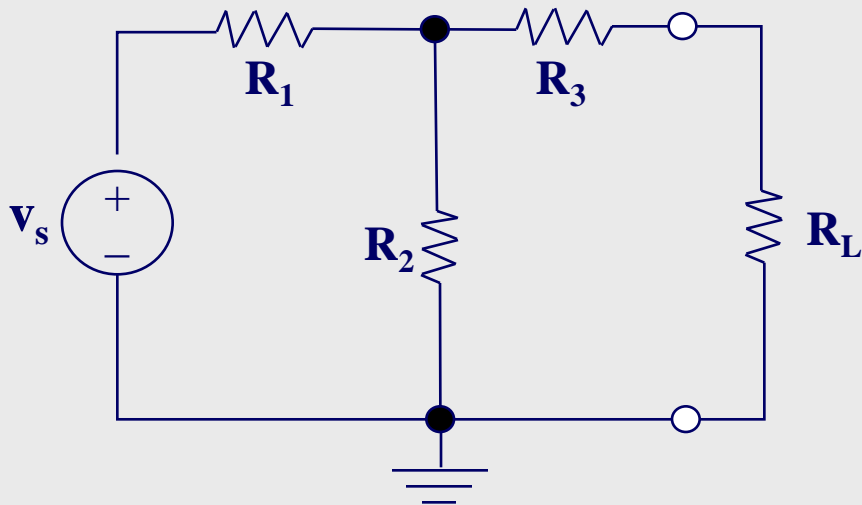▲ $v_s = 18\text{V}$, $R_1 = 3\Omega$, $R_2 = 6\Omega$, $R_3 = 2\Omega$




Maximum Power Transfer

◆ **Example1:** Find the maximum power delivered to $\mathbf{R_L}$

▲ $v_s = 18\text{V}$, $\mathbf{R_1} = 3\Omega$, $\mathbf{R_2} = 6\Omega$, $\mathbf{R_3} = 2\Omega$

1. Find Thévenin equivalent circuit

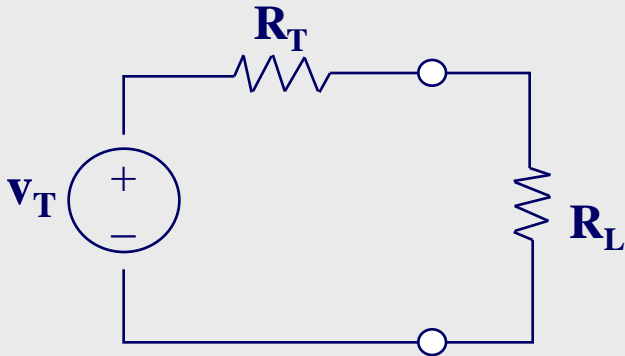


$$v_T = \frac{R_2}{R_1 + R_2} v_s$$
$$= 12\text{V}$$

$$R_T = R_3 + R_1 \parallel R_2$$
$$= 4\Omega$$

Maximum Power Transfer

◆ **Example1:** Find the maximum power delivered to $\mathbf{R_L}$

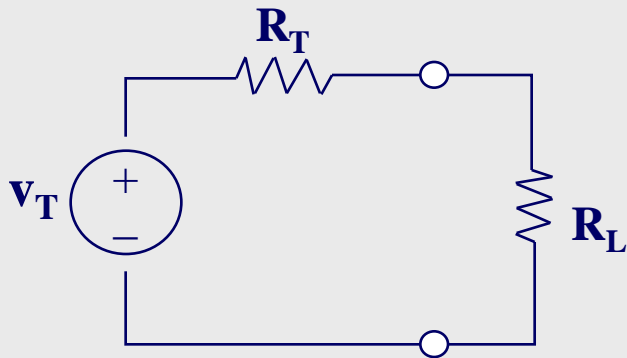▲ $v_s = 18\text{V}$, $\mathbf{R_1} = 3\Omega$, $\mathbf{R_2} = 6\Omega$, $\mathbf{R_3} = 2\Omega$



1. Find Thévenin equivalent circuit
2. Set $\mathbf{R_L} = \mathbf{R_T}$
3. Calculate $\mathbf{P_{LMax}}$


$$\begin{aligned} P_{L\max} &= 0.5 P_{\text{inmax}} \\ &= 0.5 \frac{v_T^2}{2R_L} \\ &= 0.5 \frac{(12)^2}{8} \\ &= 9\text{W} \end{aligned}$$

Dynamic Energy Storage Elements


Capacitor and Inductor

Storage Elements

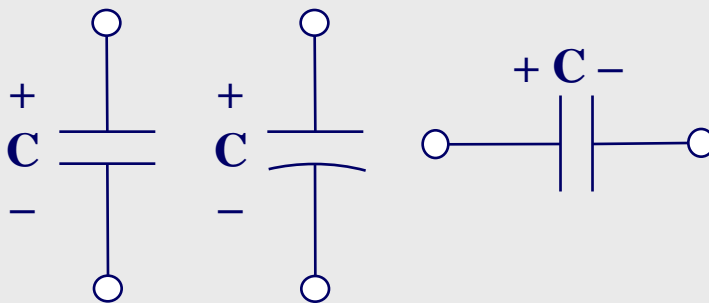- ◆ To this point, circuits have consisted of either:
 - ▶ **DC Sources** (active element, provide energy)
 - ▶ **Resistors** (passive element, absorb energy)
- ◆ Some passive (non-source) elements can store energy
 - ▶ **Capacitors** – store voltage
 - ▶ **Inductors** – store current



Capacitor symbols

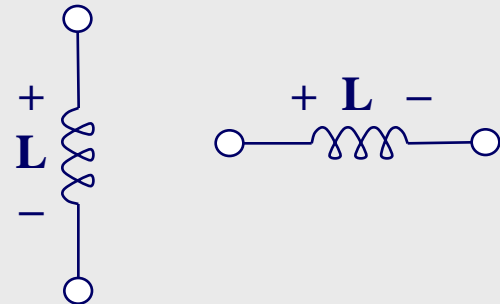


Inductor symbols

Ideal Capacitor

◆ A capacitor (**C**) is composed of:

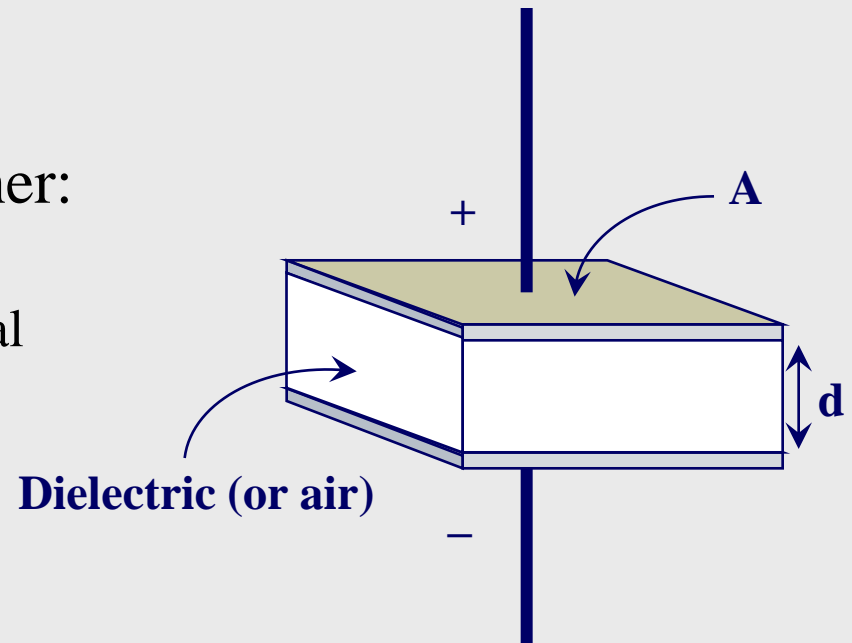- ▶ 2 parallel conducting plates
 - cross-sectional area **A**
- ▶ Separated distance **d** by either:
 - Air
 - Dielectric (insulating) material



$$C = \frac{\epsilon A}{d}$$

C – Capacitance

ϵ – relative permittivity
(dielectric constant)


NB: the parallel plates **do not touch** – thus under DC current a capacitor acts like an **open circuit**

Ideal Capacitor

Capacitance: a measure of the ability to store energy in the form of separated charge (or an electric field)

$$q = Cv$$

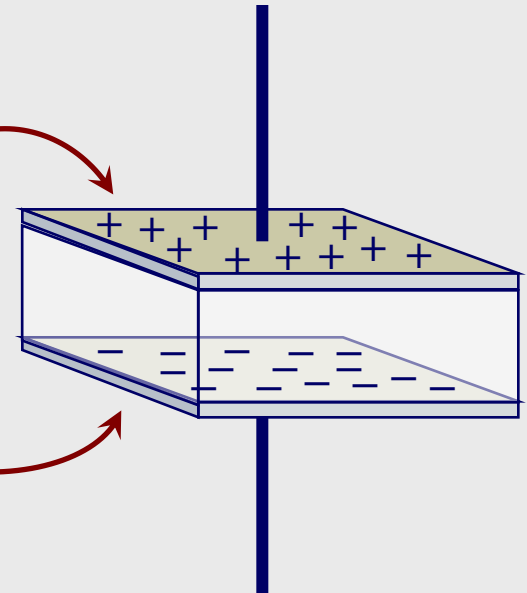The charge q_+ on one plate is equal to the charge q_- on the other plate



Farad (F): unit of capacitance.
1 farad = 1 coulomb/volt (C/V)


Ideal Capacitor

- ◆ **No current** can flow through a capacitor if the voltage across it is **constant** (i.e. connected to a **DC source**)
- ◆ **BUT** when a DC source is applied to a capacitor, there is an **initial** circuit current as the capacitor plates are charged ('**charging**' the capacitor)

$$i(t) = \frac{dq(t)}{dt}$$


Charging the capacitor: a current flows as electrons leave one plate to accumulate on the other.

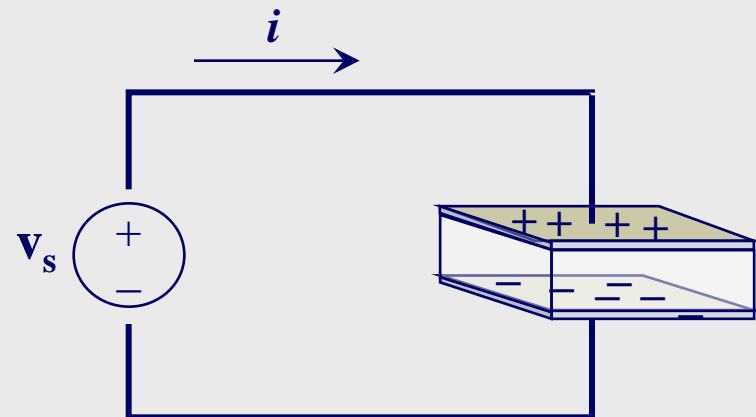This occurs until the voltage across the capacitor = source voltage



Ideal Capacitor

- ◆ **Capacitor with an AC source:** since AC sources periodically reverse voltage directions, the capacitor plates will change charge polarity accordingly
 - ▲ With each polarity change, the capacitor goes through a '**charging**' state, thus current continuously flows
 - ▲ Just as with a DC source, **no electrons cross between the plates**
 - ▲ Just as with a DC source, **voltage across a capacitor cannot change instantaneously**

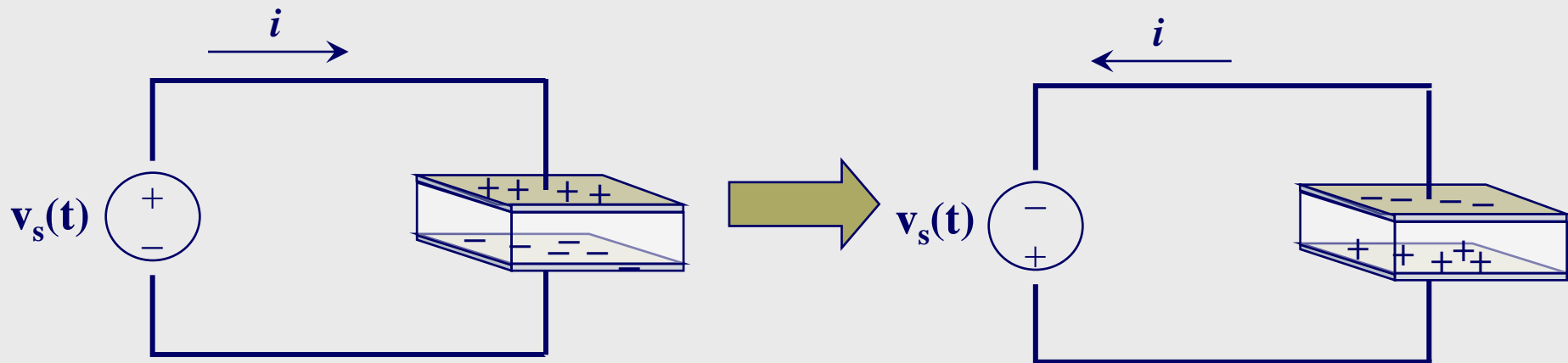

Ideal Capacitor

◆ i – v characteristic for an ideal capacitor

Differentiate both sides

$$q(t) = Cv(t) \quad \Rightarrow \quad \frac{dq(t)}{dt} = \frac{dCv(t)}{dt} \quad \text{BUT} \quad i(t) = \frac{dq(t)}{dt}$$

$$i(t) = C \frac{dv(t)}{dt}$$

OR

$$v(t) = \frac{1}{C} \int_{-\infty}^t i_C(\tau) d\tau$$

Ideal Capacitor

◆ i – v characteristic for an ideal capacitor

$$v(t) = \frac{1}{C} \int_{-\infty}^t i_C(\tau) d\tau$$

NB: Assumes we know the value of the capacitor from time ($\tau = -\infty$) until time ($\tau = t$)

Instead


$$v(t) = \frac{1}{C} \int_{t_0}^t i_C(\tau) d\tau + v(t_0)$$

Initial time (often $t_0 = 0$)

Initial condition


Ideal Capacitor

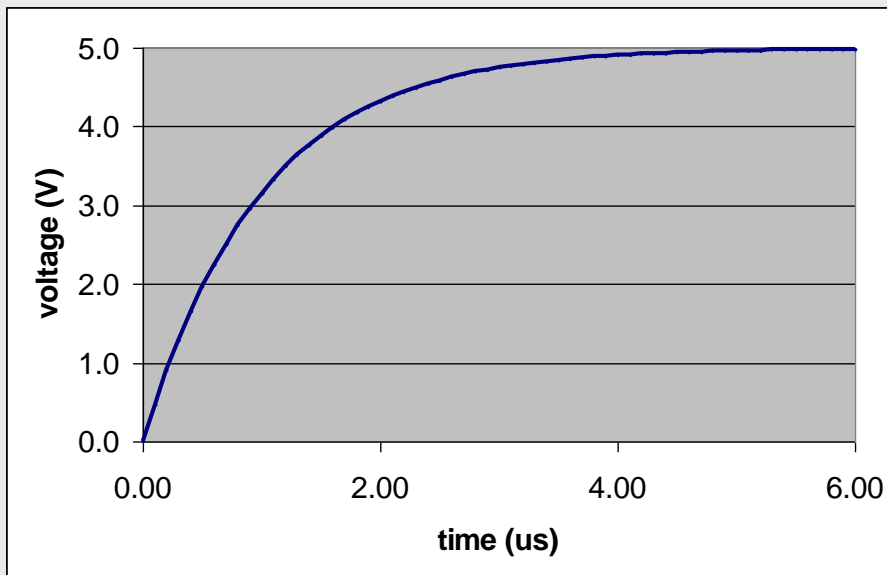- ◆ **Example2:** calculate the current through the capacitor $C = 0.1\mu\text{F}$ with the voltage as shown: $v(t) = 5(1 - e^{-t/10^{-6}})$



Ideal Capacitor


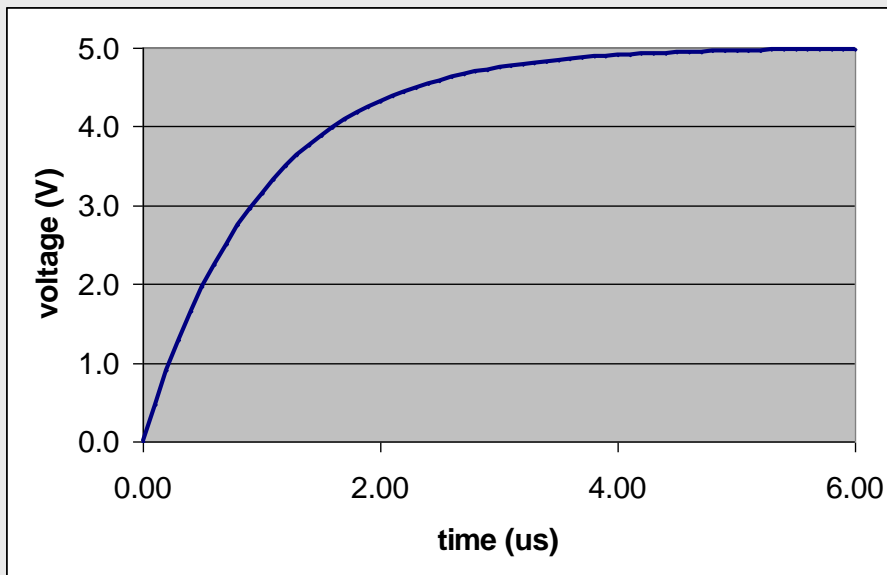
- ◆ **Example2:** calculate the current through the capacitor $C = 0.1\mu\text{F}$ with the voltage as shown: $v(t) = 5(1 - e^{-t/10^{-6}})$



$$\begin{aligned} i(t) &= C \frac{dv(t)}{dt} \\ &= (10^{-7}) \frac{5}{10^{-6}} e^{-t/10^{-6}} \\ &= 0.5e^{-t/10^{-6}} \text{ A} \end{aligned}$$

Ideal Capacitor

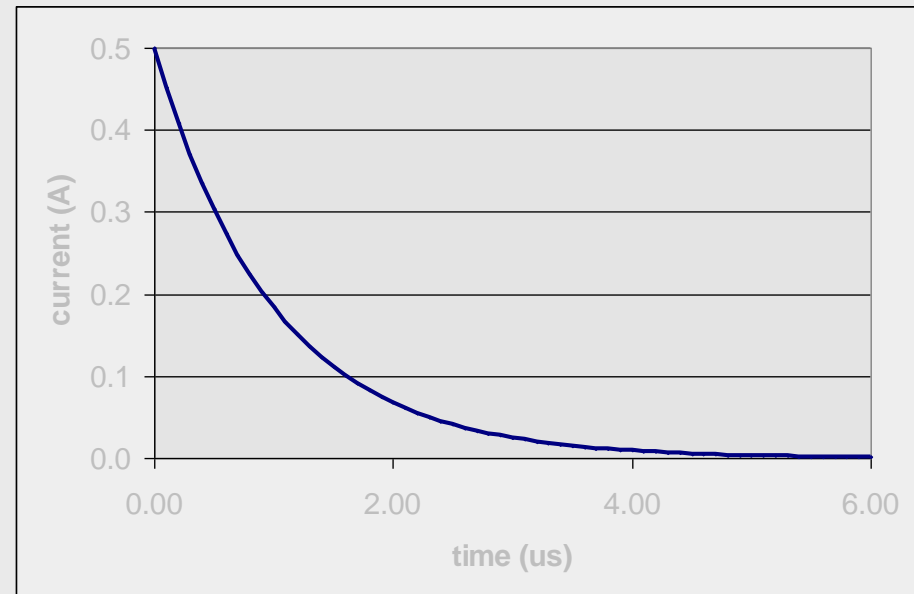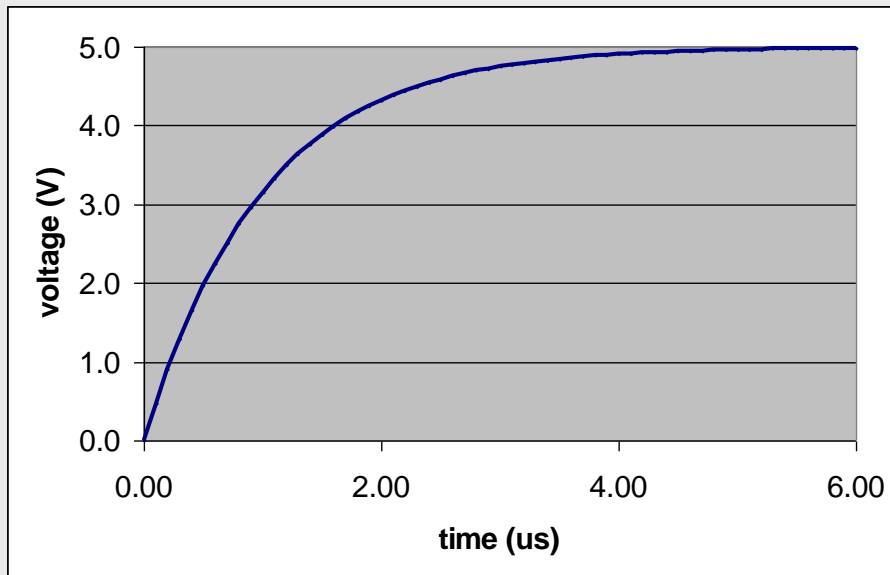- ◆ **Example2:** calculate the current through the capacitor $C = 0.1\mu\text{F}$ with the voltage as shown: $v(t) = 5(1 - e^{-t/10^{-6}})$




NB: the capacitor's current jumps '**instantaneously**' to 0.5A. The ability of a capacitor's current to change instantaneously is an important property of capacitors

$$i(t) = 0.5e^{-t/10^{-6}} \text{ A}$$


Ideal Capacitor

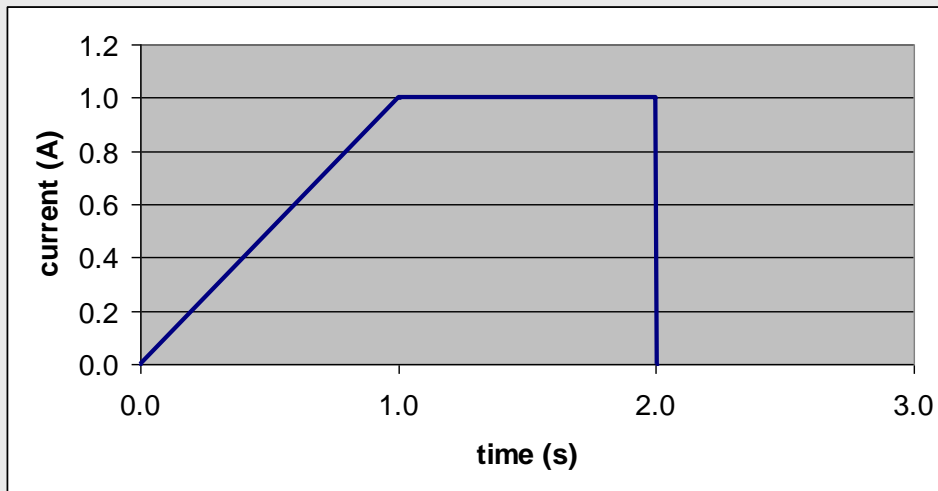◆ **Example3**: find the voltage $v(t)$ for a capacitor $C = 0.5\text{F}$ with the current as shown and $v(0) = 0$



Ideal Capacitor

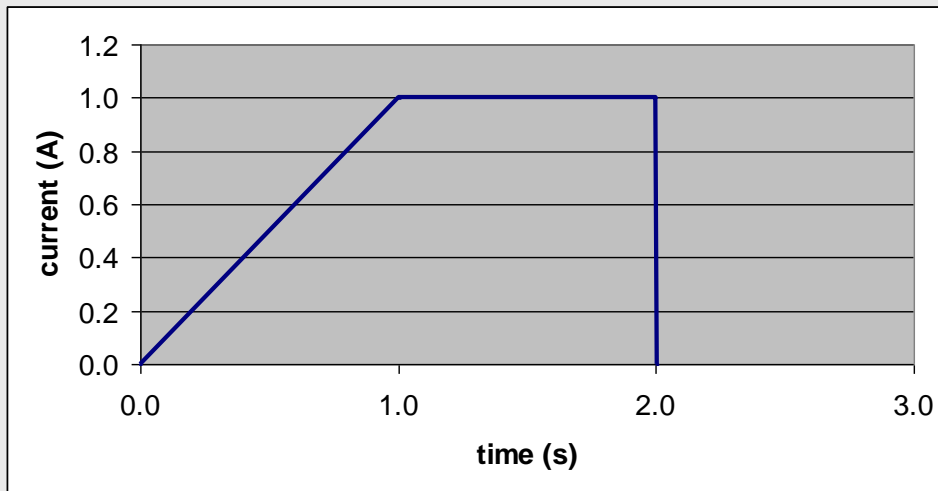◆ **Example3:** find the voltage $v(t)$ for a capacitor $C = 0.5\text{F}$ with the current as shown and $v(0) = 0$




Interval	current $i(t)$
$t \leq 0$	0
$0 < t \leq 1$	t
$1 < t \leq 2$	1
$2 < t$	0

$$v(t) = \frac{1}{C} \int_0^t i d\tau + v(0)$$

Ideal Capacitor

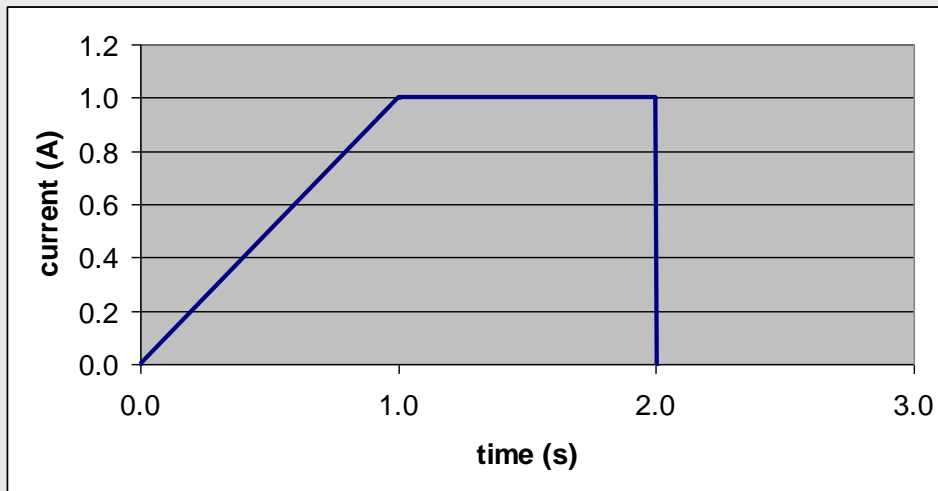◆ **Example3:** find the voltage $v(t)$ for a capacitor $C = 0.5\text{F}$ with the current as shown and $v(0) = 0$




Interval	voltage $v(t)$
$t \leq 0$	0
$0 < t \leq 1$	$2 \int_0^t \tau d\tau + 0$
$1 < t \leq 2$	$2 \int_0^t (1) d\tau + v(1)$
$2 < t$	$0 + v(2)$

$$v(t) = \frac{1}{C} \int_0^t i d\tau + v(0)$$

Ideal Capacitor


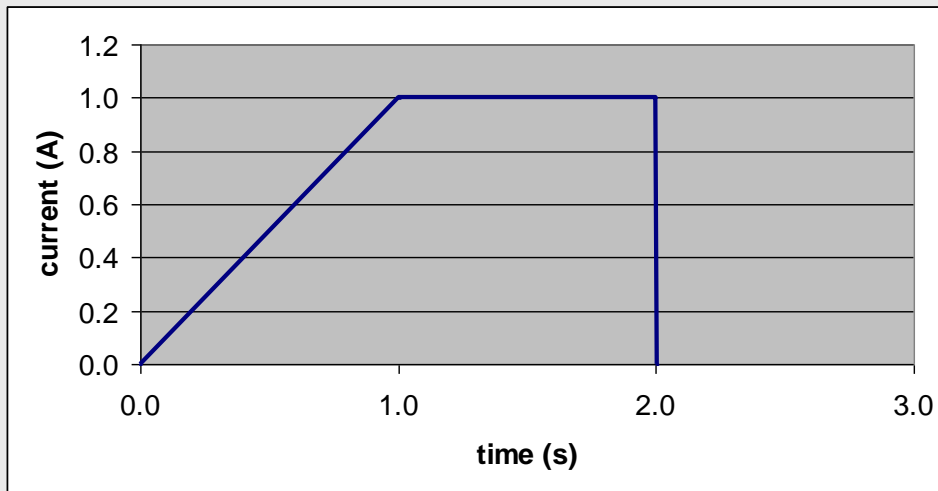
◆ **Example3:** find the voltage $v(t)$ for a capacitor $C = 0.5\text{F}$ with the current as shown and $v(0) = 0$



Interval	voltage $v(t)$
$t \leq 0$	0
$0 < t \leq 1$	t^2
$1 < t \leq 2$	$2t - 1$
$2 < t$	3

Ideal Capacitor

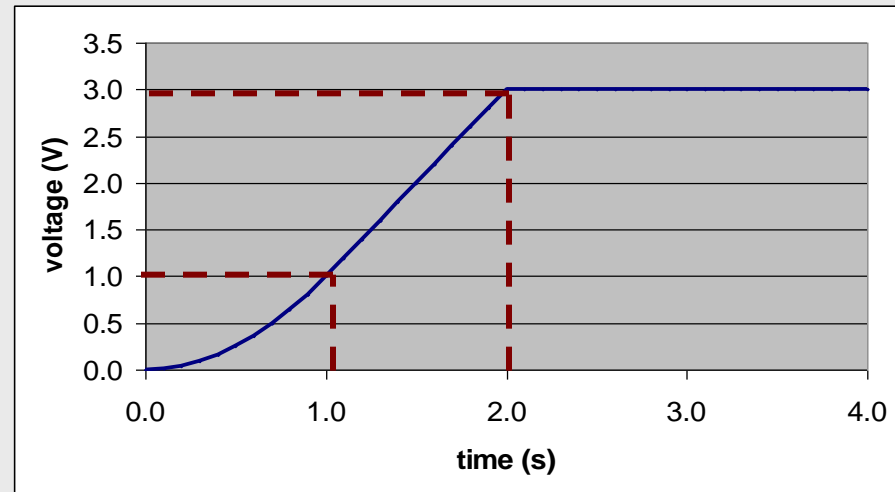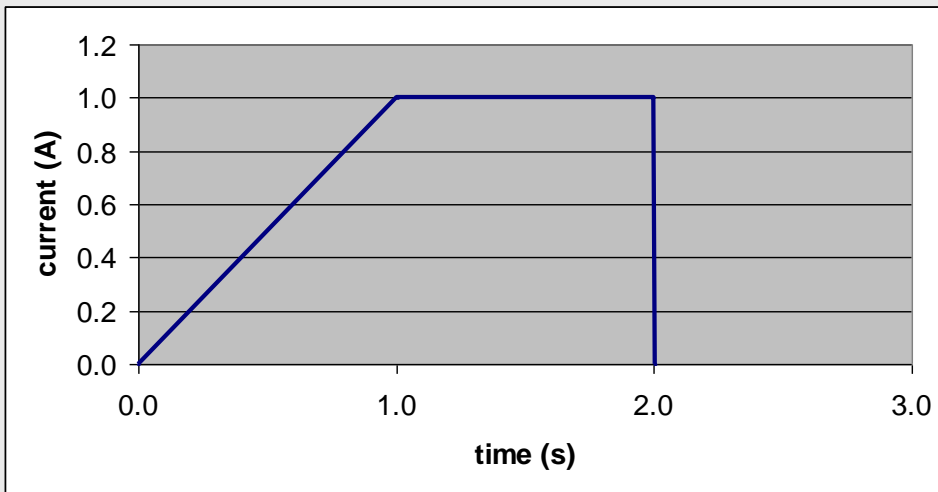◆ **Example3:** find the voltage $v(t)$ for a capacitor $C = 0.5\text{F}$ with the current as shown and $v(0) = 0$



NB: The final value of the capacitor voltage after the current source has stopped charging the capacitor depends on two things:

1. The initial capacitor voltage
2. The history of the capacitor current


Interval	voltage $v(t)$
$t \leq 0$	0
$0 < t \leq 1$	t^2
$1 < t \leq 2$	$2t - 1$
$2 < t$	3

Series Capacitors

◆ **Capacitor Series Rule:** two or more circuit elements are said to be **in series** if the current from one element *exclusively* flows into the next element.

▲ Capacitors in **series** add the same way resistors in **parallel** add
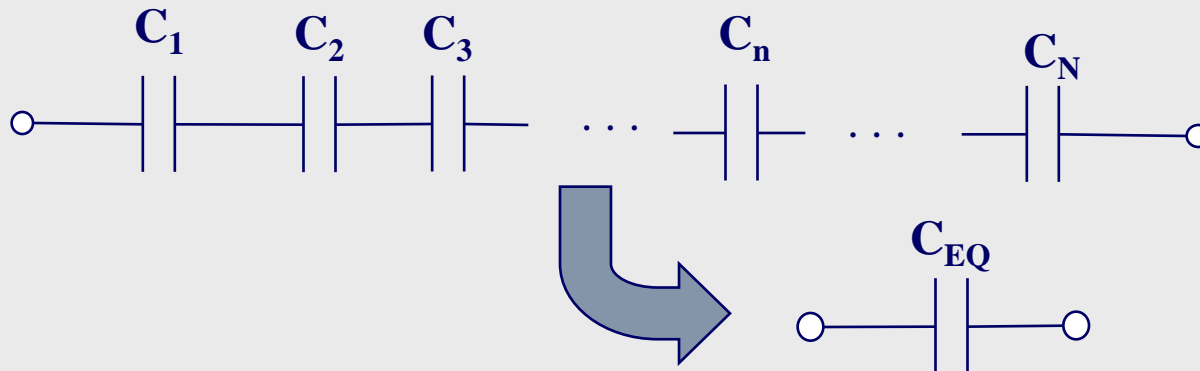
$$\frac{1}{C_{EQ}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N} \quad C_{EQ} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}}$$




Parallel Capacitors

◆ **Parallel Rule**: two or more circuit elements are said to be **in parallel** if the elements share the *same* terminals

▲ Capacitors in **parallel** add the same way resistors in **series** add


$$C_{EQ} = \sum_{n=1}^N C_n$$

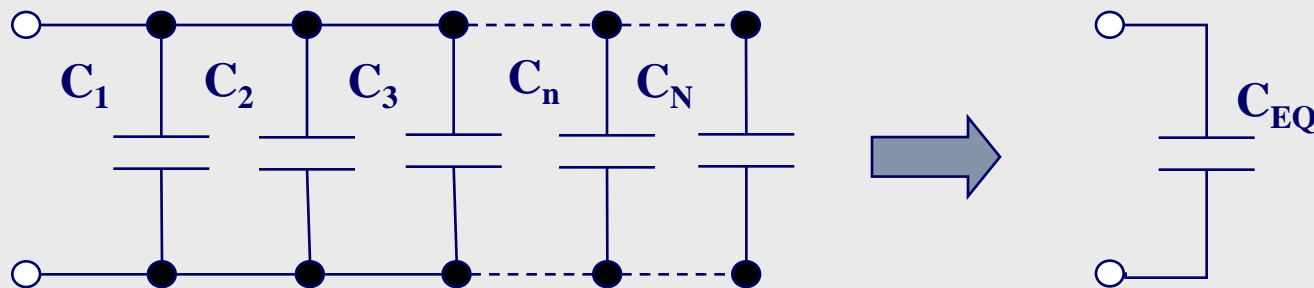

Parallel and Series Capacitors

◆ **Example4:** determine the equivalent capacitance C_{EQ}

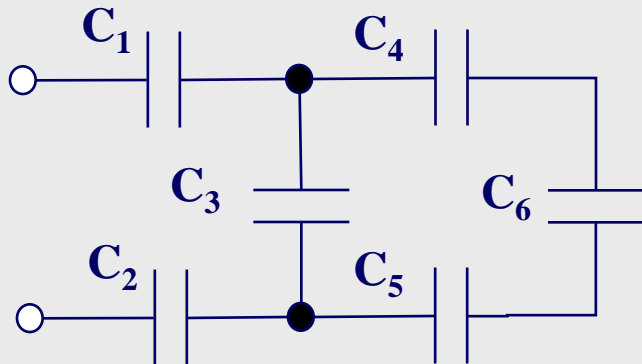
▲ $C_1 = 2\text{mF}$, $C_2 = 2\text{mF}$, $C_3 = 1\text{mF}$, $C_4 = 1/3\text{mF}$, $C_5 = 1/3\text{mF}$,
 $C_6 = 1/3\text{mF}$



Parallel and Series Capacitors

◆ **Example4:** determine the equivalent capacitance C_{EQ}

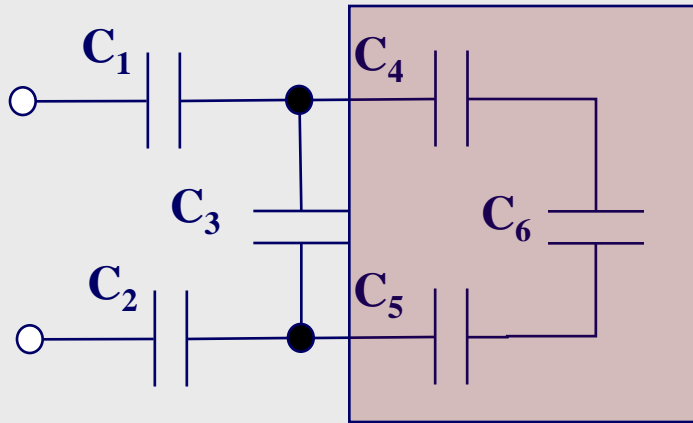▲ $C_1 = 2\text{mF}$, $C_2 = 2\text{mF}$, $C_3 = 1\text{mF}$, $C_4 = 1/3\text{mF}$, $C_5 = 1/3\text{mF}$,
 $C_6 = 1/3\text{mF}$




$$\begin{aligned} C_{EQ1} &= \frac{C_4 C_5 C_6}{C_4 C_5 + C_4 C_6 + C_5 C_6} \\ &= \frac{(1/3)(1/3)(1/3)}{(1/3)(1/3) + (1/3)(1/3) + (1/3)(1/3)} \\ &= \frac{1/27}{1/3} \\ &= \frac{1}{9} \text{ mF} \end{aligned}$$

Parallel and Series Capacitors

◆ **Example4:** determine the equivalent capacitance C_{EQ}

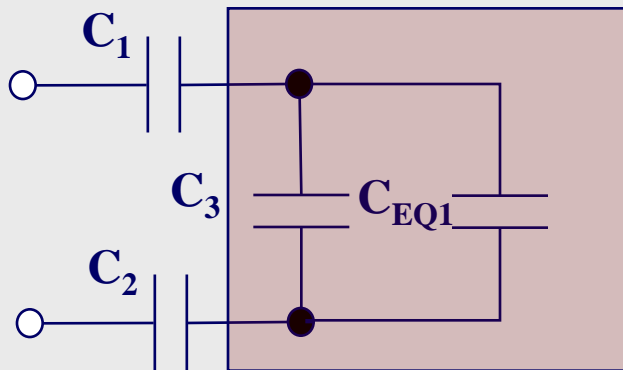▲ $C_1 = 2\text{mF}$, $C_2 = 2\text{mF}$, $C_3 = 1\text{mF}$, $C_4 = 1/3\text{mF}$, $C_5 = 1/3\text{mF}$,
 $C_6 = 1/3\text{mF}$




$$C_{EQ1} = \frac{1}{9} \text{ mF}$$

$$\begin{aligned} C_{EQ2} &= C_3 + C_{EQ1} \\ &= (1) + \left(\frac{1}{9} \right) \\ &= \frac{10}{9} \text{ mF} \end{aligned}$$

Parallel and Series Capacitors

◆ **Example4:** determine the equivalent capacitance C_{EQ}

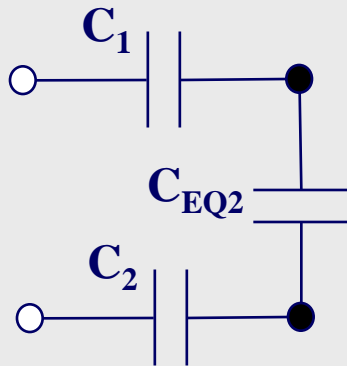▲ $C_1 = 2\text{mF}$, $C_2 = 2\text{mF}$, $C_3 = 1\text{mF}$, $C_4 = 1/3\text{mF}$, $C_5 = 1/3\text{mF}$,
 $C_6 = 1/3\text{mF}$




$$C_{EQ2} = \frac{10}{9} \text{ mF}$$

$$\begin{aligned} C_{EQ} &= \frac{C_1 C_2 C_{EQ2}}{C_1 C_2 + C_1 C_{EQ2} + C_2 C_{EQ2}} \\ &= \frac{(2)(2)(10/9)}{(2)(2) + (2)(10/9) + (2)(10/9)} \\ &= \frac{40/9}{4 + 20/9 + 20/9} \\ &= \frac{10}{19} \text{ mF} \end{aligned}$$

Parallel and Series Capacitors

◆ **Example4:** determine the equivalent capacitance C_{EQ}

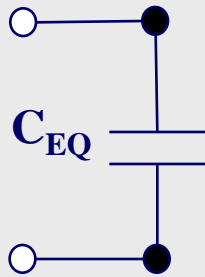▲ $C_1 = 2\text{mF}$, $C_2 = 2\text{mF}$, $C_3 = 1\text{mF}$, $C_4 = 1/3\text{mF}$, $C_5 = 1/3\text{mF}$,
 $C_6 = 1/3\text{mF}$



$$C_{EQ} = \frac{10}{19} \text{ mF}$$

Energy Storage in Capacitors

Capacitor energy $W_C(t)$: can be found by taking the integral of power

▲ Instantaneous power $\rightarrow P_C = i v$

$$\begin{aligned} W_C(t) &= \int_{-\infty}^t P_C(\tau) d\tau \\ &= \int_{-\infty}^t v_C(\tau) i_C(\tau) d\tau \\ &= \int_{-\infty}^t v_C(\tau) C \frac{dv_C(\tau)}{d\tau} d\tau \\ &= C \int_{v(-\infty)}^{v(t)} v dv \\ &= \frac{1}{2} C v^2 \Big|_{v(-\infty)}^{v(t)} \end{aligned}$$

Since the capacitor is uncharged at $t = -\infty$, $v(-\infty) = 0$, thus:

$$W_C(t) = \frac{1}{2} C v(t)^2 \text{ J}$$

Ideal Inductor


◆ Inductors are made by winding a coil of wire around a core

▲ The core can be an insulator or ferromagnetic material

$$L = \frac{\mu N^2 A}{l + 0.45d}$$

L – Inductance

μ – relative permeability

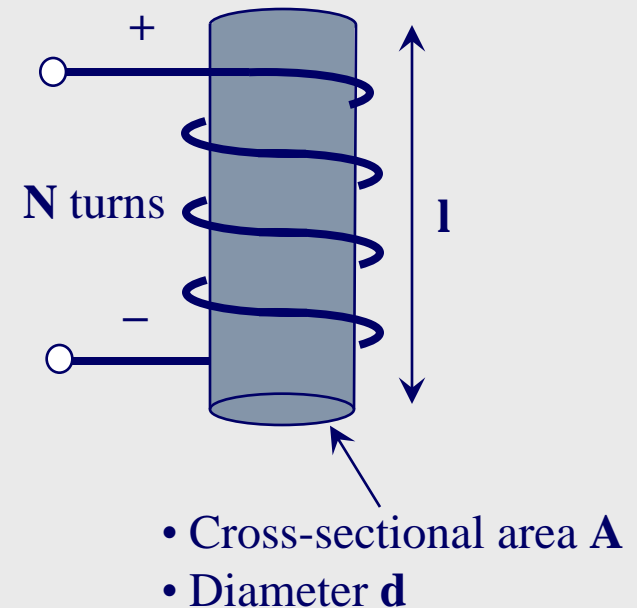


Ideal Inductor

Inductance: a measure of the ability of a device to store energy in the form of a magnetic field

Ideally the resistance through an inductor is **zero** (i.e. **no voltage drop**), thus an inductor acts like a **short circuit** in the presence of a **DC source**.

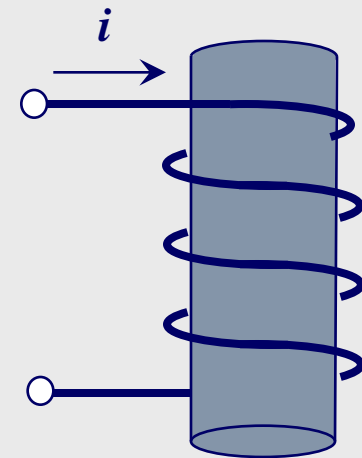BUT there is an **initial** voltage across the inductor as the current builds up (much like 'charging' with capacitors)




Henry (H): unit of inductance.

1 henry = 1 volt-second/ampere (V-s/A)

Ideal Inductor

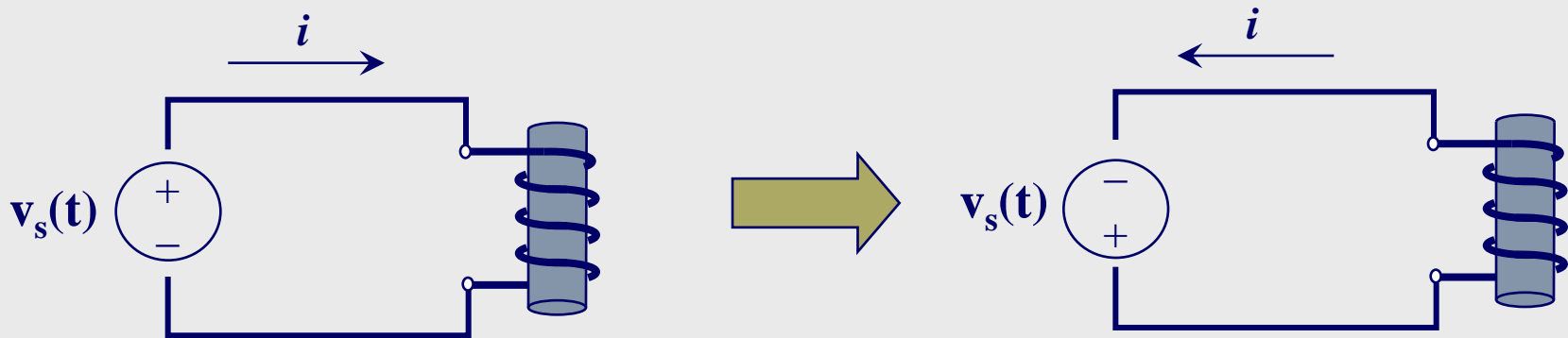- ◆ **Inductor with an AC source**: since AC sources periodically reverse current directions, the current flow through the inductor also changes
 - ▲ With each current direction change, the current through the inductor must 'build up', thus there is a continual voltage drop across the inductor
 - ▲ Just as with a DC source, **current across an inductor cannot change instantaneously**



Ideal Inductor

◆ I – v characteristic for an ideal inductor

$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v_L(\tau) d\tau$$

NB: note the **duality** between inductors and capacitors

Ideal Inductor

◆ i – v characteristic for an ideal inductor

$$i(t) = \frac{1}{L} \int_{-\infty}^t v_L(\tau) d\tau$$

NB: Assumes we know the value of the inductor from time ($\tau = -\infty$) until time ($\tau = t$)

Instead


$$i(t) = \frac{1}{L} \int_{t_0}^t v_L(\tau) d\tau + i(t_0)$$

Initial time (often $t_0 = 0$)

Initial condition


Ideal Inductor

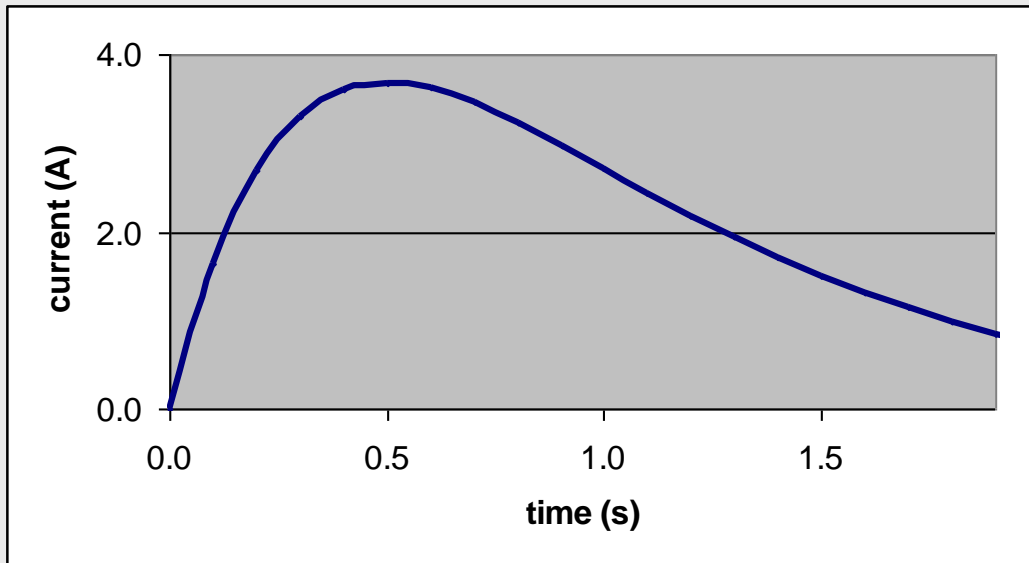◆ **Example 5:** find the voltage across an inductor $L = 0.1\text{H}$ when the current is: $i(t) = 20 t e^{-2t}$



Ideal Inductor


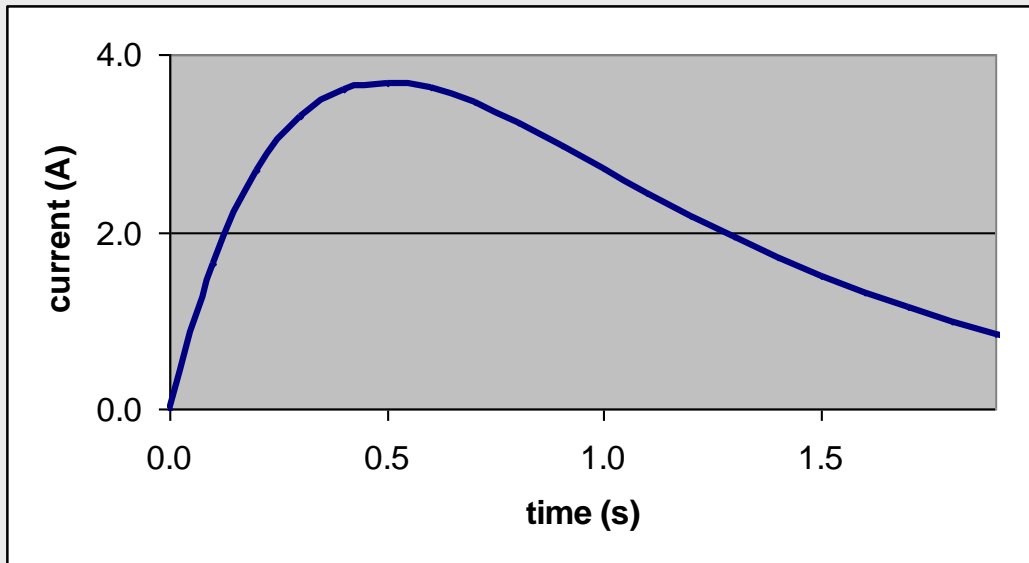
◆ **Example 5:** find the voltage across an inductor $L = 0.1\text{H}$ when the current is: $\mathbf{i(t) = 20 t e^{-2t}}$



$$\begin{aligned} v(t) &= L \frac{di(t)}{dt} \\ &= 0.1 \frac{d}{dt} (20te^{-2t}) \\ &= 2(-2te^{-2t} + e^{-2t}) \\ &= 2e^{-2t} (1 - 2t) \text{ V} \end{aligned}$$

Ideal Inductor

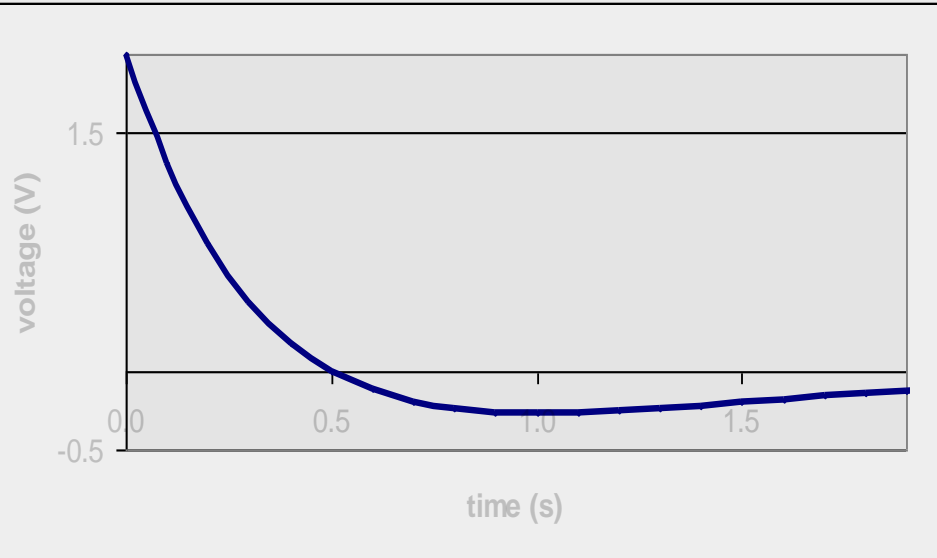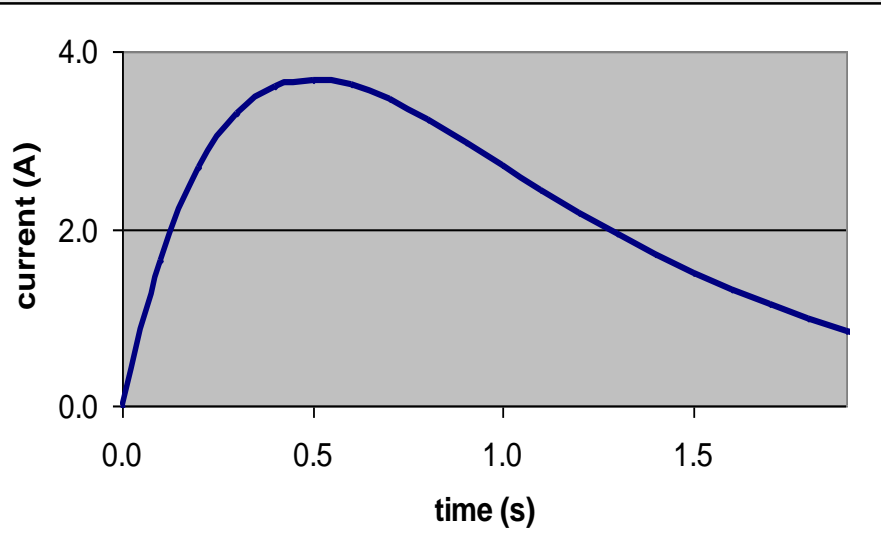◆ **Example 5:** find the voltage across an inductor $L = 0.1\text{H}$ when the current is: $\mathbf{i(t) = 20\ t\ e^{-2t}}$



NB: the inductor's voltage jumps '**instantaneously**' to 2V. The ability of an inductor's voltage to change instantaneously is an important property of inductors


$$v(t) = 2e^{-2t}(1 - 2t)V$$

Series Inductors

◆ **Series Rule**: two or more circuit elements are said to be **in series** if the current from one element *exclusively* flows into the next element.

▲ Inductors in **series** add the same way resistors in **series** add

$$L_{EQ} = \sum_{n=1}^N L_n$$

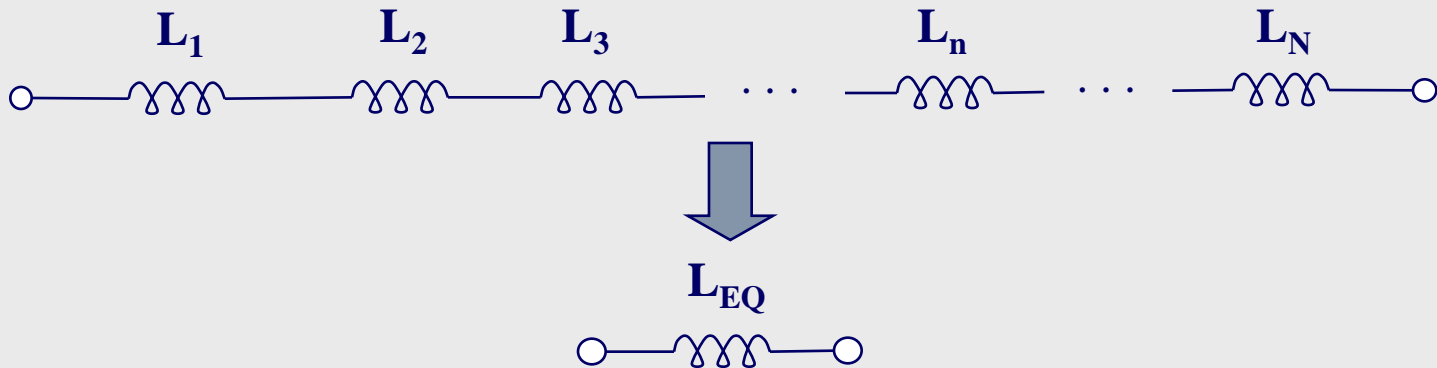


Parallel Inductors

◆ **Parallel Rule**: two or more circuit elements are said to be **in parallel** if the elements share the *same* terminals

▲ Inductors in **parallel** add the same way resistors in **parallel** add
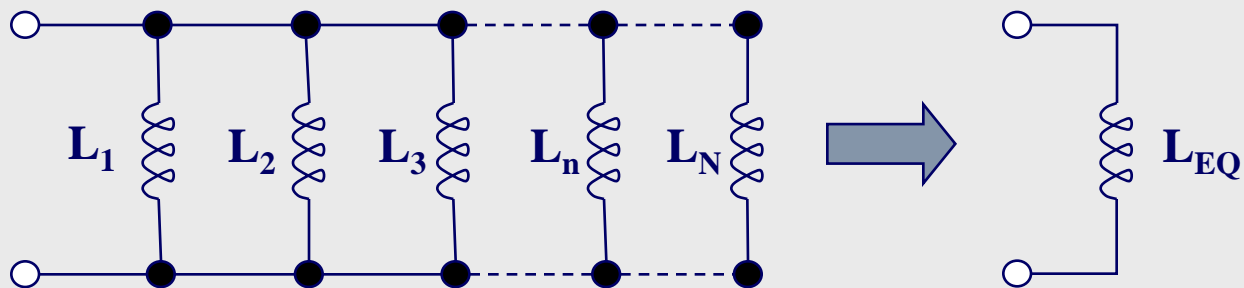
$$\frac{1}{L_{EQ}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \cdots + \frac{1}{L_N} \quad L_{EQ} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \cdots + \frac{1}{L_N}}$$



Energy Storage in Capacitors

Capacitor energy $W_L(t)$: can be found by taking the integral of power

▶ Instantaneous power $\rightarrow P_L = i v$

$$\begin{aligned} W_L(t) &= \int_{-\infty}^t P_L(\tau) d\tau \\ &= \int_{-\infty}^t v_L(\tau) i_L(\tau) d\tau \\ &= \int_{-\infty}^t L \frac{di_L(\tau)}{d\tau} i_L(\tau) d\tau \\ &= L \int_{i(-\infty)}^{i(t)} i di \\ &= \frac{1}{2} L i^2 \Big|_{i(-\infty)}^{i(t)} \end{aligned}$$

Since the inductor is uncharged at $t = -\infty$, $i(-\infty) = 0$, thus:

$$W_L(t) = \frac{1}{2} L i(t)^2 \text{ J}$$

Energy Storage in Capacitors

◆ **Example6:** calculate the power and energy stored in a 0.1-H inductor when:

▲ $i = 20 t e^{-2t} \text{ A}$ ($i = 0$ for $t < 0$)

▲ $V = 2 e^{-2t} (1 - 2t) \text{ V}$ (for $t \geq 0$)

Energy Storage in Capacitors

◆ **Example6:** calculate the power and energy stored in a 0.1-H inductor when:

▲ $i = 20 t e^{-2t} \text{ A}$ ($i = 0$ for $t < 0$)

▲ $V = 2 e^{-2t} (1 - 2t) \text{ V}$ (for $t \geq 0$)

$$\begin{aligned} P_L(t) &= v_L(t) i_L(t) \\ &= 2e^{-2t} (1 - 2t) \cdot 20te^{-2t} \\ &= 40te^{-4t} (1 - 2t) \text{ W} \end{aligned}$$

Energy Storage in Capacitors

◆ **Example6:** calculate the **power** and **energy** stored in a 0.1-H inductor when:



▲ $i = 20 t e^{-2t} \text{ A}$ ($i = 0$ for $t < 0$)

▲ $V = 2 e^{-2t} (1 - 2t) \text{ V}$ (for $t \geq 0$)

$$\begin{aligned} P_L(t) &= v_L(t) i_L(t) \\ &= 2e^{-2t} (1 - 2t) 20te^{-2t} \\ &= 40te^{-4t} (1 - 2t) \text{ W} \end{aligned}$$

$$\begin{aligned} W_L(t) &= \frac{1}{2} L i_L(t)^2 \\ &= \frac{1}{2} (0.1) (20te^{-2t})^2 \\ &= 20t^2 e^{-4t} \text{ J} \end{aligned}$$

Ideal Capacitors and Inductors

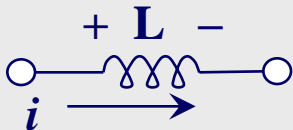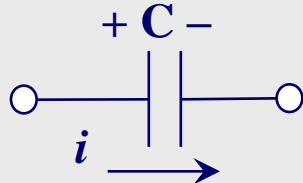	Inductors	Capacitors
Passive sign convention		
Voltage	$v(t) = L \frac{di(t)}{dt}$	$v(t) = \frac{1}{C} \int_0^t i_C(\tau) d\tau + v(t_0)$
Current	$i(t) = \frac{1}{L} \int_0^t v_L(\tau) d\tau + i(t_0)$	$i(t) = C \frac{dv(t)}{dt}$
Power	$P_L(t) = Li(t) \frac{di(t)}{dt}$	$P_C(t) = Cv(t) \frac{dv(t)}{dt}$

Ideal Capacitors and Inductors

	Inductors	Capacitors
Energy	$W_L(t) = \frac{1}{2} Li(t)^2$	$W_C(t) = \frac{1}{2} Cv(t)^2$
An instantaneous change is not permitted in:	Current	Voltage
Will permit an instantaneous change in:	Voltage	Current
With DC source element acts as a:	Short Circuit	Open Circuit