Schedule...

| Date | Day | Class No. | Title | Chapters | HW Due date | Lab Due date | Exam |
|--------|-----|--------------|---------------------|----------|----------------|-----------------|----------|
| 13 Oct | Mon | 12 | Exam 1 Review | | | LAB 4 | |
| 14 Oct | Tue | | | | | | |
| 15 Oct | Wed | 13 | Phasors | 4.4 | | | EXAM 1 |
| 16 Oct | Thu | | | | | | |
| 17 Oct | Fri | | Recitation | | | | , |
| 18 Oct | Sat | | | | | | |
| 19 Oct | Sun | | | | | | |
| 20 Oct | Mon | 14 | AC Circuit Analysis | 4.5 | | NO LAB | |
| 21 Oct | Tue | | | (| | NOLAB | 1 |



Examine Yourselves

<u>2 Cor. 13: 5</u>

5 **Examine** yourselves, whether ye be in the faith; prove your own selves.



Lecture 12 – Exam 1 Review

Chapters 2 - 3





Discussion #12 – Exam 1 Review

Exam 1

- 20 23 February (Tuesday Friday)
- Chapters 2 and 3
- 18 questions
 - ▲ 15 multiple choice (answer on bubble sheet!)
 - 1 point each
 - ▲ 3 long answer (show your work!)
 - Up to 5 points each
- Closed book!
 - ▲ One 3x5 card allowed
- Calculators allowed
- No time limit
- Study lecture slides and homework



Exam 1 Review...Overview

- 1. Kirchoff's current law
- 2. Kirchoff's voltage law
- 3. Passive sign convention
- 4. Voltage/current dividers (Ohm's Law)
- 5. Wheatstone bridge
- 6. Measuring Devices
- 7. Node voltage method
- 8. Mesh current method
- 9. Principle of superposition
- 10. Source transformation
- 11. Thévenin equivalent circuits
- 12. Norton equivalent circuits
- 13. Maximum power transfer
- 14. Dependent Sources



1. What is Kirchoff's current law?



What is Kirchoff's current law?
 a) What is an expression for the current at Node a?





What is Kirchoff's current law?
 a) What is an expression for the current at Node a?



$$i_{s1} + i_{s2} - i_2 = 0$$



- 1. What is Kirchoff's current law?
 - a) What is an expression for the current at **Node a**?
 - b) what expressions for the current through R_2 are valid?





- 1. What is Kirchoff's current law?
 - a) What is an expression for the current at Node a?
 - b) what expressions for the current through R_2 are valid?





ECEN 301

Discussion #12 –Exam 1 Review

- 1. What is Kirchoff's current law?
 - a) What is an expression for the current at Node a?
 - b) what expressions for the current through R_2 are valid?





2. What is Kirchoff's voltage law?



2. What is Kirchoff's voltage law?
a) If V_s = 3V, what are the voltages across R₁, R₂, and R₃?





2. What is Kirchoff's voltage law?
a) If V_s = 3V, what are the voltages across R₁, R₂, and R₃?





3. What is the passive sign convention?



- 3. What is the passive sign convention?
 - a) Which element dissipates power and which generates power?





- 3. What is the passive sign convention?
 - a) Which element dissipates power and which generates power?





17

ECEN 301

Discussion #12 –Exam 1 Review

- 3. What is the passive sign convention?
 - b) Find the power dissipated by each element





- 3. What is the passive sign convention?
 - b) Find the power dissipated by each element



NB: since **load D** and **load E** share the same nodes their voltages will be the same

KCL at node a :

$$i_a - i_d - i_e = 0$$

 $i_a = i_d + i_e$
 $= 3 + 2$
 $= 5A$

KVL at Loop1 :

$$-v_a - v_b + v_e + v_c = 0$$

$$v_a = v_e + v_c - v_b$$

$$= 10 + 5 - 3$$

$$= 12V$$



19

ECEN 301

Discussion #12 –Exam 1 Review

- 3. What is the passive sign convention?
 - b) Find the power dissipated by each element





20

 $P_c = 5V \times 5A$

Discussion #12 –Exam 1 Review

4. What is a voltage/current divider?



4. What is a voltage/current divider?





22

ECEN 301

Discussion #12 –Exam 1 Review

- 4. What is a voltage/current divider?
 - a) Using a voltage divider find the voltage across \mathbf{R}_3 $\mathbf{V}_s = 3\mathbf{V}, \mathbf{R}\mathbf{1} = 10\Omega, \mathbf{R}_2 = 6\Omega, \mathbf{R}_3 = 8\Omega$





- 4. What is a voltage/current divider?
 - a) Using a voltage divider find the voltage across \mathbf{R}_3 $\mathbf{V}_s = 3\mathbf{V}, \mathbf{R}\mathbf{1} = 10\Omega, \mathbf{R}_2 = 6\Omega, \mathbf{R}_3 = 8\Omega$





4. What is a voltage/current divider?

a) Using a current divider find i_1 $\mathbf{R}_1 = 10\Omega$, $\mathbf{R}_2 = 2 \Omega$, $\mathbf{R}_3 = 20 \Omega$, $I_s = 4A$





4. What is a voltage/current divider?
a) Using a current divider find *i*₁

 $\mathbf{R_1} = 10\Omega, \, \mathbf{R_2} = 2 \,\Omega, \, \mathbf{R_3} = 20 \,\Omega, \, \mathbf{I_s} = 4 \mathrm{A}$





26

Discussion #12 –Exam 1 Review

Exam 1 Review...Wheatstone

5. What is the voltage across the terminals a and b of the Wheatstone bridge?





Exam 1 Review...Wheatstone

5. What is the voltage across the terminals a and b of the Wheatstone bridge?





28

Discussion #12 –Exam 1 Review

6. How do measuring devices connect to circuits?



6. How do measuring devices connect to circuits?



NB: the resistance of an element can only be measured when the element is **disconnected** from **all** other circuit elements



6. How do measuring devices connect to circuits?



NB: 1. the ammeter must be connected in **series** with the circuit element

2. the ammeter should not restrict the flow of current (i.e. cause a voltage drop) – an ideal ammeter has **zero** resistance



6. How do measuring devices connect to circuits?



NB: 1. the voltmeter must be connected in parallel with the circuit element
2. the voltmeter should not draw any current away from the element

– an ideal voltmeter has infinite resistance



6. How do measuring devices connect to circuits?



NB: 1. the wattmeter must be connected in **parallel** with the circuit element, but also in **series** with the circuit.

– a wattmeter is simply the combination of a voltmeter and an ammeter



Exam 1 Review...Node Voltage

7. What is the node voltage method of circuit analysis?



Exam 1 Review...Node Voltage

- 7. What is the node voltage method of circuit analysis?
 - a) Find all unknown voltages
 - $i_a = 1$ mA, $i_b = 2$ mA, $\mathbf{R_1} = 1$ k Ω , $\mathbf{R_2} = 500\Omega$, $\mathbf{R_3} = 2.2$ k Ω , $\mathbf{R_4} = 4.7$ k Ω





Exam 1 Review...Node Voltage

- 7. What is the node voltage method of circuit analysis?
 - a) Find all unknown voltages

 $i_a = 1$ mA, $i_b = 2$ mA, $\mathbf{R_1} = 1$ k Ω , $\mathbf{R_2} = 500\Omega$, $\mathbf{R_3} = 2.2$ k Ω , $\mathbf{R_4} = 4.7$ k Ω



- Label currents and voltages (polarities "arbitrarily" chosen)
- . Choose Node c (\mathbf{v}_c) as the reference node $(\mathbf{v}_c = 0)$

B. Define remaining
$$n - 1$$
 (2) voltages

- **v**_a is **independent**
- **v**_b is **independent**
- Apply KCL at nodes **a** and **b**


Exam 1 Review...Node Voltage

- 7. What is the node voltage method of circuit analysis?
 - a) Find all unknown voltages

$$i_a = 1$$
mA, $i_b = 2$ mA, $\mathbf{R_1} = 1$ k Ω , $\mathbf{R_2} = 500\Omega$, $\mathbf{R_3} = 2.2$ k Ω , $\mathbf{R_4} = 4.7$ k Ω





Exam 1 Review...Node Voltage

- 7. What is the node voltage method of circuit analysis?
 - a) Find all unknown voltages
 - $i_a = 1$ mA, $i_b = 2$ mA, $\mathbf{R_1} = 1$ k Ω , $\mathbf{R_2} = 500\Omega$, $\mathbf{R_3} = 2.2$ k Ω , $\mathbf{R_4} = 4.7$ k Ω





Exam 1 Review...Node Voltage

- 7. What is the node voltage method of circuit analysis?
 - a) Find all unknown voltages
 - $i_a = 1$ mA, $i_b = 2$ mA, $\mathbf{R_1} = 1$ k Ω , $\mathbf{R_2} = 500\Omega$, $\mathbf{R_3} = 2.2$ k Ω , $\mathbf{R_4} = 4.7$ k Ω





39

ECEN 301

8. What is the mesh current method of circuit analysis?



- 8. What is the mesh current method of circuit analysis?
 - a) Find the mesh currents

$$V_s = 6V, I_s = 0.5A, R_1 = 3\Omega, R_2 = 8\Omega, R_3 = 6\Omega, R_4 = 4\Omega$$





- 8. What is the mesh current method of circuit analysis?
 - a) Find the mesh currents

 $\mathbf{V_s} = 6\mathbf{V}, \ \mathbf{I_s} = 0.5\mathbf{A}, \ \mathbf{R_1} = 3\Omega, \ \mathbf{R_2} = 8\Omega, \ \mathbf{R_3} = 6\Omega, \ \mathbf{R_4} = 4\Omega$



- 1. Mesh current directions given
- 2. Voltage polarities chosen and labeled
- 3. Identify n m (3) mesh currents

$$i_a$$
 is dependent ($i_a = i_s$)

- *i*_a is independent
- ➢ i_c is independent

4. Apply KVL around meshes **b** and **c**



- 8. What is the mesh current method of circuit analysis?
 - a) Find the mesh currents

 $V_s = 6V, I_s = 0.5A, R_1 = 3\Omega, R_2 = 8\Omega, R_3 = 6\Omega, R_4 = 4\Omega$





- 8. What is the mesh current method of circuit analysis?
 - a) Find the mesh currents

$$\mathbf{V_s} = 6\mathbf{V}, \mathbf{I_s} = 0.5\mathbf{A}, \mathbf{R_1} = 3\Omega, \mathbf{R_2} = 8\Omega, \mathbf{R_3} = 6\Omega, \mathbf{R_4} = 4\Omega$$



Express voltages in terms of currents $i_b(R_2 + R_3) - i_c R_3 = v_s + i_s R_2$

$$-i_b R_3 + i_c (R_1 + R_3 + R_4) = i_s R_1$$



 $\Delta \Delta$

- 8. What is the mesh current method of circuit analysis?
 - a) Find the mesh currents

$$V_s = 6V, I_s = 0.5A, R_1 = 3\Omega, R_2 = 8\Omega, R_3 = 6\Omega, R_4 = 4\Omega$$





9. What is the superposition method of circuit analysis?



9. What is the superposition method of circuit analysis?

- a) Use superposition to find $\mathbf{v}_{\mathbf{R}}$
- $i_s = 12A, v_s = 12V, R_1 = 1\Omega, R_2 = 0.3\Omega, R_3 = 0.23\Omega$





9. What is the superposition method of circuit analysis?

a) Use superposition to find $\mathbf{v}_{\mathbf{R}}$

 $i_s = 12A, v_s = 12V, R_1 = 1\Omega, R_2 = 0.3\Omega, R_3 = 0.23\Omega$



- 1. Remove all sources except i_s
 - Source \mathbf{v}_{s} is replaced with short circuit



9. What is the superposition method of circuit analysis?

a) Use superposition to find $\mathbf{v}_{\mathbf{R}}$

 $i_s = 12A, v_s = 12V, R_1 = 1\Omega, R_2 = 0.3\Omega, R_3 = 0.23\Omega$





9. What is the superposition method of circuit analysis?

- a) Use superposition to find $\mathbf{v}_{\mathbf{R}}$
- $i_s = 12A, v_s = 12V, R_1 = 1\Omega, R_2 = 0.3\Omega, R_3 = 0.23\Omega$



- 2. Remove all sources except \mathbf{v}_s
 - Source i_s is replaced with open circuit



9. What is the superposition method of circuit analysis?

a) Use superposition to find $\mathbf{v}_{\mathbf{R}}$

 $i_s = 12A, v_s = 12V, R_1 = 1\Omega, R_2 = 0.3\Omega, R_3 = 0.23\Omega$



KCL at Node a:

$$-i_{1} + i_{2} - i_{3} = 0$$

$$\frac{v_{R2}}{R_{1}} - \frac{v_{sR2}}{R_{2}} + \frac{v_{R2}}{R_{3}} = 0$$

$$v_{R2} \left(\frac{1}{R_{1}} + \frac{1}{R_{2}} + \frac{1}{R_{3}}\right) = \frac{v_{s}}{R_{2}}$$

$$v_{R2} = \frac{1}{8.68} \left(\frac{12}{0.3}\right)$$

$$= 4.61V$$



9. What is the superposition method of circuit analysis?

a) Use superposition to find $\mathbf{v}_{\mathbf{R}}$

$$i_s = 12A, v_s = 12V, R_1 = 1\Omega, R_2 = 0.3\Omega, R_3 = 0.23\Omega$$





Exam 1 Review...Source Transform

10. How are voltage sources transformed to current sources (and vice-versa)?





Exam 1 Review...Source Transform

10. How are voltage sources transformed to current sources (and vice-versa)?





54

ECEN 301

11. What is the Thévenin theorem?



11. What is the Thévenin theorem?

a) find i_L by finding the Thévenin equivalent circuit

 $v_s = 10V, R_1 = 4\Omega, R_2 = 6\Omega, R_3 = 10\Omega, R_L = 10\Omega$





11. What is the Thévenin theorem?

a) find i_L by finding the Thévenin equivalent circuit

 $v_s = 10V, R_1 = 4\Omega, R_2 = 6\Omega, R_3 = 10\Omega, R_L = 10\Omega$





11. What is the Thévenin theorem?

a) find i_L by finding the Thévenin equivalent circuit

 $v_s = 10V, R_1 = 4\Omega, R_2 = 6\Omega, R_3 = 10\Omega, R_L = 10\Omega$







11. What is the Thévenin theorem?

a) find i_L by finding the Thévenin equivalent circuit

 $v_s = 10V, R_1 = 4\Omega, R_2 = 6\Omega, R_3 = 10\Omega, R_L = 10\Omega$



1. Compute \mathbf{R}_{T} • Remove \mathbf{R}_{L} • Zero sources • Compute $\mathbf{R}_{T} = \mathbf{R}_{EQ}$

$$R_T = R_3 + R_1 \parallel R_2$$



59

11. What is the Thévenin theorem?

a) find i_L by finding the Thévenin equivalent circuit

 $v_s = 10V, R_1 = 4\Omega, R_2 = 6\Omega, R_3 = 10\Omega, R_L = 10\Omega$



1. Compute
$$\mathbf{R}_{T}$$

2. Compute \mathbf{v}_{T}

$$R_T = R_3 + R_1 \parallel R_2$$



ECEN 301

11. What is the Thévenin theorem?

a) find i_L by finding the Thévenin equivalent circuit

 $v_s = 10V, R_1 = 4\Omega, R_2 = 6\Omega, R_3 = 10\Omega, R_L = 10\Omega$



| 1. | Cor | mpute R _T |
|----|-------------------------------|-----------------------------|
| 2. | Compute v _T | |
| | a) | Remove the load |
| | 1 \ | |

b) Define
$$\mathbf{v}_{oc}$$

$$R_T = R_3 + R_1 \parallel R_2$$

ECEN 301



11. What is the Thévenin theorem?

a) find i_L by finding the Thévenin equivalent circuit

 $v_s = 10V, R_1 = 4\Omega, R_2 = 6\Omega, R_3 = 10\Omega, R_L = 10\Omega$



| 1. Compute | e R _T |
|------------|------------------|
|------------|------------------|

- 2. Compute $\mathbf{v}_{\mathbf{T}}$
 - a) Remove the load
 - b) Define **v**_{oc}
 - c) Choose a network analysis method
 - Voltage divider





62

ECEN 301

11. What is the Thévenin theorem?

a) find i_L by finding the Thévenin equivalent circuit

 $v_s = 10V, R_1 = 4\Omega, R_2 = 6\Omega, R_3 = 10\Omega, R_L = 10\Omega$



| 1. | Compute R _T | | | | |
|----|-------------------------------|--|--|--|--|
| 2. | Con | Compute $\mathbf{v}_{\mathbf{T}}$ | | | |
| | a) | Remove the load | | | |
| | b) | Define v _{oc} | | | |
| | c) | Choose a network analysis method | | | |
| | | Voltage divider | | | |
| | d) | $\mathbf{V}_{\mathbf{T}} = \mathbf{V}_{\mathbf{oc}}$ | | | |
| | | | | | |
| | | R | | | |

63

ECEN 301

11. What is the Thévenin theorem?

a) find i_L by finding the Thévenin equivalent circuit







64

11. What is the Thévenin theorem?

a) find i_L by finding the Thévenin equivalent circuit





65

ECEN 301

12. What is the Norton theorem?



12. What is the Norton theorem?

a) Find the Norton equivalent circuit

 $v_s = 6V, i_s = 2A, R_1 = 6\Omega, R_2 = 3\Omega, R_3 = 2\Omega, R_L = 10\Omega$





ECEN 301

12. What is the Norton theorem?

a) Find the Norton equivalent circuit

 $v_s = 6V, i_s = 2A, R_1 = 6\Omega, R_2 = 3\Omega, R_3 = 2\Omega, R_L = 10\Omega$







12. What is the Norton theorem?

a) Find the Norton equivalent circuit

 $v_s = 6V, i_s = 2A, R_1 = 6\Omega, R_2 = 3\Omega, R_3 = 2\Omega, R_L = 10\Omega$



Compute R_N
 Remove R_L
 Zero sources



12. What is the Norton theorem?

a) Find the Norton equivalent circuit

 $\mathbf{v_s} = 6\mathbf{V}, \, \mathbf{i_s} = 2\mathbf{A}, \, \mathbf{R_1} = 6\Omega, \, \mathbf{R_2} = 3\Omega, \, \mathbf{R_3} = 2\Omega, \, \mathbf{R_L} = 10\Omega$



1. Compute
$$\mathbf{R}_{\mathbf{N}}$$

• Remove $\mathbf{R}_{\mathbf{L}}$
• Zero sources
• Compute $\mathbf{R}_{\mathbf{N}} = \mathbf{R}_{\mathbf{EQ}}$
 $\mathbf{R}_{N} = \mathbf{R}_{3} + \mathbf{R}_{1} || \mathbf{R}_{2}$



12. What is the Norton theorem?

a) Find the Norton equivalent circuit

 $v_s = 6V, i_s = 2A, R_1 = 6\Omega, R_2 = 3\Omega, R_3 = 2\Omega, R_L = 10\Omega$





12. What is the Norton theorem?

a) Find the Norton equivalent circuit

 $v_s = 6V, i_s = 2A, R_1 = 6\Omega, R_2 = 3\Omega, R_3 = 2\Omega, R_L = 10\Omega$



- 1.Compute \mathbf{R}_N 2.Compute i_N
 - a) Short circuit the load
 - b) Define i_{sc}


12. What is the Norton theorem?

a) Find the Norton equivalent circuit

 $v_s = 6V, i_s = 2A, R_1 = 6\Omega, R_2 = 3\Omega, R_3 = 2\Omega, R_L = 10\Omega$



Electrical Engineering Computer Engineering

12. What is the Norton theorem?

a) Find the Norton equivalent circuit

 $v_s = 6V, i_s = 2A, R_1 = 6\Omega, R_2 = 3\Omega, R_3 = 2\Omega, R_L = 10\Omega$





12. What is the Norton theorem?

a) Find the Norton equivalent circuit

 $v_s = 6V, i_s = 2A, R_1 = 6\Omega, R_2 = 3\Omega, R_3 = 2\Omega, R_L = 10\Omega$





75

12. What is the Norton theorem?

a) Find the Norton equivalent circuit

 $\mathbf{v_s} = 6\mathbf{V}, \, \mathbf{i_s} = 2\mathbf{A}, \, \mathbf{R_1} = 6\Omega, \, \mathbf{R_2} = 3\Omega, \, \mathbf{R_3} = 2\Omega, \, \mathbf{R_L} = 10\Omega$



Discussion #12 –Exam 1 Review

Electrical Engineering Computer Engineering

12. What is the Norton theorem?

a) Find the Norton equivalent circuit





ECEN 301

12. What is the Norton theorem?

a) Find the Norton equivalent circuit



Discussion #12 –Exam 1 Review

Electrical Engineering Computer Engineering

12. What is the Norton theorem?

a) Find the Norton equivalent circuit

 $\mathbf{v_s} = 6\mathbf{V}, \, \mathbf{i_s} = 2\mathbf{A}, \, \mathbf{R_1} = 6\Omega, \, \mathbf{R_2} = 3\Omega, \, \mathbf{R_3} = 2\Omega, \, \mathbf{R_L} = 10\Omega$



. Compute
$$i_N$$

c) Choose a network analysis method
• Node voltage
d) $i_N = i_{sc}$

$$i_N = i_{sc}$$

= 1.5A



ECEN 301

12. What is the Norton theorem?

a) Find the Norton equivalent circuit

$$v_s = 6V, i_s = 2A, R_1 = 6\Omega, R_2 = 3\Omega, R_3 = 2\Omega, R_L = 10\Omega$$





ECEN 301

13. What is the maximum power theorem?



13. What is the maximum power theorem?

a) Find the maximum power delivered to the load $v_s = 18V, R_1 = 3\Omega, R_2 = 6\Omega, R_3 = 2\Omega$





13. What is the maximum power theorem?

a) Find the maximum power delivered to the load

 $v_s = 18V, R_1 = 3\Omega, R_2 = 6\Omega, R_3 = 2\Omega$





13. What is the maximum power theorem?

a) Find the maximum power delivered to the load

 $v_s = 18V, R_1 = 3\Omega, R_2 = 6\Omega, R_3 = 2\Omega$



- 1. Find Thévenin equivalent circuit
- 2. Set $\mathbf{R}_{\mathbf{L}} = \mathbf{R}_{\mathbf{T}}$





ECEN 301

Network analysis with controlled sources:
 Initially treat controlled sources as ideal sources
 In addition to equations obtained by node/mesh analysis there will be the constraint equation (the controlled source equation)
 Substitute constraint equation into node/mesh

Substitute constraint equation into node/mesh equations







14. find the gain $(\mathbf{A}_{\mathbf{v}} = \mathbf{v}_{\mathbf{out}} / \mathbf{v}_{\mathbf{in}})$

 \mathbf{A} **R**₁ = 1Ω, **R**₂ = 0.5Ω, **R**₃ = 0.25Ω, **R**₄ = 0.25Ω, **R**₅ = 0.25Ω



Choose mesh analysis – simpler than node analysis

- 1. Mesh current directions chosen
- 2. Voltage polarities chosen and labeled
- 3. Identify $\mathbf{n} \mathbf{m}$ (3) mesh currents
 - $\rightarrow i_{a}$ is independent
 - \rightarrow i_{a} is independent
 - $i_{\rm c}$ is independent
- 4. Apply KVL around meshes **a**, **b**, and **c**







88

ECEN 301

14. find the gain (
$$A_v = v_{out}/v_{in}$$
)
 $A_R_1 = 1\Omega, R_2 = 0.5\Omega, R_3 = 0.25\Omega, R_4 = 0.25\Omega, R_5 = 0.25\Omega$
 $+R_4^-$
 $v_{in} + i_a R_2 + v_2 + i_c R_5 + v_{out}$
 $= -1.5i_a + 2i_b - 0.25i_c = 0$
 $i_a - 1.25i_b + 0.5i_c = 0$
 $i_a = 0.88v_{in}A$
 $i_b = 0.64v_{in}A$
 $i_c = -0.16v_{in}A$



89

ECEN 301





90

ECEN 301





91

14. find the gain (
$$A_v = v_{out}/v_{in}$$
)
 $\land R_1 = 1\Omega, R_2 = 0.5\Omega, R_3 = 0.25\Omega, R_4 = 0.25\Omega, R_5 = 0.25\Omega$





92

ECEN 301

Find the Thévenin equivalent resistance $v_s = 20V, R_1 = 1M\Omega, R_2 = 2k\Omega, R_3 = 3k\Omega, R_4 = 6k\Omega, R_5 = 6k\Omega, R_6 = 3k\Omega, R_7 = 2k\Omega, R_L = 10\Omega$





Find the Thévenin equivalent resistance $v_s = 20V, R_1 = 1M\Omega, R_2 = 2k\Omega, R_3 = 3k\Omega, R_4 = 6k\Omega, R_5 = 6k\Omega, R_6 = 3k\Omega, R_7 = 2k\Omega, R_L = 10\Omega$





Find the Thévenin equivalent resistance $v_s = 20V, R_1 = 1M\Omega, R_2 = 2k\Omega, R_3 = 3k\Omega, R_4 = 6k\Omega, R_5 = 6k\Omega, R_6 = 3k\Omega, R_7 = 2k\Omega, R_L = 10\Omega$





Find the Thévenin equivalent resistance $v_s = 20V, R_1 = 1M\Omega, R_2 = 2k\Omega, R_3 = 3k\Omega, R_4 = 6k\Omega, R_5 = 6k\Omega, R_6 = 3k\Omega, R_7 = 2k\Omega, R_L = 10\Omega$



Discussion #12 –Exam 1 Review



Find the Thévenin equivalent resistance $v_s = 20V, R_1 = 1M\Omega, R_2 = 2k\Omega, R_3 = 3k\Omega, R_4 = 6k\Omega, R_5 = 6k\Omega, R_6 = 3k\Omega, R_7 = 2k\Omega, R_L = 10\Omega$



97

ECEN 301

Find the Thévenin equivalent resistance $v_s = 20V, R_1 = 1M\Omega, R_2 = 2k\Omega, R_3 = 3k\Omega, R_4 = 6k\Omega, R_5 = 6k\Omega, R_6 = 3k\Omega, R_7 = 2k\Omega, R_L = 10\Omega$



Discussion #12 –Exam 1 Review



Find the Thévenin equivalent resistance $v_s = 20V, R_1 = 1M\Omega, R_2 = 2k\Omega, R_3 = 3k\Omega, R_4 = 6k\Omega, R_5 = 6k\Omega, R_6 = 3k\Omega, R_7 = 2k\Omega, R_L = 10\Omega$



Discussion #12 –Exam 1 Review

99

Electrical Engineering Computer Engineering

Find the Thévenin equivalent resistance $v_s = 20V, R_1 = 1M\Omega, R_2 = 2k\Omega, R_3 = 3k\Omega, R_4 = 6k\Omega, R_5 = 6k\Omega, R_6 = 3k\Omega, R_7 = 2k\Omega, R_L = 10\Omega$





ECEN 301