

Schedule...

Date	Day	Class No.	Title	Chapters	HW Due date	Lab Due date	Exam
15 Oct	Wed	13	Phasors	4.4			EXAM 1
16 Oct	Thu						
17 Oct	Fri		Recitation				
18 Oct	Sat						
19 Oct	Sun						
20 Oct	Mon	14	AC Circuit Analysis	4.5		NO LAB	
21 Oct	Tue					NO LAB	
22 Oct	Wed	15	Transient Response 1 st Order Circuits	5.4			

Imaginary

JS-H 1: 16


16 But, exerting all my powers to call upon God to deliver me out of the power of this enemy which had seized upon me, and at the very moment when I was ready to sink into despair and abandon myself to destruction—not to an **imaginary** ruin, but to the power of some actual being from the unseen world, who had such marvelous power as I had never before felt in any being—just at this moment of great alarm, I saw a pillar of light exactly over my head, above the brightness of the sun, which descended gradually until it fell upon me.

Lecture 13 – Network Analysis with Capacitors and Inductors

Phasors

Euler's Identity

◆ Appendix A reviews complex numbers

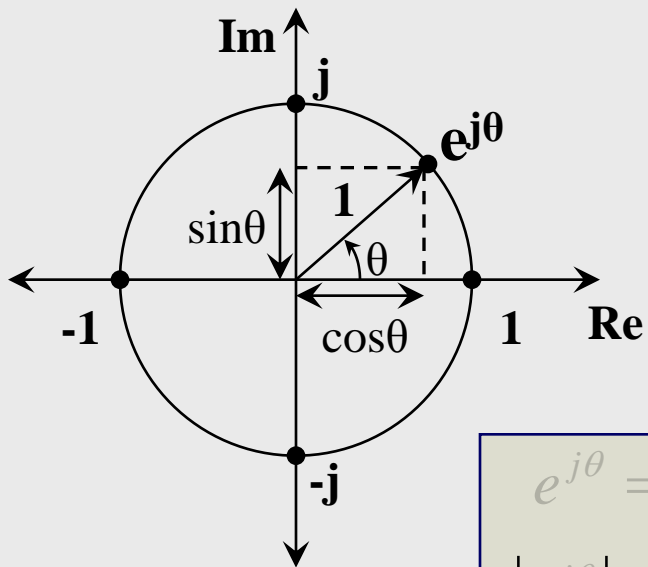

Complex exponential ($e^{j\theta}$) is a point on the complex plane

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$|e^{j\theta}| = 1 \rightarrow |\cos \theta + j \sin \theta| = \sqrt{\cos^2 \theta + \sin^2 \theta} = 1$$

$$Ae^{j\theta} = A \cos \theta + jA \sin \theta$$

$$= A \angle \theta$$

Phasors

- ◆ Rewrite the expression for a **general sinusoid signal**:

$$A \cos(\omega t + \theta) = \text{Re}\{Ae^{j(\omega t + \theta)}\}$$

magnitude Angle (or argument)


Complex phasor notation for the **simplification**:

$$A \cos(\omega t + \theta) \rightarrow A \angle \theta = Ae^{j\theta}$$

NB: The $e^{j\omega t}$ term is **implicit** (it is there but not written)


Frequency Domain

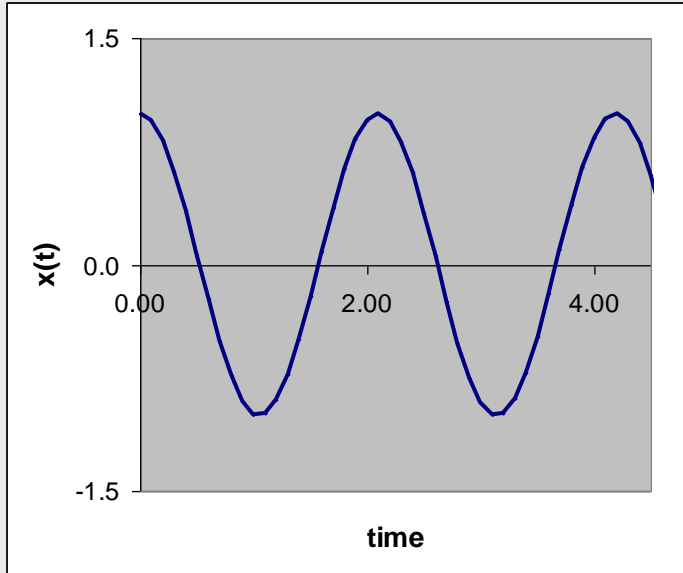Graphing in the frequency domain: helpful in order to understand Phasors



$\cos(\omega_0 t)$


Time domain

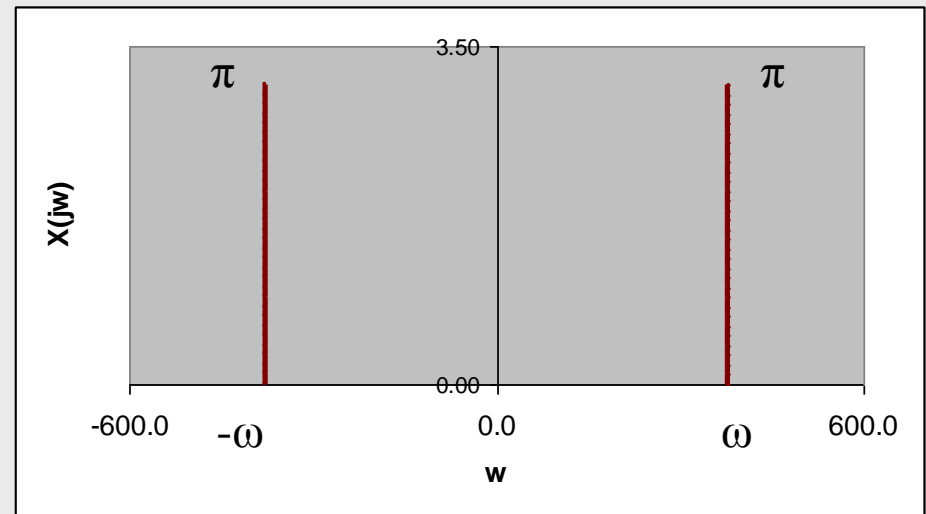

$\pi[\delta(\omega - \omega_0) + \delta(\omega + \omega_0)]$

Frequency domain

Electromagnetic Spectrum

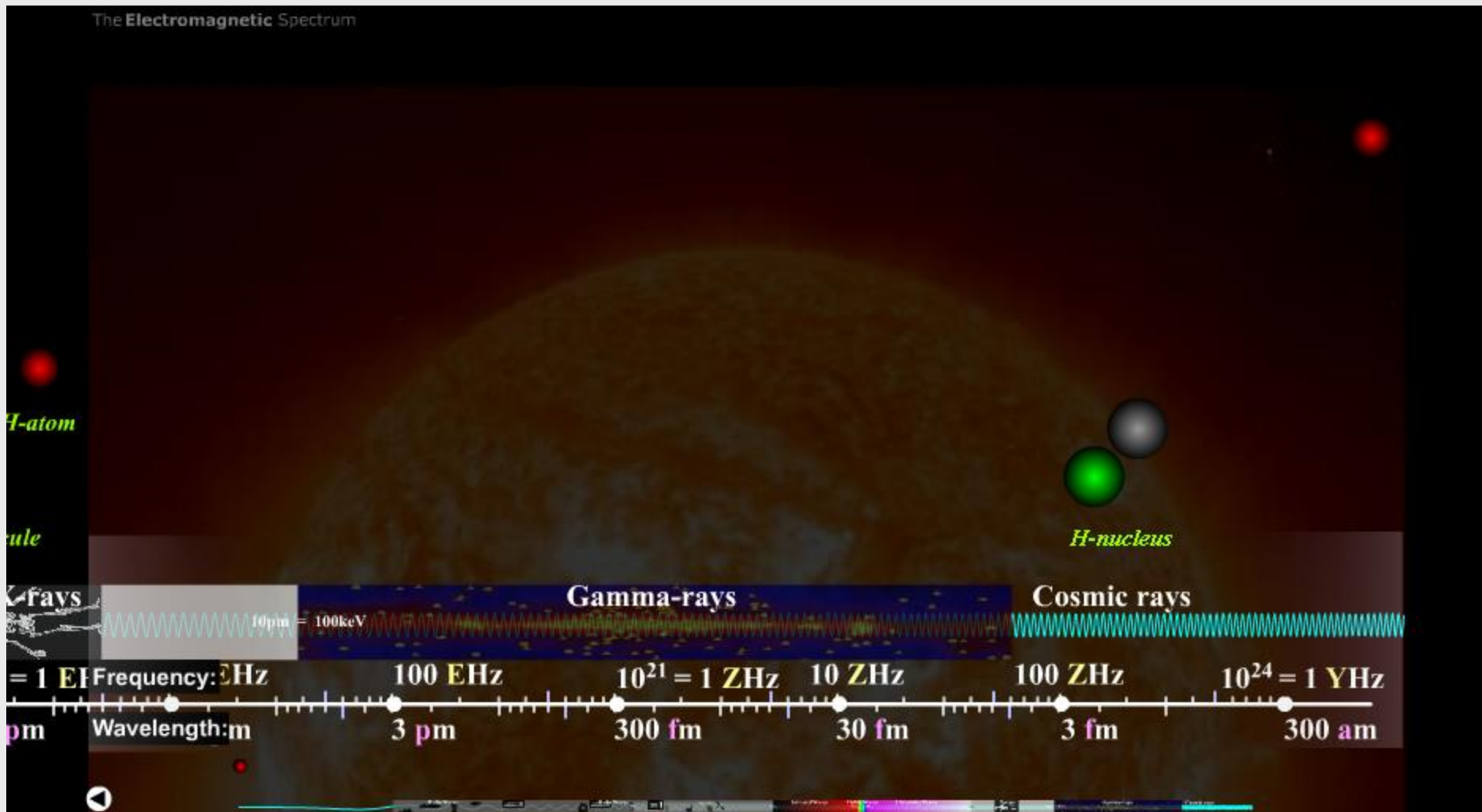

Phasors


1. Any sinusoidal signal can be represented by either:
 - ◆ **Time-domain form**: $v(t) = A\cos(\omega t + \theta)$
 - ◆ **Frequency-domain form**: $V(j\omega) = Ae^{j\theta} = A\angle\theta$
2. **Phasor**: a complex number expressed in polar form consisting of:
 - ◆ **Magnitude (A)**
 - ◆ **Phase angle (θ)**
3. Phasors do not explicitly include the sinusoidal frequency (ω) but this information is still important

Phasors

◆ **Example1:** compute the phasor voltage for the equivalent voltage $\mathbf{v}_s(\mathbf{t})$

▲ $\mathbf{v}_1(\mathbf{t}) = 15\cos(377\mathbf{t}+\pi/4)$

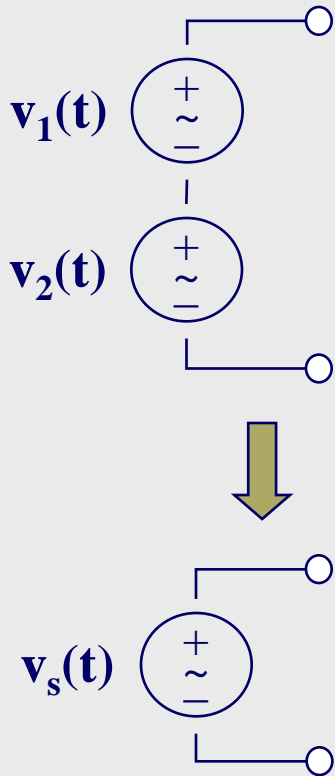▲ $\mathbf{v}_2(\mathbf{t}) = 15\cos(377\mathbf{t}+\pi/12)$




Phasors

◆ **Example1:** compute the phasor voltage for the equivalent voltage $\mathbf{v}_s(\mathbf{t})$

▲ $\mathbf{v}_1(\mathbf{t}) = 15\cos(377\mathbf{t}+\pi/4)$

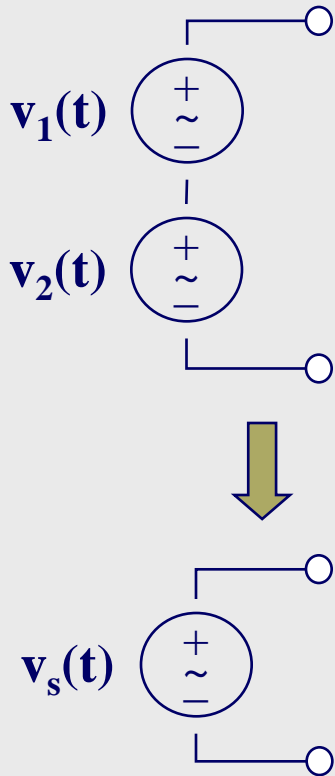▲ $\mathbf{v}_2(\mathbf{t}) = 15\cos(377\mathbf{t}+\pi/12)$



1. Write voltages in phasor notation


$$\begin{aligned} V_1(j\omega) &= 15e^{j\pi/4} \\ &= 15\angle\frac{\pi}{4} \text{ V} \\ V_2(j\omega) &= 15e^{j\pi/12} \\ &= 15\angle\frac{\pi}{12} \text{ V} \end{aligned}$$

Phasors

◆ **Example1:** compute the phasor voltage for the equivalent voltage $\mathbf{v}_s(t)$

▲ $\mathbf{v}_1(t) = 15\cos(377t+\pi/4)$

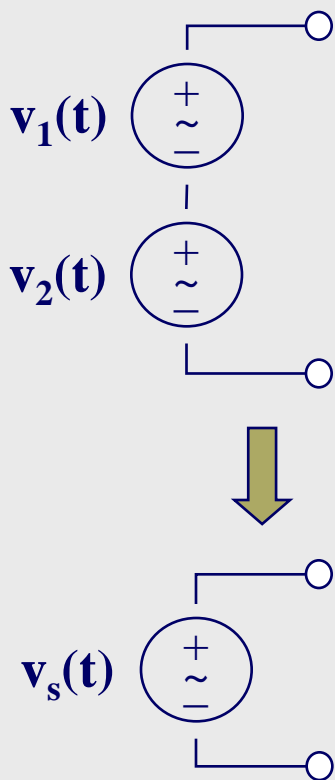▲ $\mathbf{v}_2(t) = 15\cos(377t+\pi/12)$



1. Write voltages in phasor notation
2. Convert phasor voltages from polar to rectangular form (see Appendix A)

$$V_1(j\omega) = 15 \angle \frac{\pi}{4} \text{ V}$$

Convert to rectangular r :

$$\begin{aligned} V_1(j\omega) &= 15 \cos\left(\frac{\pi}{4}\right) + j15 \sin\left(\frac{\pi}{4}\right) \\ &= 10.61 + j10.61 \text{ V} \end{aligned}$$

$$V_2(j\omega) = 15 \angle \frac{\pi}{12} \text{ V}$$

Convert to rectangular r :


$$\begin{aligned} V_2(j\omega) &= 15 \cos\left(\frac{\pi}{12}\right) + j15 \sin\left(\frac{\pi}{12}\right) \\ &= 14.49 + j3.88 \text{ V} \end{aligned}$$

Phasors

◆ **Example1:** compute the phasor voltage for the equivalent voltage $\mathbf{v}_s(\mathbf{t})$

▲ $\mathbf{v}_1(\mathbf{t}) = 15\cos(377\mathbf{t}+\pi/4)$

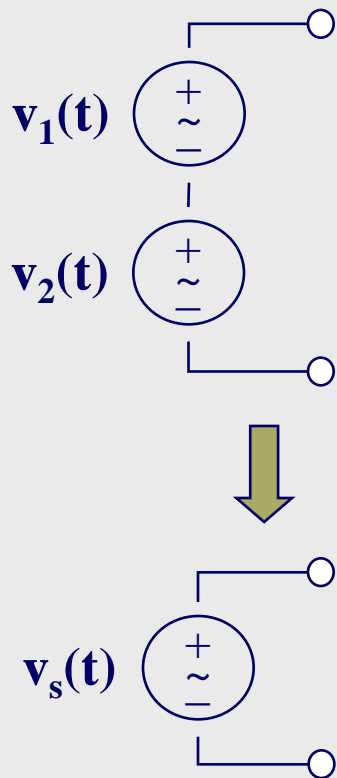▲ $\mathbf{v}_2(\mathbf{t}) = 15\cos(377\mathbf{t}+\pi/12)$



1. Write voltages in phasor notation
2. Convert phasor voltages from polar to rectangular form (see Appendix A)
3. Combine voltages


$$\begin{aligned} V_s(j\omega) &= V_1(j\omega) + V_2(j\omega) \\ &= 25.10 + j14.49 \end{aligned}$$

Phasors

◆ **Example1:** compute the phasor voltage for the equivalent voltage $\mathbf{v}_s(\mathbf{t})$

▲ $\mathbf{v}_1(\mathbf{t}) = 15\cos(377\mathbf{t}+\pi/4)$

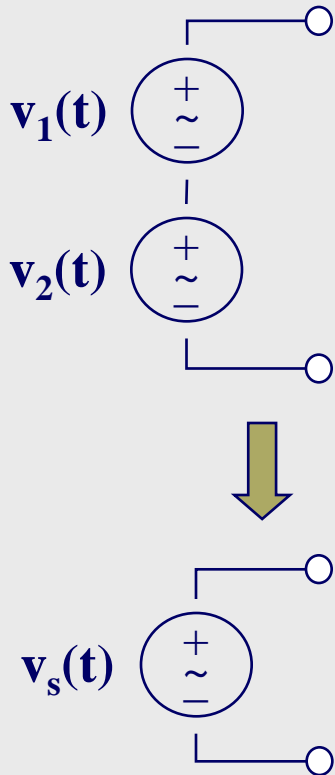▲ $\mathbf{v}_2(\mathbf{t}) = 15\cos(377\mathbf{t}+\pi/12)$



1. Write voltages in phasor notation
2. Convert phasor voltages from polar to rectangular form (see Appendix A)
3. Combine voltages
4. Convert rectangular back to polar

$$V_s(j\omega) = 25.10 + j14.49$$

Convert to polar :

$$r = \sqrt{(25.10)^2 + (14.49)^2}$$
$$= 28.98$$

$$\theta = \tan^{-1}\left(\frac{14.49}{25.10}\right)$$
$$= \frac{\pi}{6}$$

$$V_s(j\omega) = 28.98 \angle \frac{\pi}{6}$$


Phasors

◆ **Example1:** compute the phasor voltage for the equivalent voltage $\mathbf{v}_s(t)$

▲ $\mathbf{v}_1(t) = 15\cos(377t + \pi/4)$

▲ $\mathbf{v}_2(t) = 15\cos(377t + \pi/12)$

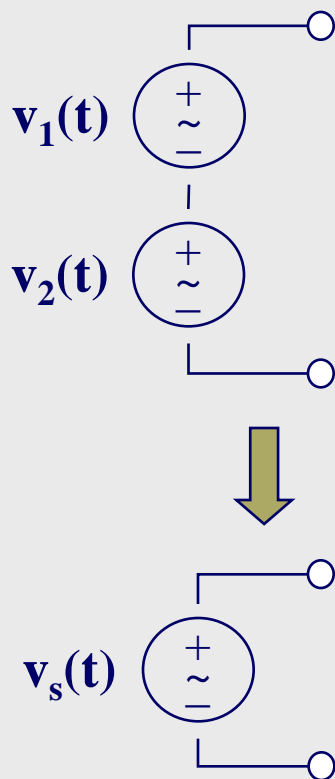1. Write voltages in phasor notation
2. Convert phasor voltages from polar to rectangular form (see Appendix A)
3. Combine voltages
4. Convert rectangular back to polar
5. Convert from phasor to time domain



$$V_S(j\omega) = 28.98 \angle \frac{\pi}{6}$$
$$v_s(t) = 28.98 \cos\left(377t + \frac{\pi}{6}\right)$$

Bring ωt back


NB: the answer is **NOT** simply the addition of the amplitudes of $\mathbf{v}_1(t)$ and $\mathbf{v}_2(t)$ (i.e. $15 + 15$), and the addition of their phases (i.e. $\pi/4 + \pi/12$)

Phasors


◆ **Example1:** compute the phasor voltage for the equivalent voltage $\mathbf{v}_s(t)$

▲ $\mathbf{v}_1(t) = 15\cos(377t + \pi/4)$

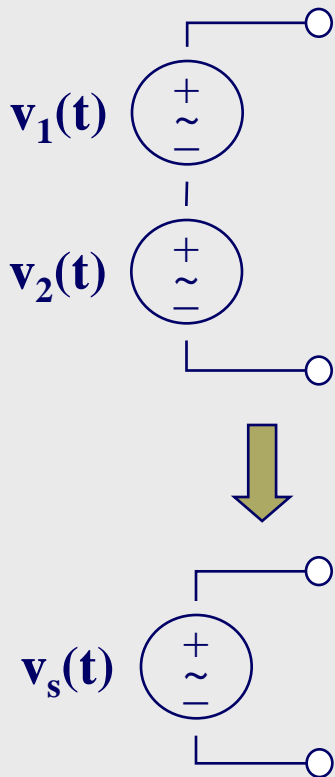▲ $\mathbf{v}_2(t) = 15\cos(377t + \pi/12)$



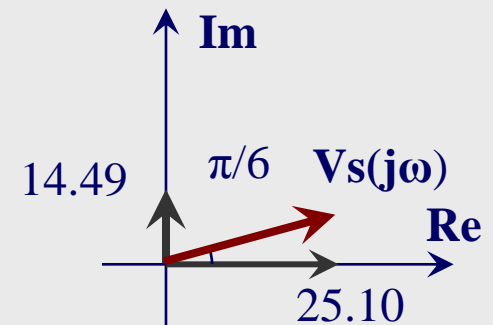
$$V_s(j\omega) = 28.98 \angle \frac{\pi}{6}$$
$$v_s(t) = 28.98 \cos\left(377t + \frac{\pi}{6}\right)$$



Phasors of Different Frequencies

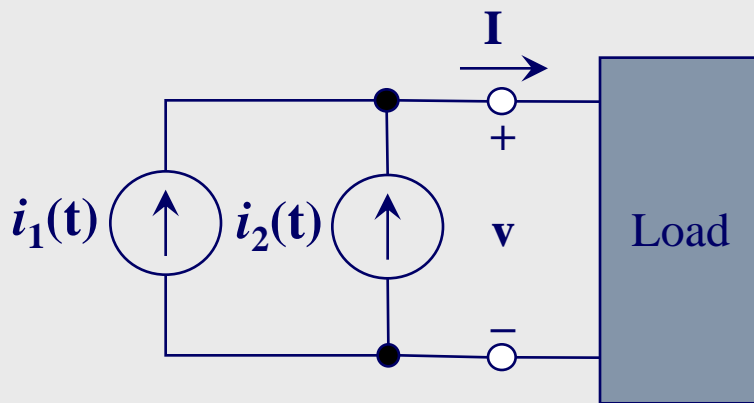Superposition of AC signals: when signals do **not** have the same frequency (ω) the $e^{j\omega t}$ term in the phasors can no longer be implicit




$$\begin{aligned} i(t) &= i_1(t) + i_2(t) \\ I(j\omega) &= I_1(j\omega_1) + I_2(j\omega_2) \\ &= A_1 e^{j0} e^{j\omega_1 t} + A_2 e^{j0} e^{j\omega_2 t} \\ &\neq A_1 e^{j0} + A_2 e^{j0} \end{aligned}$$

NB: $e^{j\omega t}$ can no longer be implicit

Phasors of Different Frequencies

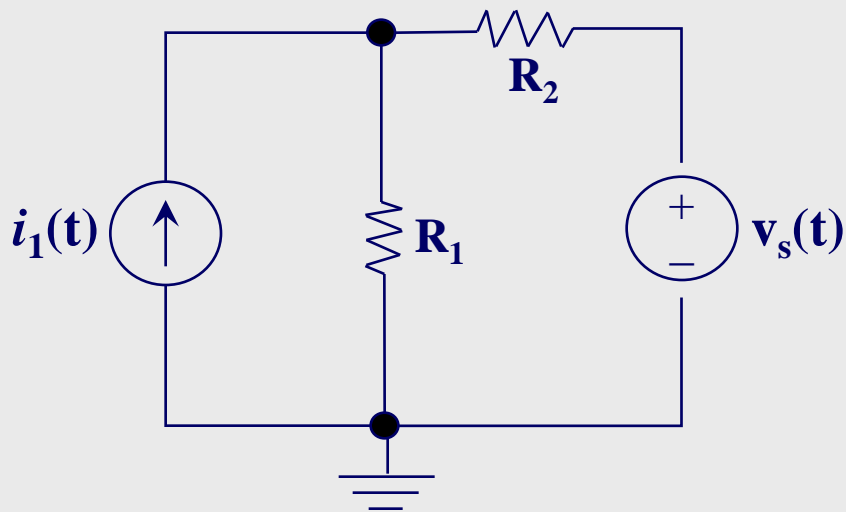Superposition of AC signals: when signals do **not** have the same frequency (ω) solve the circuit separately for each different frequency (ω) – then add the individual results




Phasors of Different Frequencies

◆ **Example2:** compute the resistor voltages

▲ $i_s(t) = 0.5\cos[2\pi(100t)]$ A

▲ $v_s(t) = 20\cos[2\pi(1000t)]$ V


▲ $R_1 = 150\Omega$, $R_2 = 50\Omega$

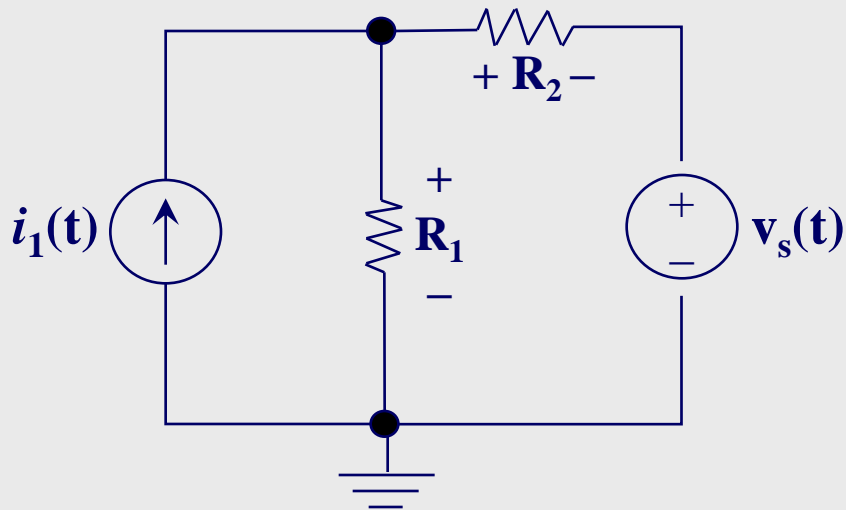

Phasors of Different Frequencies

◆ **Example2:** compute the resistor voltages

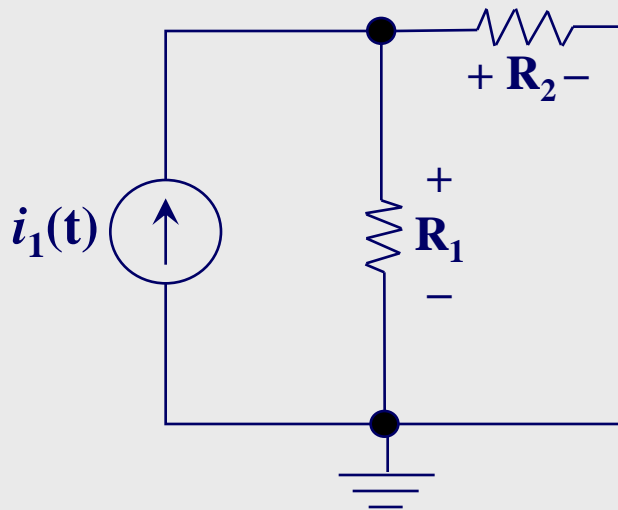- ▲ $i_s(t) = 0.5\cos[2\pi(100t)]$ A
- ▲ $v_s(t) = 20\cos[2\pi(1000t)]$ V
- ▲ $R_1 = 150\Omega$, $R_2 = 50\Omega$




1. Since the sources have different frequencies ($\omega_1 = 2\pi*100$) and ($\omega_2 = 2\pi*1000$) use superposition
 - first consider the ($\omega_1 = 2\pi*100$) part of the circuit
 - When $v_s(t) = 0$ – short circuit

Phasors of Different Frequencies

◆ **Example2:** compute the resistor voltages

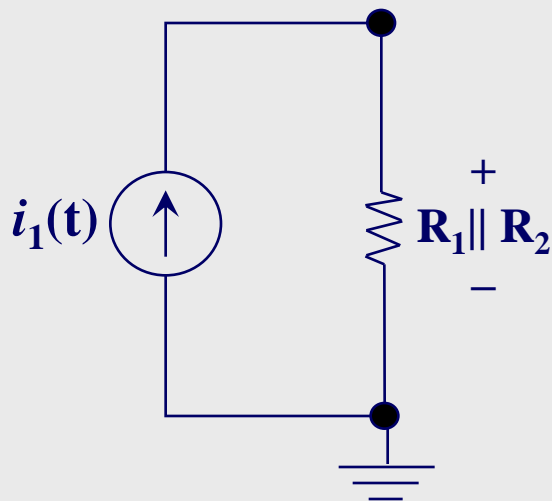- ▲ $i_s(t) = 0.5\cos[2\pi(100t)]$ A
- ▲ $v_s(t) = 20\cos[2\pi(1000t)]$ V
- ▲ $R_1 = 150\Omega$, $R_2 = 50\Omega$



1. Since the sources have different frequencies ($\omega_1 = 2\pi \cdot 100$) and ($\omega_2 = 2\pi \cdot 1000$) use superposition
 - first consider the ($\omega_1 = 2\pi \cdot 100$) part of the circuit

$$\begin{aligned} I_s(j\omega) &= 0.5\angle 0 \\ V_{I1}(j\omega) &= V_{I2}(j\omega) = I_s \cdot R_1 \parallel R_2 \\ &= I_s \cdot \frac{R_1 R_2}{R_1 + R_2} \\ &= 0.5\angle 0 \cdot \frac{(50)(150)}{(50) + (150)} \\ &= 18.75\angle 0 \end{aligned}$$


Phasors of Different Frequencies

◆ **Example2:** compute the resistor voltages

▲ $i_s(t) = 0.5\cos[2\pi(100t)]$ A

▲ $v_s(t) = 20\cos[2\pi(1000t)]$ V

▲ $R_1 = 150\Omega$, $R_2 = 50\Omega$

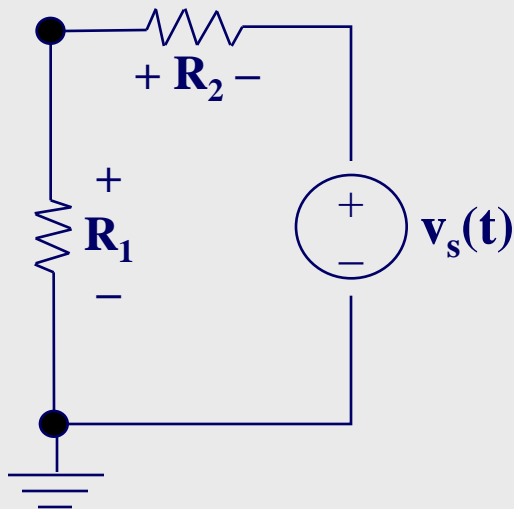

1. Since the sources have different frequencies ($\omega_1 = 2\pi \cdot 100$) and ($\omega_2 = 2\pi \cdot 1000$) use superposition

- first consider the ($\omega_1 = 2\pi \cdot 100$) part of the circuit
- Next consider the ($\omega_2 = 2\pi \cdot 1000$) part of the circuit

$$\begin{aligned}
 V_s(j\omega) &= 20 \angle 0 \\
 V_{v1}(j\omega) &= V_s \cdot \frac{R_1}{R_1 + R_2} \\
 &= 20 \angle 0 \cdot \frac{(150)}{(50) + (150)} \\
 &= 15 \angle 0
 \end{aligned}$$

$$\begin{aligned}
 V_s(j\omega) &= 20 \angle 0 \\
 V_{v2}(j\omega) &= -V_s \cdot \frac{R_2}{R_1 + R_2} \\
 &= -20 \angle 0 \cdot \frac{(50)}{(50) + (150)} \\
 &= -5 \angle 0 \\
 &= 5 \angle \pi
 \end{aligned}$$


Phasors of Different Frequencies

◆ **Example2:** compute the resistor voltages

▲ $i_s(t) = 0.5\cos[2\pi(100t)]$ A

▲ $v_s(t) = 20\cos[2\pi(1000t)]$ V

▲ $R_1 = 150\Omega$, $R_2 = 50\Omega$

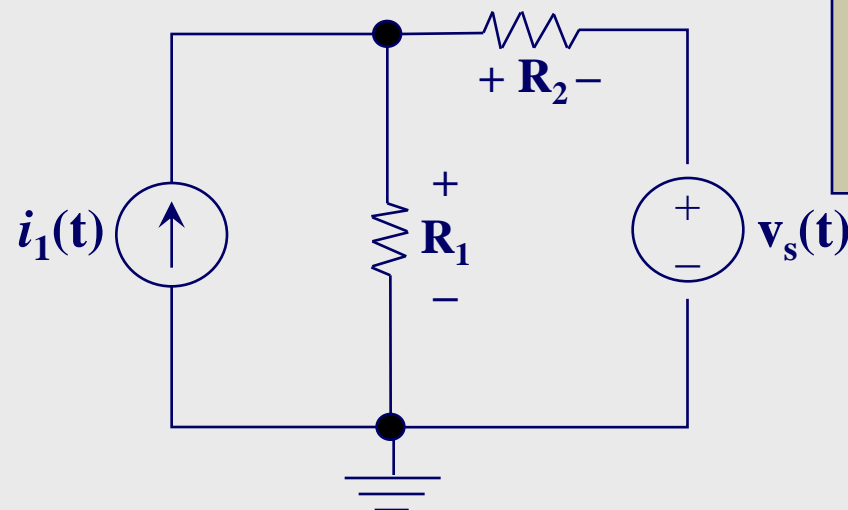

1. Since the sources have different frequencies ($\omega_1 = 2\pi \cdot 100$) and ($\omega_2 = 2\pi \cdot 1000$) use superposition
 - first consider the ($\omega_1 = 2\pi \cdot 100$) part of the circuit
 - Next consider the ($\omega_2 = 2\pi \cdot 1000$) part of the circuit
 - Add the two together

$$V_1(j\omega) = V_{I1}(j\omega) + V_{V1}(j\omega)$$

$$= 18.75\angle 0 + 15\angle 0$$

$$v_1(t) = 18.75 \cos[2\pi(100t)] + 15 \cos[2\pi(1000t)]$$

$$V_2(j\omega) = V_{I2}(j\omega) + V_{V2}(j\omega)$$


$$= 18.75\angle 0 - 5\angle 0$$

$$v_1(t) = 18.75 \cos[2\pi(100t)] - 5 \cos[2\pi(1000t)]$$

Impedance

Impedance: complex resistance (has no physical significance)

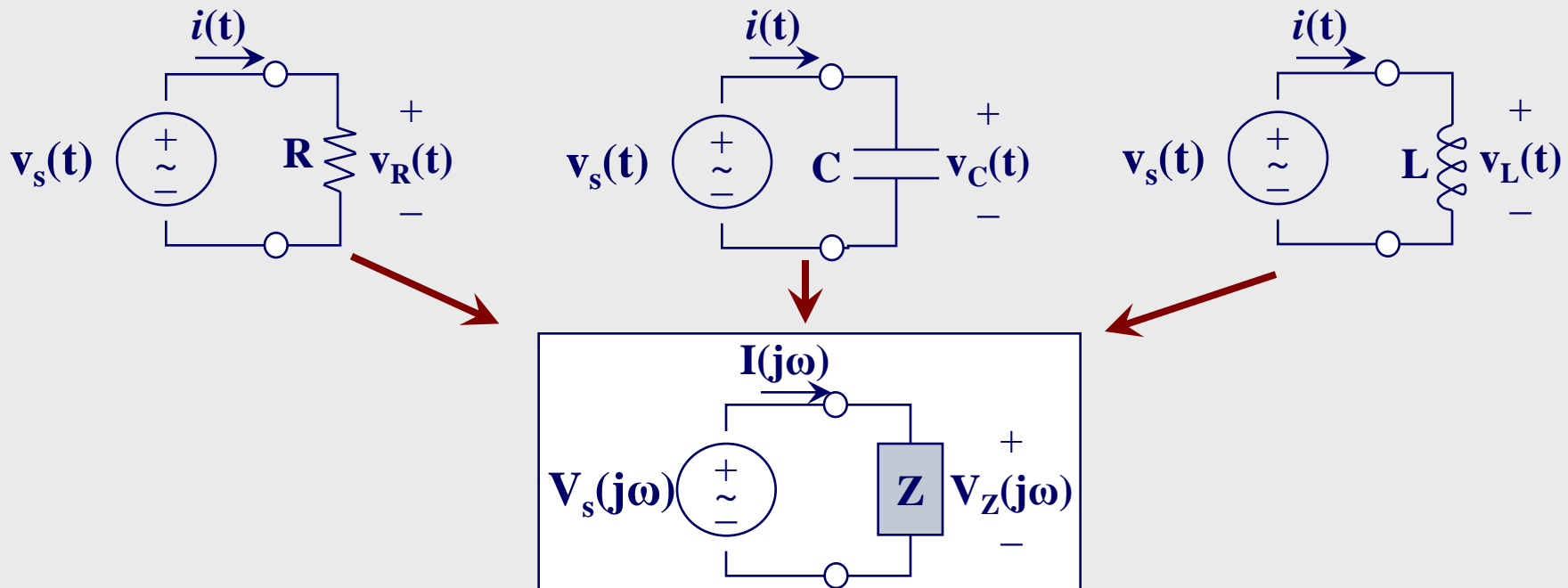
- ▲ will allow us to use network analysis methods such as node voltage, mesh current, etc.
- ▲ Capacitors and inductors act as **frequency-dependent** resistors



Impedance – Resistors


Impedance of a Resistor:

▲ Consider Ohm's Law in phasor form:

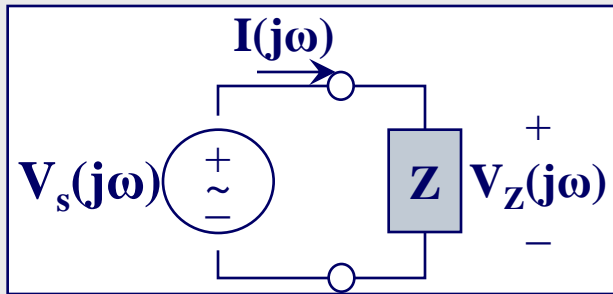


$$\begin{aligned} v_s(t) &= A \cos(\omega t) \\ i(t) &= \frac{v_s(t)}{R} \\ &= \frac{A}{R} \cos(\omega t) \end{aligned}$$

Phasor

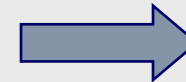
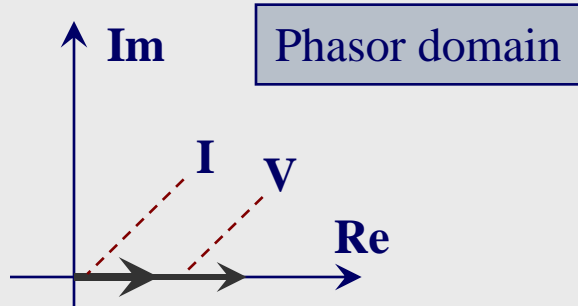
$$\begin{aligned} V_Z(j\omega) &= A \angle 0 \\ I_Z(j\omega) &= \frac{A}{R} \angle 0 \end{aligned}$$




$$Z_R(j\omega) = \frac{V_Z(j\omega)}{I_Z(j\omega)} = R$$

NB: Ohm's Law works the same in DC and AC

Impedance – Inductors


Impedance of an Inductor:

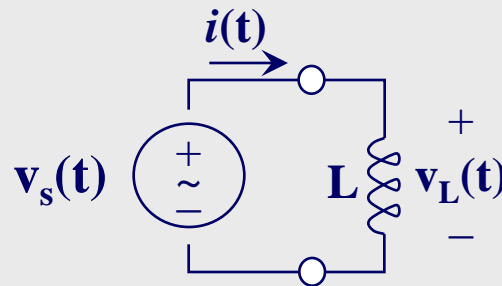▲ First consider voltage and current in the **time-domain**



$$\begin{aligned}v_L(t) &= L \frac{di_L(t)}{dt} = v_s(t) \\i_L(t) &= \frac{1}{L} \int v_L(\tau) d\tau \\&= \frac{1}{L} \int A \cos(\omega\tau) d\tau \\&= \frac{A}{\omega L} \sin(\omega t)\end{aligned}$$

NB: current is shifted
90° from voltage

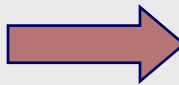


$$\begin{aligned}v_s(t) &= v_L(t) = A \cos(\omega t) \\i_L(t) &= \frac{A}{\omega L} \sin(\omega t) \\&= \frac{A}{\omega L} \cos\left(\omega t - \frac{\pi}{2}\right)\end{aligned}$$



Impedance – Inductors

Impedance of an Inductor:

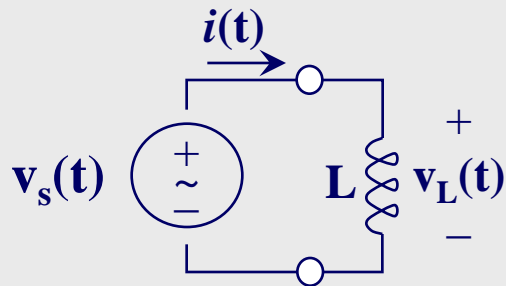▲ Now consider voltage and current in the **phasor-domain**



Phasor

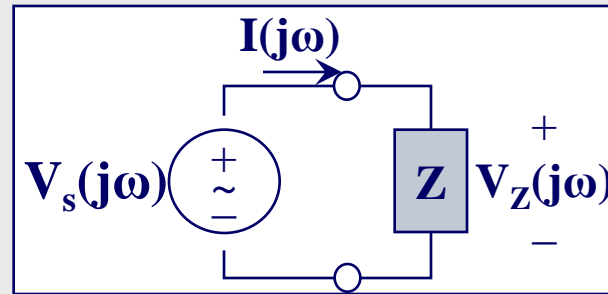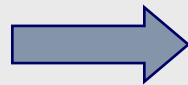


Phasor domain

$$v_s(t) = v_L(t) = A \cos(\omega t)$$

$$i_L(t) = \frac{A}{\omega L} \sin(\omega t)$$

$$= \frac{A}{\omega L} \cos\left(\omega t - \frac{\pi}{2}\right)$$


Phasor

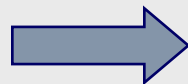

$$V_Z(j\omega) = A \angle 0$$

$$I_Z(j\omega) = \frac{A}{\omega L} \angle -\frac{\pi}{2}$$

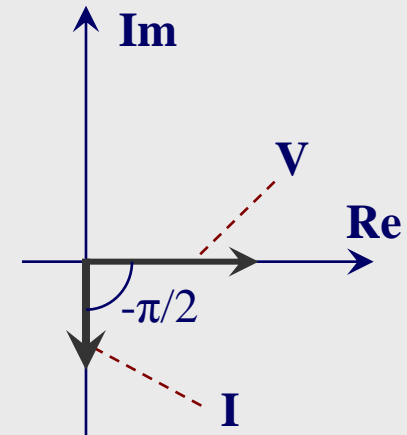
$$Z_L(j\omega) = \frac{V_Z(j\omega)}{I_Z(j\omega)} = j\omega L$$



Impedance – Capacitors

Impedance of a capacitor:

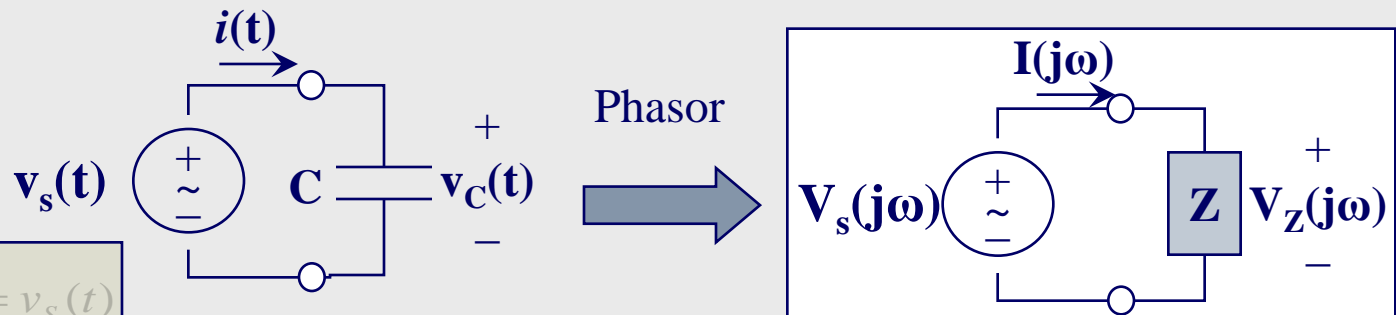▲ First consider voltage and current in the **time-domain**



$$\begin{aligned}v_C(t) &= \frac{1}{C} \int i_C(\tau) d\tau = v_s(t) \\i_C(t) &= C \frac{dv_C(t)}{dt} \\&= C \frac{d}{dt} [A \cos(\omega t)] \\&= -C [A \omega \sin(\omega t)] \\&= \omega C A \cos\left(\omega t + \frac{\pi}{2}\right)\end{aligned}$$


Phasor
→

$$\begin{aligned}V_Z(j\omega) &= A \angle 0 \\I_Z(j\omega) &= \omega C A \angle \frac{\pi}{2}\end{aligned}$$

Impedance – Capacitors

Impedance of a capacitor:

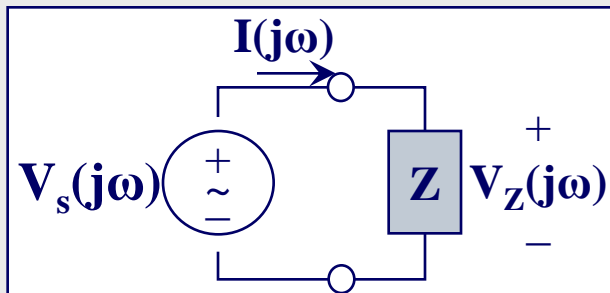▶ Next consider voltage and current in the **phasor-domain**




$$V_Z(j\omega) = A \angle 0$$

$$I_Z(j\omega) = \omega C A \angle \frac{\pi}{2}$$

$$\begin{aligned} Z_L(j\omega) &= \frac{V_Z(j\omega)}{I_Z(j\omega)} \\ &= \frac{1}{\omega C} \angle -\frac{\pi}{2} \\ &= \frac{-j}{\omega C} \\ &= \frac{1}{j\omega C} \end{aligned}$$




Phasor domain

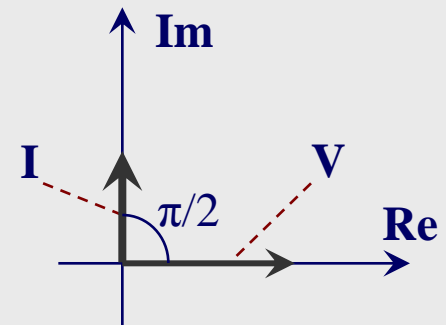

$$-j = e^{-j\frac{\pi}{2}} = \frac{1}{j}$$

Impedance

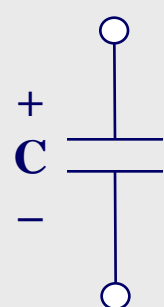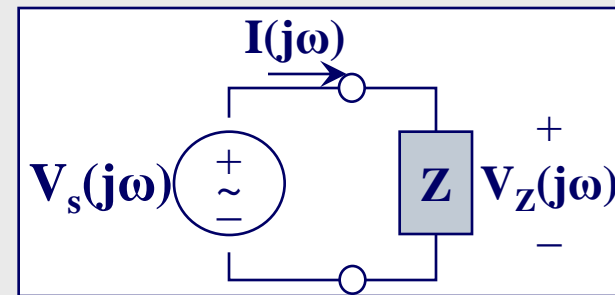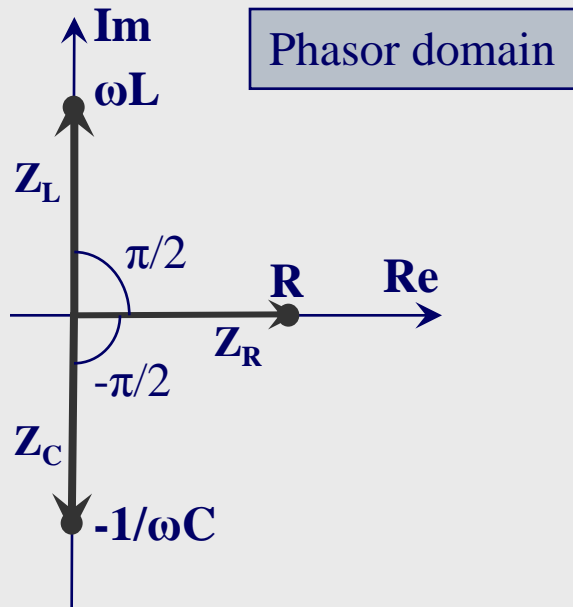Impedance of resistors, inductors, and capacitors





$$Z_R(j\omega) = R$$

$$Z_L(j\omega) = j\omega L$$

$$Z_C(j\omega) = \frac{1}{j\omega C}$$

Impedance

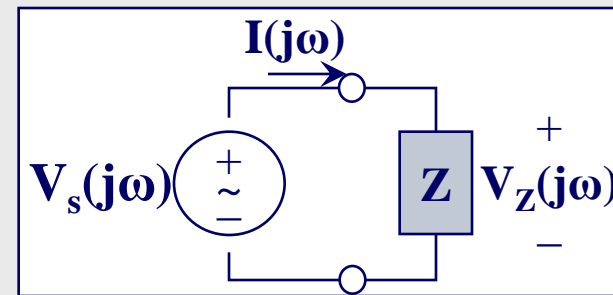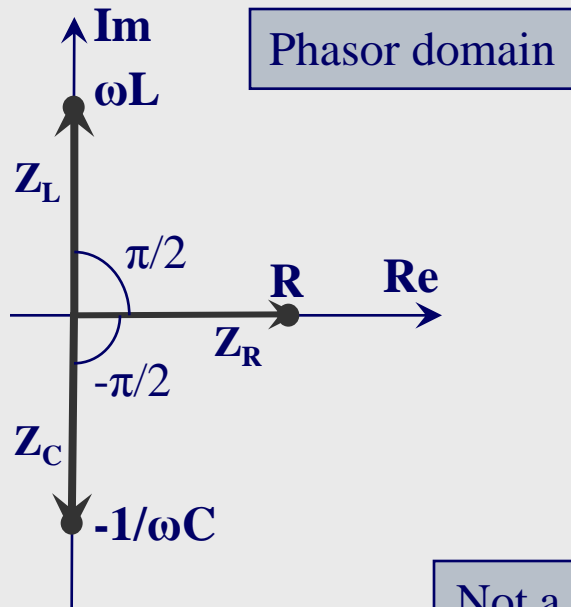Impedance of resistors, inductors, and capacitors



Impedance in general :
 $Z(j\omega) = R(j\omega) + jX(j\omega)$

Not a phasor but a complex number

AC resistance


reactance

Impedance


Practical capacitors: in practice capacitors contain a real component (represented by a resistive impedance Z_R)

- ▲ At **high frequencies** or **high capacitances**
 - **ideal** capacitor acts like a **short circuit**
- ▲ At **low frequencies** or **low capacitances**
 - **ideal** capacitor acts like an **open circuit**

Ideal Capacitor

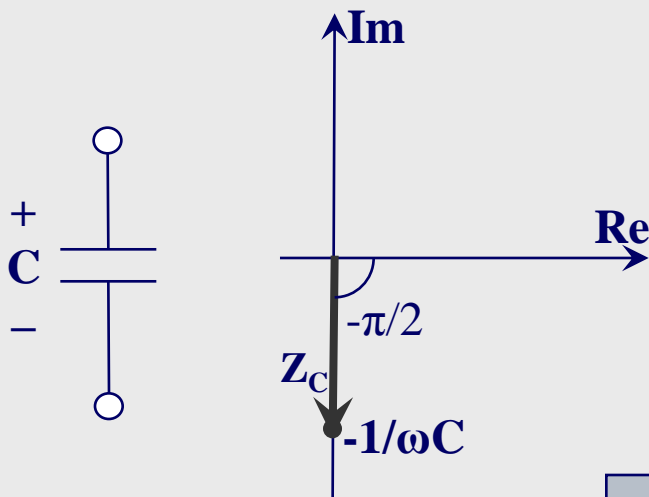

Practical Capacitor

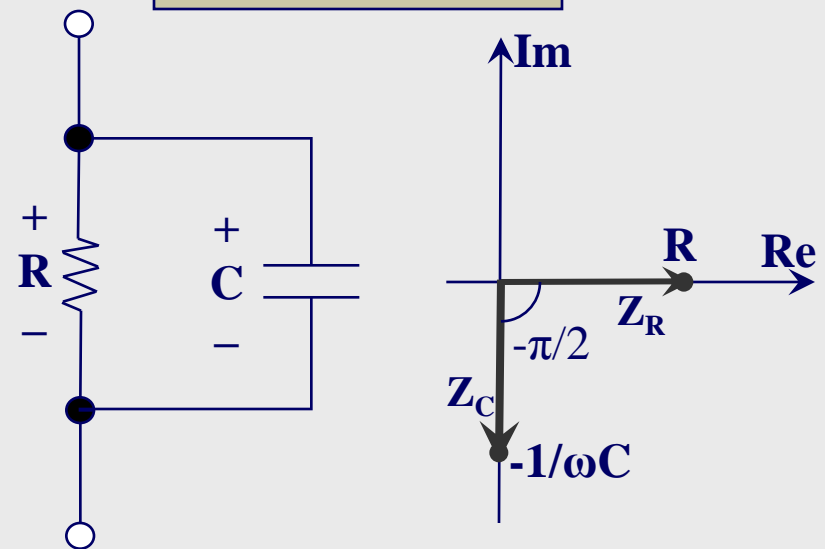


NB: the ratio of Z_C to Z_R is highly frequency dependent

Impedance


Practical inductors: in practice inductors contain a real component (represented by a resistive impedance Z_R)

- ▲ At **low frequencies** or **low inductances** Z_R has a strong influence
 - Ideal inductor acts like a **short circuit**
- ▲ At **high frequencies** or **high inductances** Z_L dominates Z_R
 - Ideal inductor acts like an **open circuit**
 - At high frequencies a capacitor is also needed to correctly model a practical inductor

Ideal Inductor

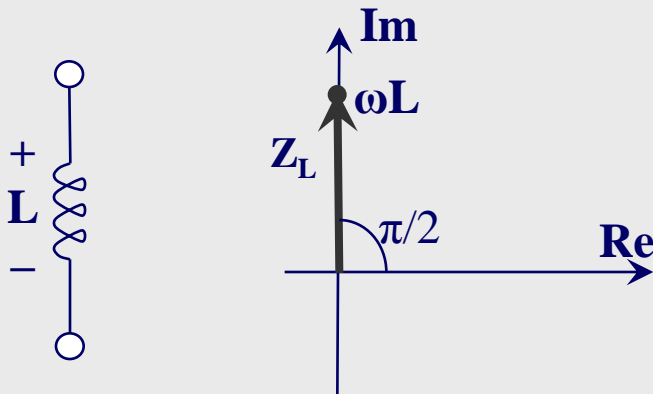

Practical Inductor

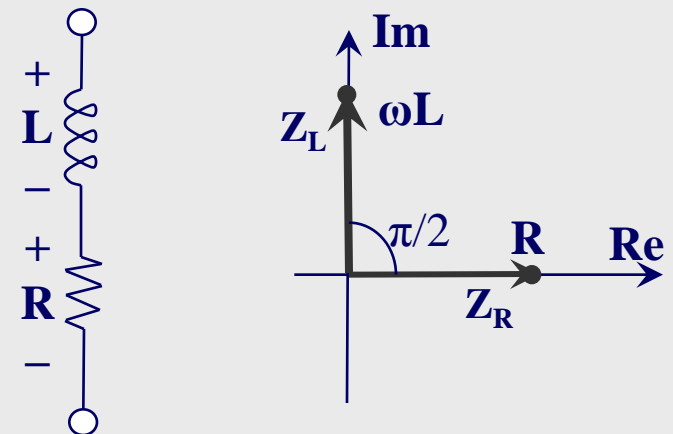


NB: the ratio of Z_L to Z_R is highly frequency dependent

Impedance

◆ Example3: impedance of a practical capacitor

▲ Find the impedance

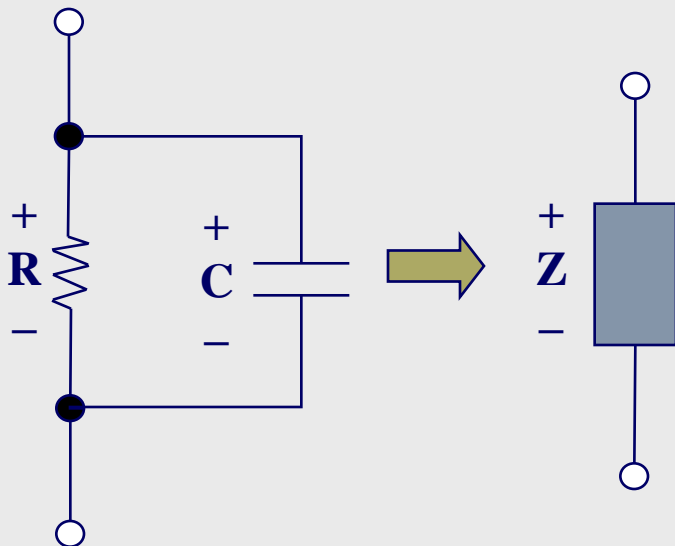▲ $\omega = 377$ rad/s, $C = 1\text{nF}$, $R = 1\text{M}\Omega$




Impedance

◆ Example3: impedance of a practical capacitor

▲ Find the impedance

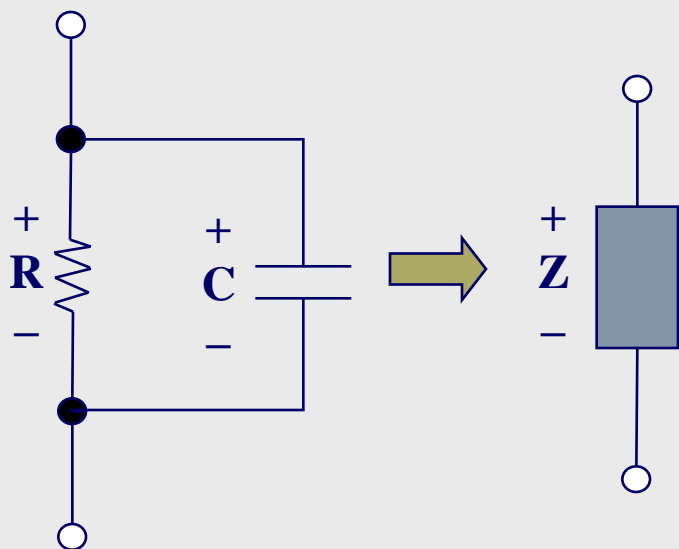▲ $\omega = 377$ rad/s, $C = 1\text{nF}$, $R = 1\text{M}\Omega$




$$\begin{aligned} Z &= Z_R \parallel Z_C \\ &= \frac{R \cdot (1/j\omega C)}{R + (1/j\omega C)} \\ &= \frac{R}{1 + j\omega CR} \\ &= \frac{10^6}{1 + j(377)(10^{-9})(10^6)} \\ &= \frac{10^6}{1 + j0.377} \\ &= 9.36 \times 10^5 \angle (-0.36) \Omega \end{aligned}$$

Impedance

◆ **Example4:** find the equivalent impedance (Z_{EQ})

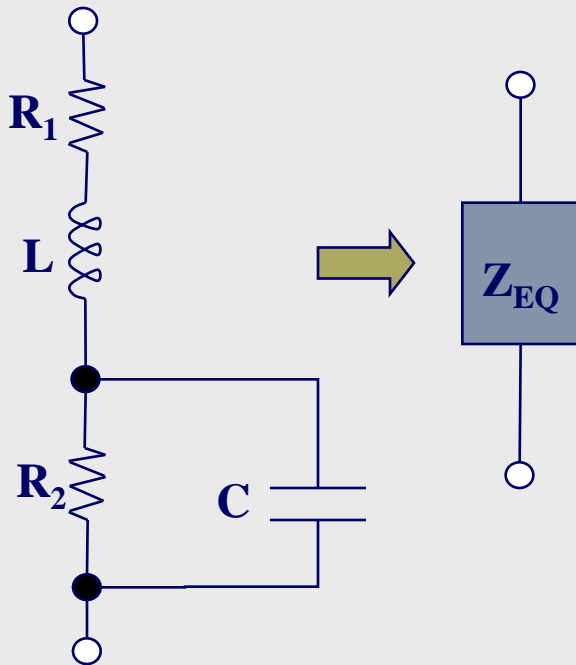
▲ $\omega = 10^4$ rad/s, $C = 10\mu\text{F}$, $R_1 = 100\Omega$, $R_2 = 50\Omega$, $L = 10\text{mH}$



Impedance

◆ **Example4:** find the equivalent impedance (Z_{EQ})

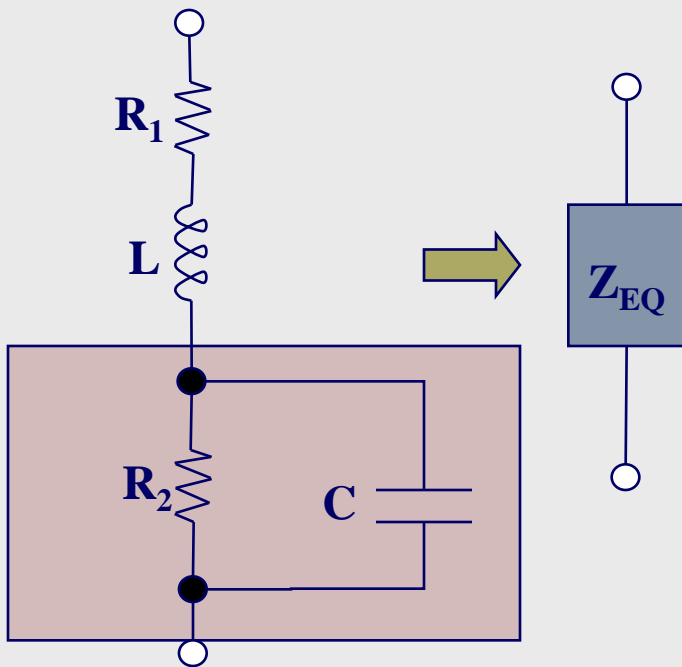▲ $\omega = 10^4$ rads/s, $C = 10\mu\text{F}$, $R_1 = 100\Omega$, $R_2 = 50\Omega$, $L = 10\text{mH}$




$$\begin{aligned} Z_{EQ1} &= Z_{R2} \parallel Z_C \\ &= \frac{R_2 (1/j\omega C)}{R_2 + (1/j\omega C)} \\ &= \frac{R_2}{1 + j\omega C R_2} \\ &= \frac{50}{1 + j(10^4)(10 \times 10^{-6})(50)} \\ &= \frac{50}{1 + j5} \\ &= 1.92 - j9.62 \\ &= 9.81 \angle (-1.37) \Omega \end{aligned}$$

Impedance

◆ **Example4:** find the equivalent impedance (Z_{EQ})

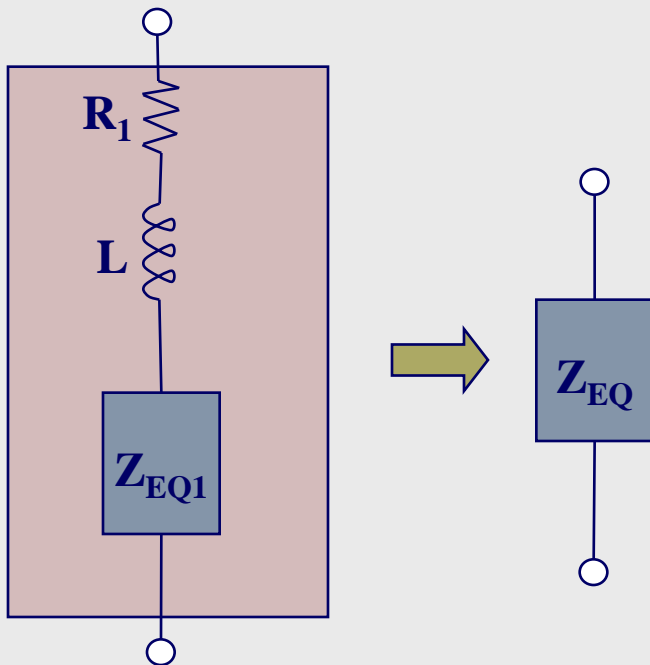▲ $\omega = 10^4$ rads/s, $C = 10\mu\text{F}$, $R_1 = 100\Omega$, $R_2 = 50\Omega$, $L = 10\text{mH}$



$$\begin{aligned} Z_{EQ} &= Z_{R1} + Z_L + Z_{EQ1} \\ &= R_1 + j\omega L + 9.81\angle(-1.37) \\ &= 100 + j(10^4)(10^{-2}) + 1.92 - j9.62 \\ &= 101.92 + j90.38 \\ &= 136.2\angle 0.723 \Omega \end{aligned}$$

NB: at this frequency (ω) the circuit has an **inductive impedance** (reactance or phase is positive)

$$Z_{EQ1} = 9.81\angle(-1.37) \Omega$$