

Schedule...

Date	Day	Class No.	Title	Chapters	HW Due date	Lab Due date	Exam
22 Oct	Wed	15	Transient Response 1 st Order Circuits	5.3 – 5.4			
23 Oct	Thu						
24 Oct	Fri		Recitation				
25 Oct	Sat						
26 Oct	Sun						
27 Oct	Mon	16	Sinusoidal Frequency Response	6.1		LAB 5	
28 Oct	Tue						
29 Oct	Wed	17	Operational Amplifiers	8.1 – 8.2			

Good, Better, Best

Elder Oaks (October 2007):

As we consider various choices, we should remember that it is not enough that something is **good**. Other choices are **better**, and still others are **best**. Even though a particular choice is more costly, its far greater value may make it the **best** choice of all.



I have never known of a man who looked back on his working life and said, "I just didn't spend enough time with my job."

Lecture 15 – Transient Response of 1st Order Circuits

DC Steady-State
Transient Response

1st Order Circuits

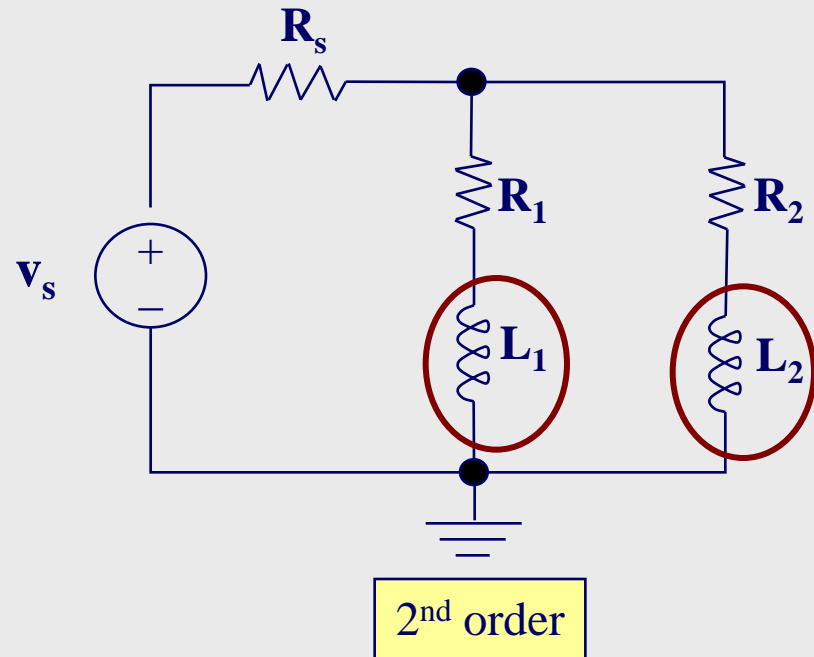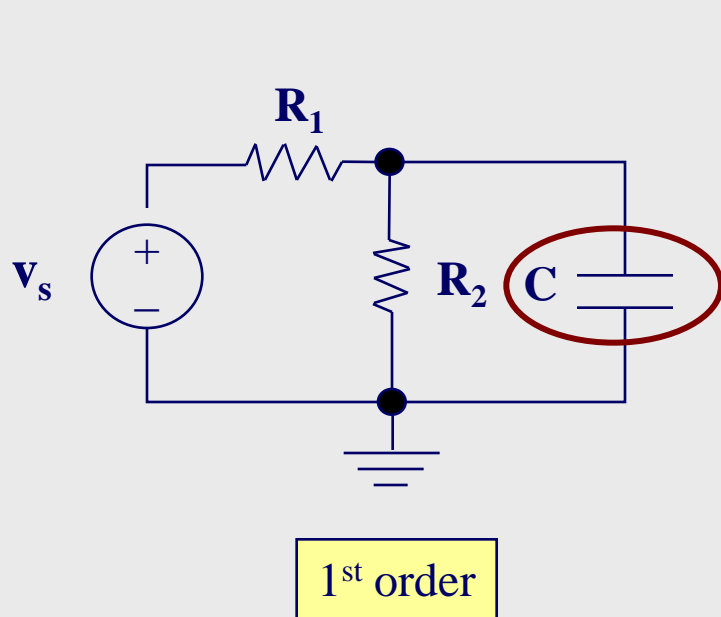
Electric circuit 1st order system: any circuit containing a **single** energy storing element (either a **capacitor** or an **inductor**) and any number of **sources** and **resistors**



Capacitor/Inductor Voltages/Currents

Review of capacitor/inductor currents and voltages


▲ exponential growth/decay

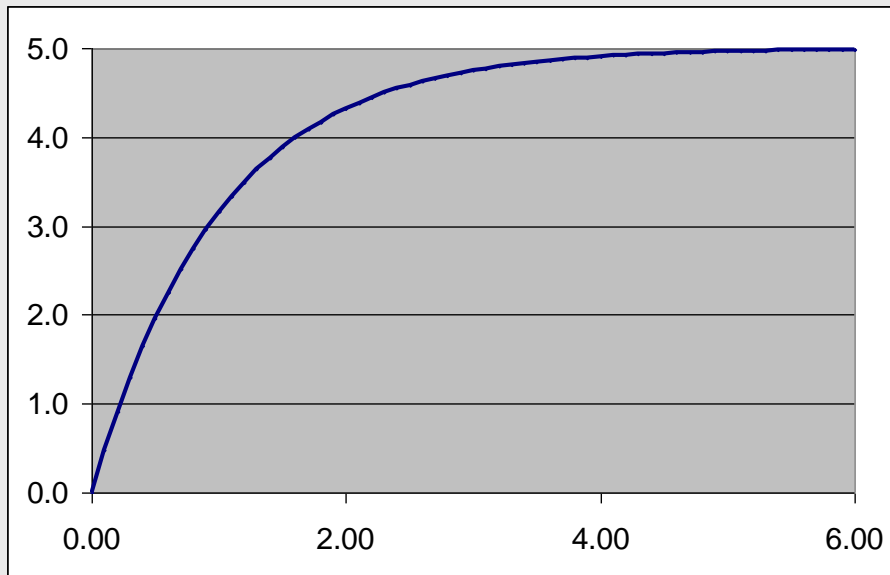

Capacitor voltage $v_C(t)$

Inductor current $i_L(t)$

NB: neither can change instantaneously

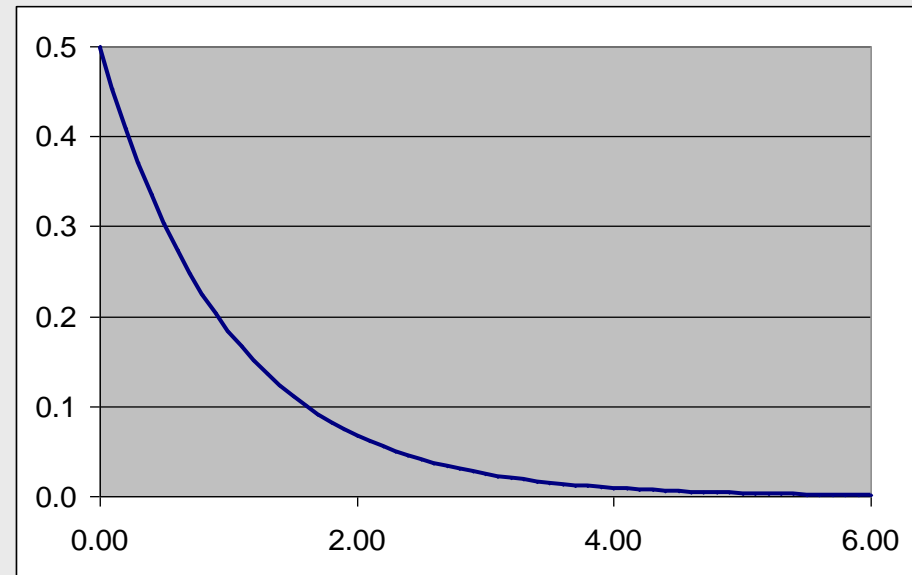

Capacitor current $i_C(t)$


Inductor voltage $v_L(t)$

NB: both can change instantaneously

Transient Response

Transient response of a circuit consists of 3 parts:

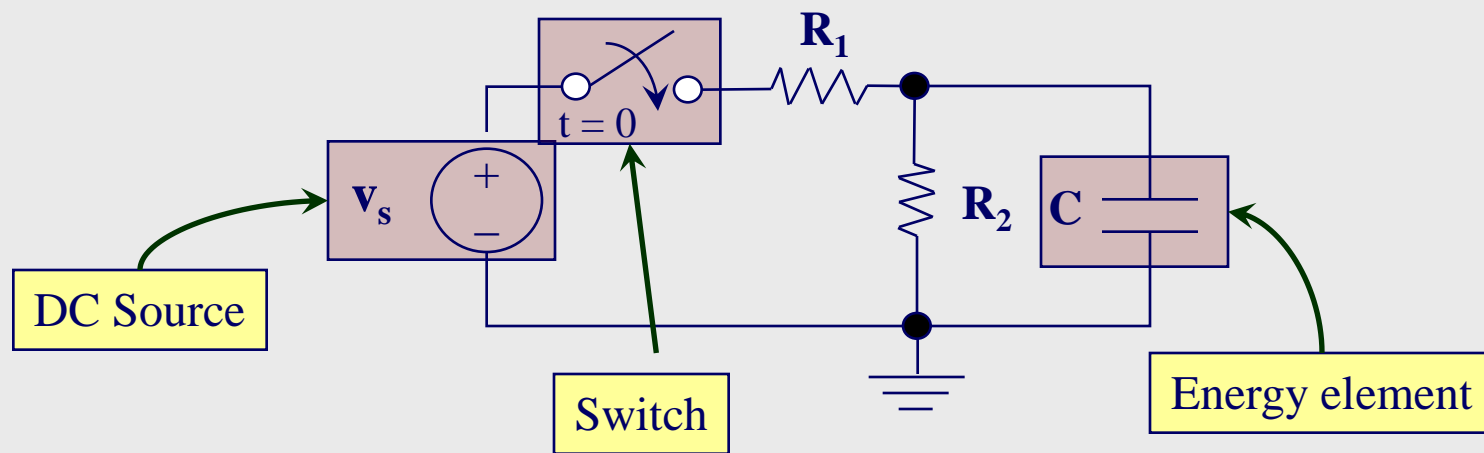1. Steady-state response **prior** to the **switching** on/off of a **DC source**
2. Transient response – the circuit **adjusts** to the **DC source**
3. Steady-state response **following** the transient response



1. DC Steady State

1st and 3rd Step in Transient Response

DC Steady-State

DC steady-state: the **stable** voltages and currents in a circuit connected to a DC source

$$i_C(t) = C \frac{dv_C(t)}{dt} \quad \text{capacitor current}$$

$$i_C(t) \rightarrow 0 \quad \text{as } t \rightarrow \infty \quad \text{steady state current}$$

Capacitors act like **open circuits** at DC steady-state

$$v_L(t) = L \frac{di_L(t)}{dt} \quad \text{inductor voltage}$$

$$v_L(t) \rightarrow 0 \quad \text{as } t \rightarrow \infty \quad \text{steady state voltage}$$

Inductors act like **short circuits** at DC steady-state



DC Steady-State

Initial condition $x(0)$: DC steady state **before** a switch is first activated

▲ $x(0^-)$: right before the switch is closed

▲ $x(0^+)$: right after the switch is closed

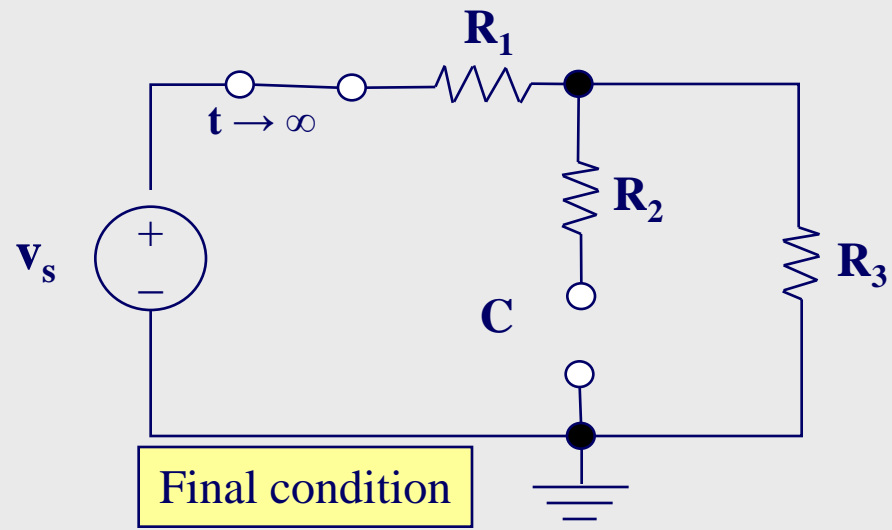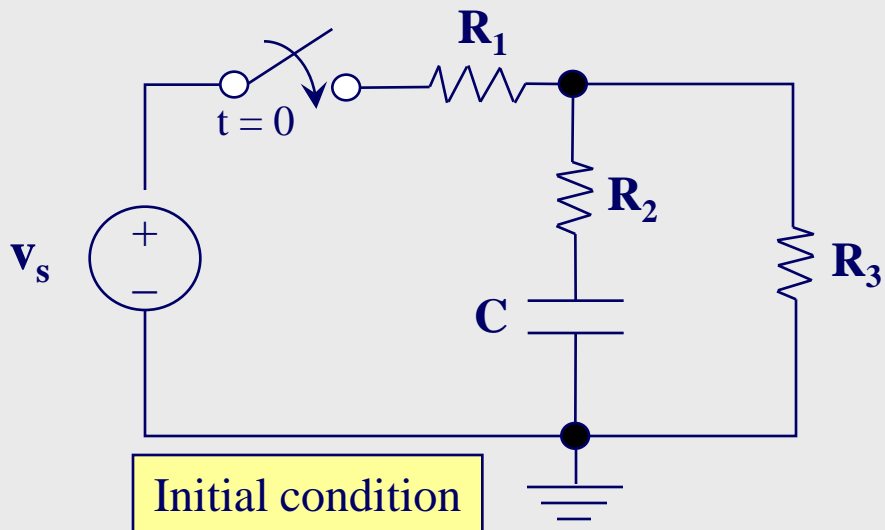
Final condition $x(\infty)$: DC steady state a long time **after** a switch is activated



DC Steady-State

◆ **Example1:** determine the final condition capacitor voltage

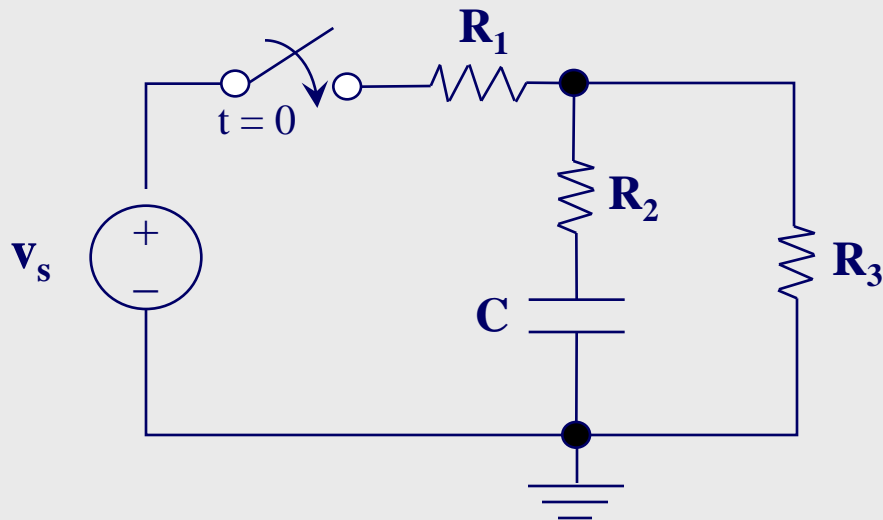
$$v_s = 12\text{V}, R_1 = 100\Omega, R_2 = 75\Omega, R_3 = 250\Omega, C = 1\mu\text{F}$$



DC Steady-State

◆ **Example1:** determine the final condition capacitor voltage
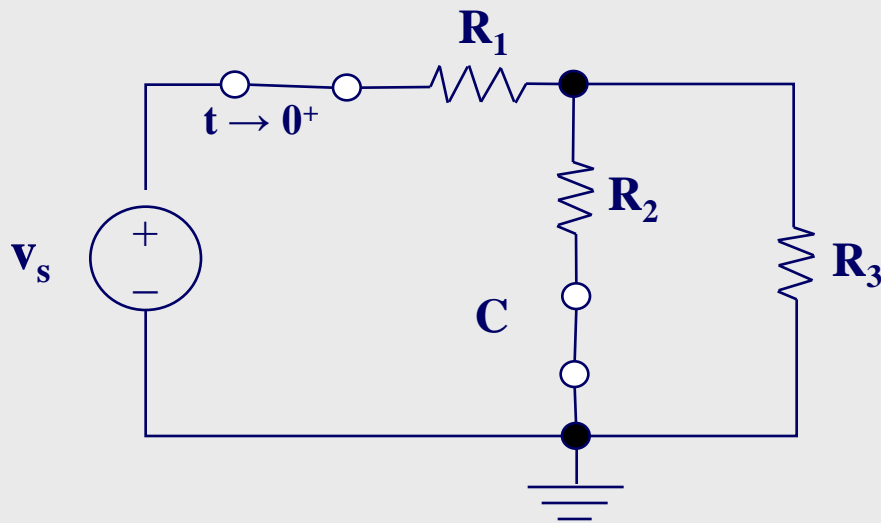
$$v_s = 12V, R_1 = 100\Omega, R_2 = 75\Omega, R_3 = 250\Omega, C = 1\mu F$$



1. Close the switch and find **initial** conditions to the capacitor


NB: Initially ($t = 0^+$) current across the capacitor changes **instantly** but voltage cannot change instantly thus it acts as a **short circuit**

$$v_C(0^+) = v_C(0^-) = 0V$$

DC Steady-State

◆ **Example1:** determine the final condition capacitor voltage
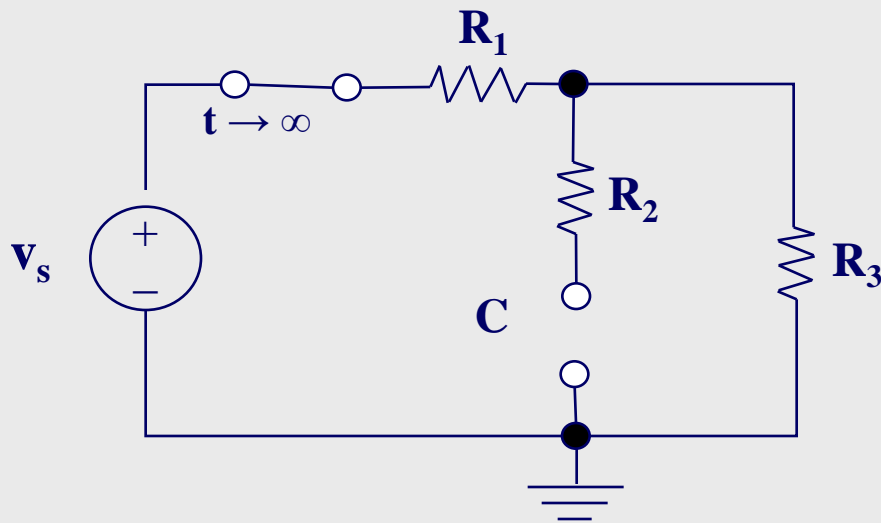
$$v_s = 12V, R_1 = 100\Omega, R_2 = 75\Omega, R_3 = 250\Omega, C = 1\mu F$$



2. Close the switch and apply **final** conditions to the capacitor

NB: since we have an open circuit no current flows through R_2

Voltage divider :

$$\begin{aligned} v_3(\infty) &= \frac{R_3}{R_1 + R_3} v_s \\ &= \frac{250}{350} (12) \\ &= 8.57V \end{aligned}$$

$$\begin{aligned} v_C(\infty) &= v_3(\infty) \\ &= 8.57V \end{aligned}$$

DC Steady-State

Remember – capacitor voltages and inductor currents **cannot change instantaneously**


- ▲ Capacitor voltages and inductor currents don't change right before closing and right after closing a switch

$$v_C(0^+) = v_C(0^-)$$
$$i_L(0^+) = i_L(0^-)$$

DC Steady-State

◆ **Example2**: find the initial and final current conditions at the inductor

$$i_s = 10\text{mA}$$

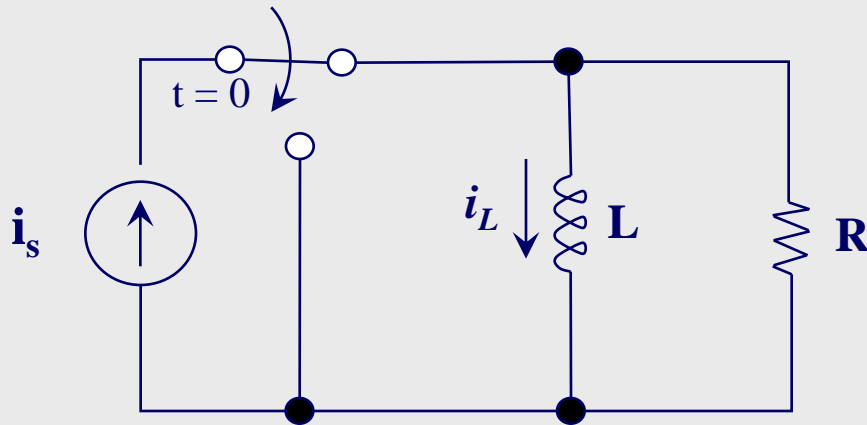


DC Steady-State

◆ **Example2:** find the initial and final current conditions at the inductor

$$i_s = 10\text{mA}$$

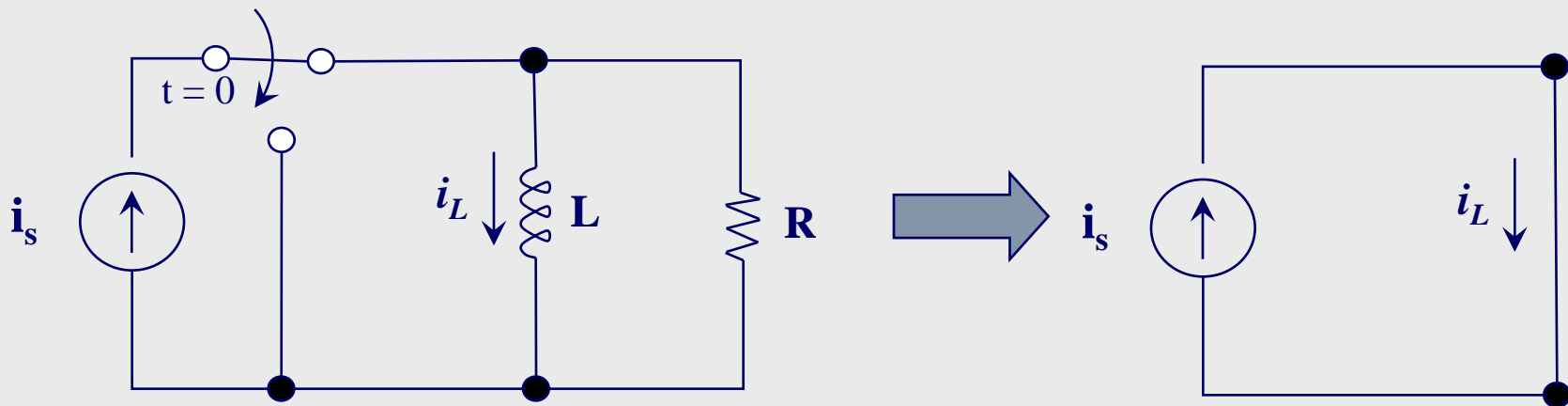1. Initial conditions – assume the current across the inductor is in steady-state.




NB: in DC steady state inductors act like **short circuits**, thus no current flows through **R**

DC Steady-State

◆ **Example2**: find the initial and final current conditions at the inductor

$$i_s = 10\text{mA}$$

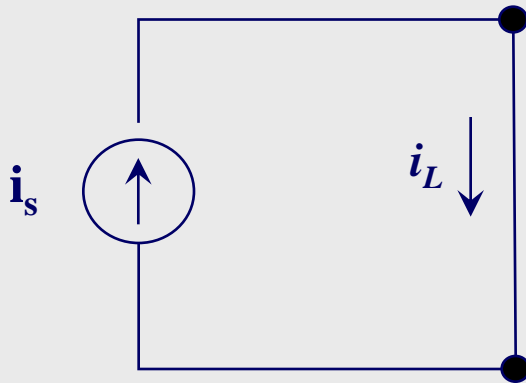1. Initial conditions – assume the current across the inductor is in steady-state.




$$i_L(0^-) = i_s = 10\text{mA}$$

DC Steady-State

◆ **Example2:** find the initial and final current conditions at the inductor

$$i_s = 10\text{mA}$$

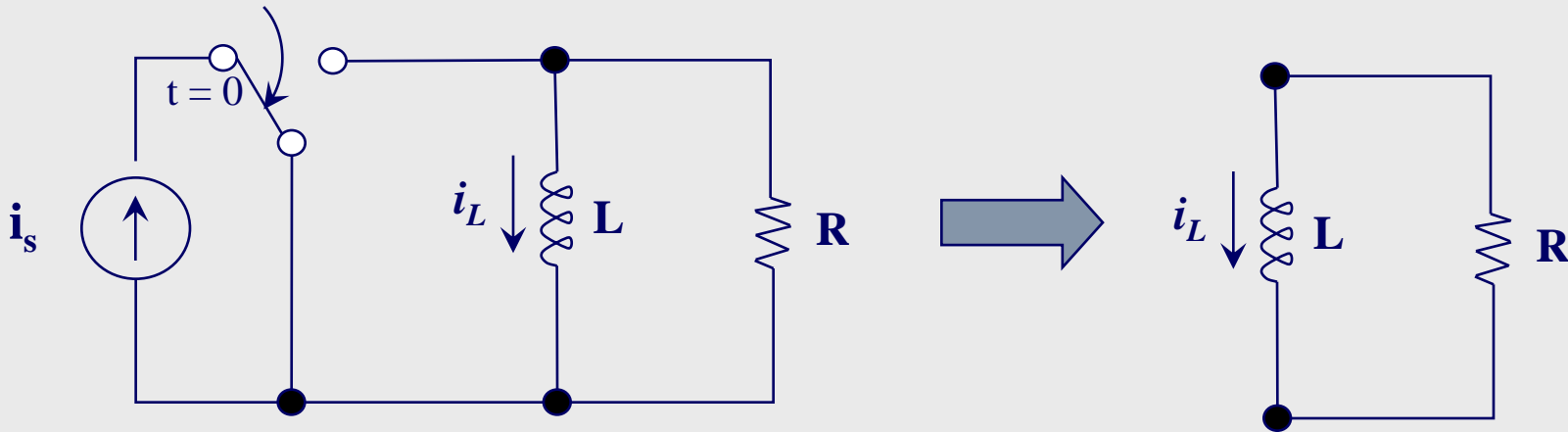1. Initial conditions – assume the current across the inductor is in steady-state.
2. Throw the switch




NB: inductor current cannot change instantaneously

DC Steady-State

◆ **Example2:** find the initial and final current conditions at the inductor

$$i_s = 10\text{mA}$$

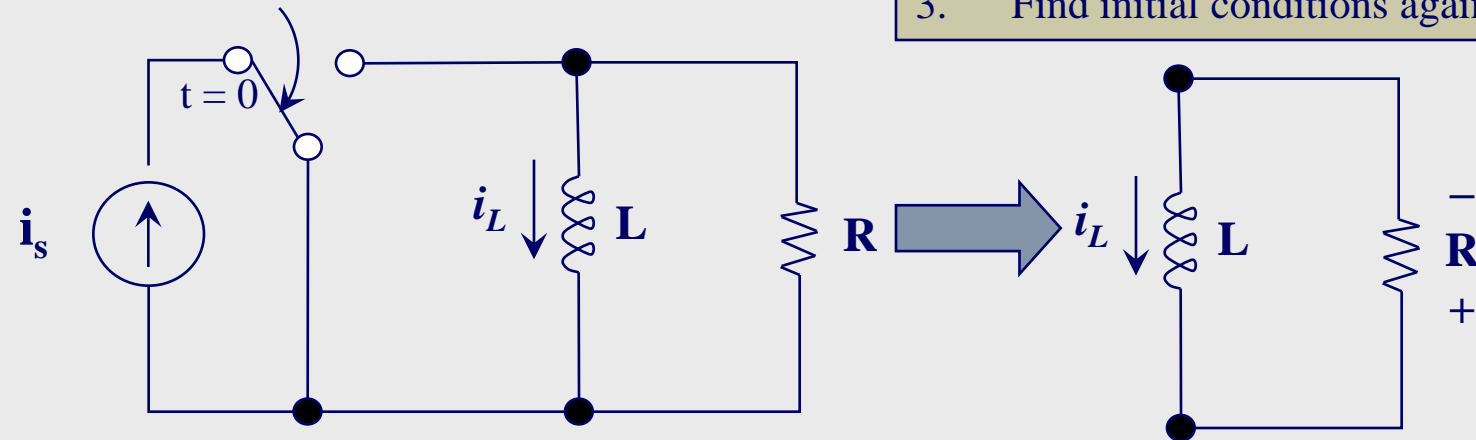1. Initial conditions – assume the current across the inductor is in steady-state.
2. Throw the switch
3. Find initial conditions again (non-steady state)



$$i_L(0^+) = i_L(0^-) = 10\text{mA}$$


NB: polarity of R

NB: inductor current cannot change instantaneously

DC Steady-State

◆ **Example2:** find the initial and final current conditions at the inductor

$$i_s = 10\text{mA}$$

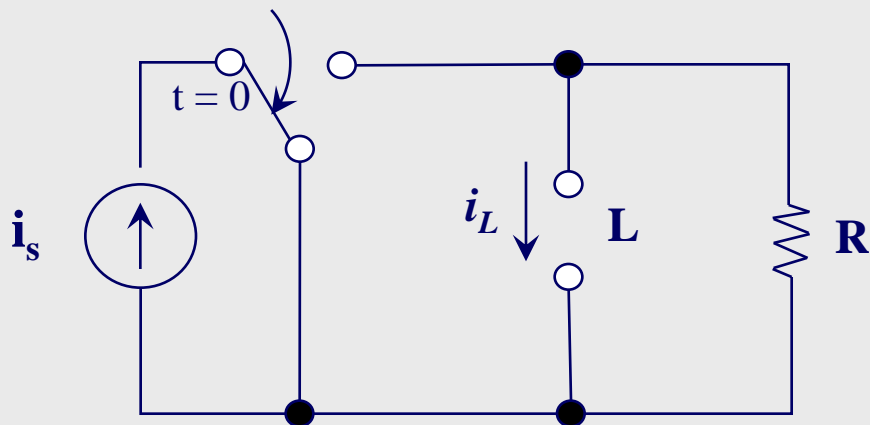

1. Initial conditions – assume the current across the inductor is in steady-state.
2. Throw the switch
3. Find initial conditions again (non-steady state)
4. Final conditions (steady-state)

$$i_L(\infty) = 0\text{A}$$


NB: since there is **no source attached** to the inductor, its current is drained by the resistor **R**

2. Adjusting to Switch

2nd Step in Transient Response

General Solution of 1st Order Circuits

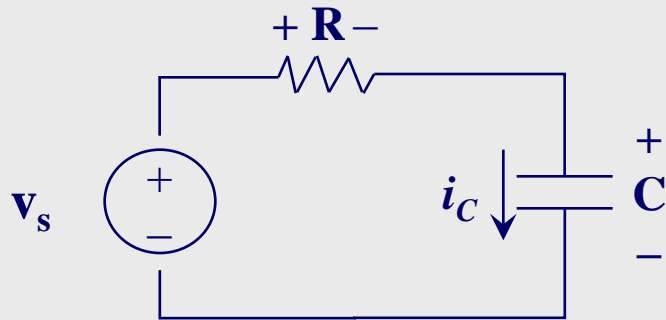- ◆ Expressions for voltage and current of a 1st order circuit will be a 1st order differential equation



NB: Review lecture 11 for derivation of these equations

$$\frac{di_c(t)}{dt} + \frac{1}{RC} i_c(t) = \frac{1}{R} \frac{dv_s(t)}{dt}$$

$$\frac{dv_c(t)}{dt} + \frac{1}{RC} v_c(t) = \frac{1}{RC} v_s(t)$$

General Solution of 1st Order Circuits

- ◆ Expressions for voltage and current of a 1st order circuit will be a 1st order differential equation

$$\frac{di_C(t)}{dt} + \frac{1}{RC} i_C(t) = \frac{1}{R} \frac{dv_s(t)}{dt}$$

$$\frac{dv_C(t)}{dt} + \frac{1}{RC} v_C(t) = \frac{1}{RC} v_s(t)$$

General Solution of 1st Order Circuits

- ◆ Expressions for voltage and current of a 1st order circuit will be a 1st order differential equation

The diagram shows two differential equations for RC circuits. The first equation is $\frac{di_C(t)}{dt} + \frac{1}{RC}i_C(t) = \frac{1}{R} \frac{dv_S(t)}{dt}$ and the second is $\frac{dv_C(t)}{dt} + \frac{1}{RC}v_C(t) = \frac{1}{RC}v_S(t)$. In both equations, the source terms on the right-hand side are circled in red. Green arrows point from these circled terms to a central box labeled "NB: Constants".

$$\frac{di_C(t)}{dt} + \frac{1}{RC}i_C(t) = \frac{1}{R} \frac{dv_S(t)}{dt}$$
$$\frac{dv_C(t)}{dt} + \frac{1}{RC}v_C(t) = \frac{1}{RC}v_S(t)$$

NB: Constants

General Solution of 1st Order Circuits

- ◆ Expressions for voltage and current of a 1st order circuit will be a 1st order differential equation

The diagram illustrates the similarity between the differential equations for an RL circuit and an RC circuit. Two equations are shown side-by-side, each enclosed in a light yellow box with a blue border. The left equation is for an RL circuit: $\frac{di_C(t)}{dt} + \frac{1}{RC}i_C(t) = \frac{1}{R}\frac{dv_s(t)}{dt}$. The right equation is for an RC circuit: $\frac{dv_C(t)}{dt} + \frac{1}{RC}v_C(t) = \frac{1}{RC}v_s(t)$. Both equations have their left-hand sides circled in red. A blue box at the bottom center contains the text "NB: similarities", with two green curved arrows pointing from it to the circled left-hand sides of the two equations.

$$\frac{di_C(t)}{dt} + \frac{1}{RC}i_C(t) = \frac{1}{R}\frac{dv_s(t)}{dt}$$
$$\frac{dv_C(t)}{dt} + \frac{1}{RC}v_C(t) = \frac{1}{RC}v_s(t)$$

NB: similarities

General Solution of 1st Order Circuits

- ◆ Expressions for voltage and current of a 1st order circuit will be a 1st order differential equation

In General :

$$a_1 \frac{dx(t)}{dt} + a_0 x(t) = b_0 y(t)$$

General Solution of 1st Order Circuits

- ◆ Expressions for voltage and current of a 1st order circuit will be a 1st order differential equation

In General :

$$a_1 \frac{dx(t)}{dt} + a_0 x(t) = b_0 y(t)$$

Capacitor/inductor
voltage/current

General Solution of 1st Order Circuits

- ◆ Expressions for voltage and current of a 1st order circuit will be a 1st order differential equation

In General :

$$a_1 \frac{dx(t)}{dt} + a_0 x(t) = b_0 y(t)$$

Forcing function
(F – for DC source)


General Solution of 1st Order Circuits

- ◆ Expressions for voltage and current of a 1st order circuit will be a 1st order differential equation

In General :

$$a_1 \frac{dx(t)}{dt} + a_0 x(t) = b_0 y(t)$$

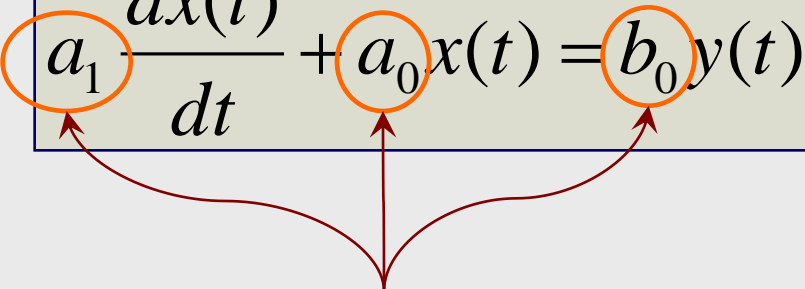Combinations of circuit element parameters
(Constants)



General Solution of 1st Order Circuits

- ◆ Expressions for voltage and current of a 1st order circuit will be a 1st order differential equation

In General :

$$a_1 \frac{dx(t)}{dt} + a_0 x(t) = b_0 y(t)$$

In General re - written :

$$\frac{a_1}{a_0} \frac{dx(t)}{dt} + x(t) = \frac{b_0}{a_0} F$$

Forcing Function **F**

General Solution of 1st Order Circuits

- ◆ Expressions for voltage and current of a 1st order circuit will be a 1st order differential equation

In General re - written :

$$\frac{a_1}{a_0} \frac{dx(t)}{dt} + x(t) = \frac{b_0}{a_0} F$$

In General re - written :

$$\tau \frac{dx(t)}{dt} + x(t) = K_s F$$

DC gain

General Solution of 1st Order Circuits

- ◆ Expressions for voltage and current of a 1st order circuit will be a 1st order differential equation

In General re - written :

$$\frac{a_1}{a_0} \frac{dx(t)}{dt} + x(t) = \frac{b_0}{a_0} F$$

In General re - written :

$$\tau \frac{dx(t)}{dt} + x(t) = K_s F$$

Time constant

DC gain

General Solution of 1st Order Circuits

The solution to this equation (the **complete response**) consists of two parts:

- ▲ **Natural response** (homogeneous solution)
 - Forcing function equal to zero
- ▲ **Forced response** (particular solution)

$$\tau \frac{dx(t)}{dt} + x(t) = K_s F$$

General Solution of 1st Order Circuits


Natural response (homogeneous solution)

▲ Forcing function equal to zero

$$\tau \frac{dx_N(t)}{dt} + x_N(t) = 0$$

$$\frac{dx_N(t)}{dt} = -\frac{x_N(t)}{\tau}$$

Has known solution
of the form:

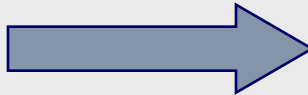


$$x_N(t) = \alpha e^{-t/\tau}$$

General Solution of 1st Order Circuits

Forced response (particular solution)

$$\tau \frac{dx_F(t)}{dt} + x_F(t) = K_S F$$

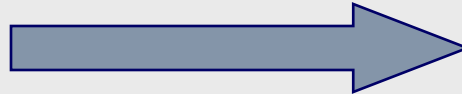F is constant for DC sources,
thus derivative is zero



$$x_F(t) = K_S F$$

NB: This is the **DC steady-state** solution


$$x_F(t) = x(\infty) = K_S F$$

General Solution of 1st Order Circuits

Complete response (natural + forced)

$$\begin{aligned}x(t) &= x_N(t) + x_F(t) \\&= \alpha e^{-t/\tau} + K_S F \\&= \alpha e^{-t/\tau} + x(\infty)\end{aligned}$$

Solve for α by
solving $x(t)$ at $t = 0$

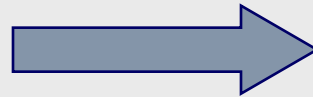

$$\begin{aligned}\text{Solve for } \alpha : \\x(0) &= \alpha + x(\infty) \\ \alpha &= x(0) - x(\infty)\end{aligned}$$

$$x(t) = [x(0) - x(\infty)]e^{-t/\tau} + x(\infty)$$

Initial condition

Final condition

Time constant

General Solution of 1st Order Circuits

Complete response (natural + forced)

$$x(t) = [x(0) - x(\infty)]e^{-t/\tau} + x(\infty)$$

Transient Response

Steady-State Response


3. DC Steady-State + Transient Response

Full Transient Response

Transient Response

Transient response of a circuit consists of 3 parts:

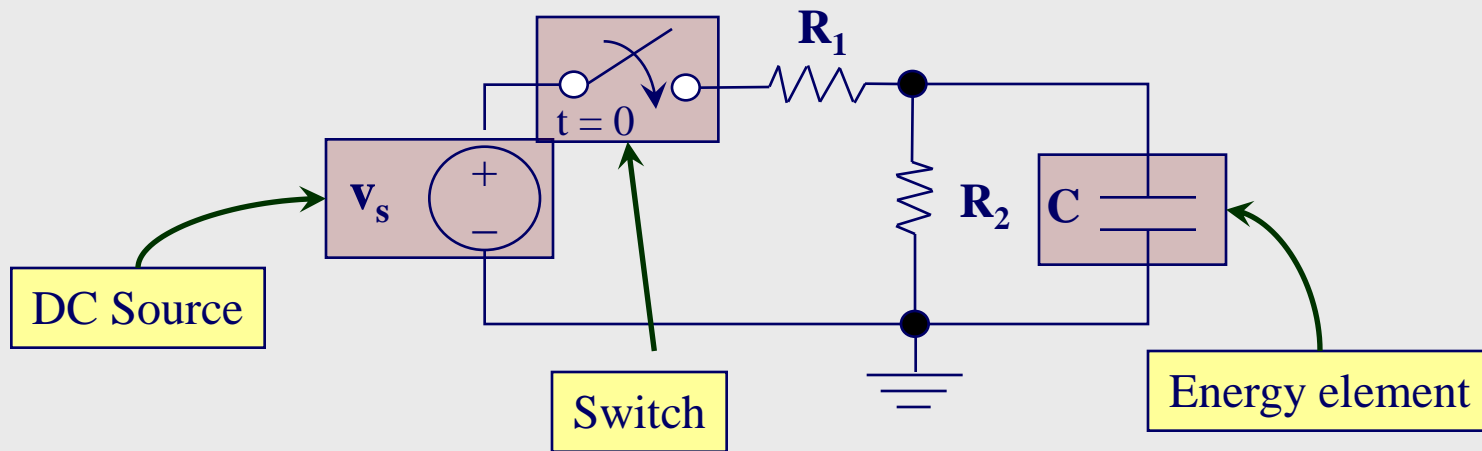1. Steady-state response **prior** to the **switching** on/off of a **DC source**
2. Transient response – the circuit **adjusts** to the **DC source**
3. Steady-state response **following** the transient response



Transient Response


Solving 1st order transient response:

1. Solve the **DC steady-state** circuit:
 - ▲ Initial condition $\mathbf{x}(0^-)$: before switching (on/off)
 - ▲ Final condition $\mathbf{x}(\infty)$: After any transients have died out ($t \rightarrow \infty$)
2. Identify $\mathbf{x}(0^+)$: the circuit **initial conditions**
 - ▲ Capacitors: $\mathbf{v}_C(0^+) = \mathbf{v}_C(0^-)$
 - ▲ Inductors: $\mathbf{i}_L(0^+) = \mathbf{i}_L(0^-)$
3. Write a **differential equation** for the circuit at time $t = 0^+$
 - ▲ Reduce the circuit to its **Thévenin or Norton equivalent**
 - ▲ The energy storage element (capacitor or inductor) is the load
 - ▲ The differential equation will be either in terms of $\mathbf{v}_C(t)$ or $\mathbf{i}_L(t)$
 - ▲ Reduce this equation to standard form
4. Solve for the **time constant**
 - ▲ Capacitive circuits: $\tau = \mathbf{R}_T \mathbf{C}$
 - ▲ Inductive circuits: $\tau = \mathbf{L} / \mathbf{R}_T$
5. Write the **complete response** in the form:
 - ▲ $\mathbf{x}(t) = \mathbf{x}(\infty) + [\mathbf{x}(0) - \mathbf{x}(\infty)]e^{-t/\tau}$

Transient Response

◆ **Example3:** find $v_c(t)$ for all t

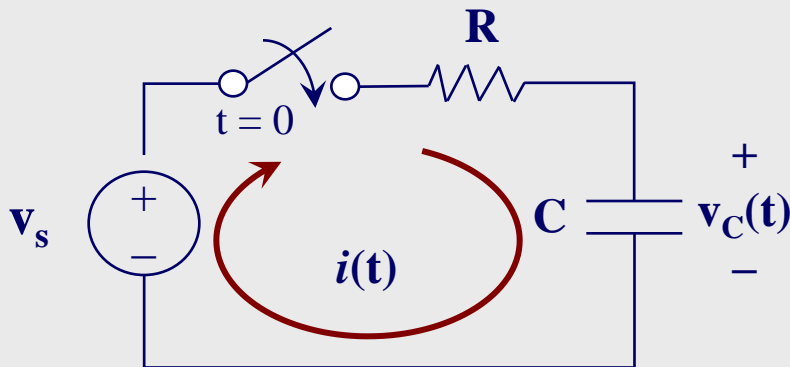
$v_s = 12V$, $v_c(0^-) = 5V$, $R = 1000\Omega$, $C = 470\mu F$



Transient Response

◆ **Example3:** find $v_C(t)$ for all t
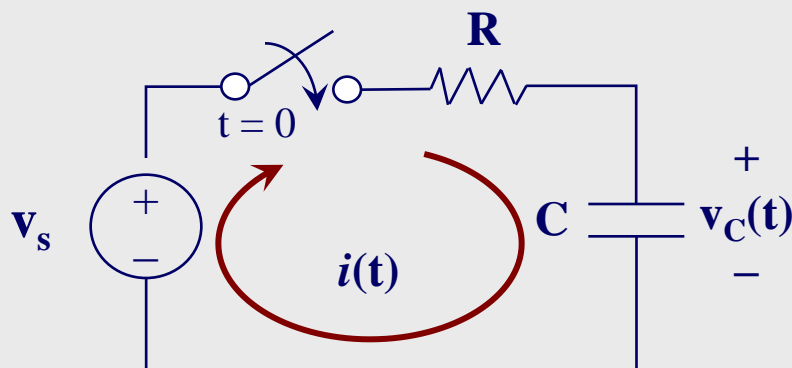
$$v_s = 12V, v_C(0^-) = 5V, R = 1000\Omega, C = 470\mu F$$



NB: as $t \rightarrow \infty$ the capacitor acts like an open circuit thus $v_C(\infty) = v_s$

1. DC steady-state
 - a) Initial condition: $v_C(0)$
 - b) Final condition: $v_C(\infty)$


$$v_C(t < 0) = v_C(0^-) = 5V$$

$$\begin{aligned} v_C(\infty) &= v_s \\ &= 12V \end{aligned}$$

Transient Response

◆ **Example3:** find $v_C(t)$ for all t

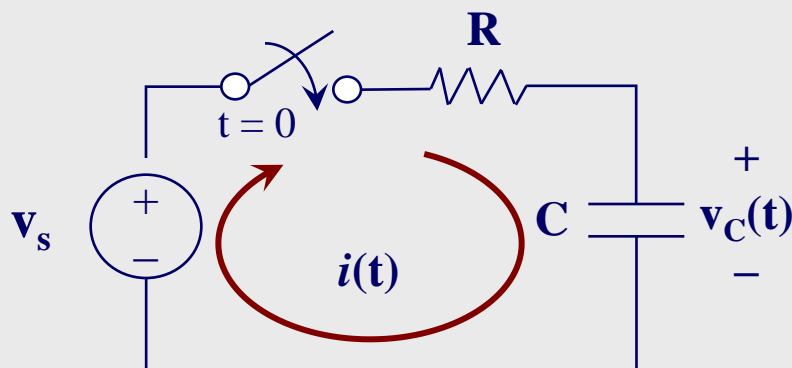$v_s = 12V$, $v_C(0^-) = 5V$, $R = 1000\Omega$, $C = 470\mu F$




2. Circuit initial conditions: $v_C(0^+)$

$$v_C(0^+) = v_C(0^-) = 5V$$

Transient Response

◆ **Example3:** find $v_C(t)$ for all t

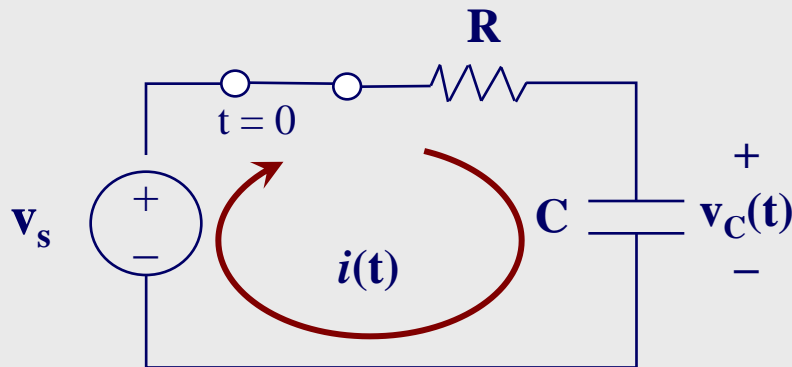$v_s = 12V$, $v_C(0^-) = 5V$, $R = 1000\Omega$, $C = 470\mu F$



3. Write differential equation (already in Thévenin equivalent) at $t = 0$

KVL :

$$-v_S + v_R(t) + v_C(t) = 0$$


$$i_C(t)R + v_C(t) = v_S$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = v_S$$

Transient Response

◆ **Example3:** find $v_C(t)$ for all t
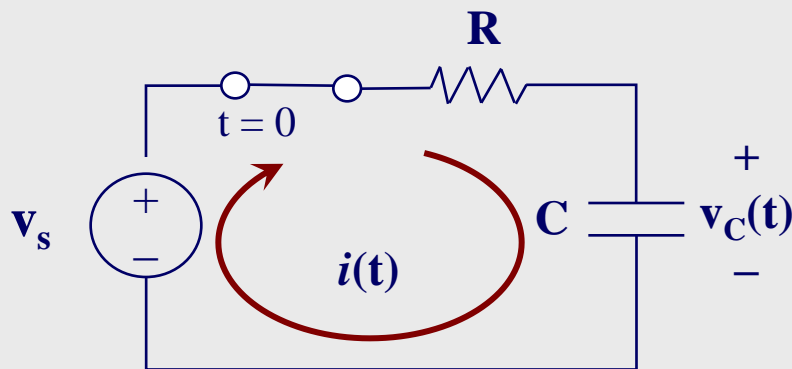
$$v_s = 12V, v_C(0^-) = 5V, R = 1000\Omega, C = 470\mu F$$



NB: solution is of the form:

$$\tau \frac{dx(t)}{dt} + x(t) = K_s F$$

3. Write differential equation (already in Thévenin equivalent) at $t = 0$

KVL :

$$-v_S + v_R(t) + v_C(t) = 0$$


$$i_C(t)R + v_C(t) = v_S$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = v_S$$

Transient Response

◆ **Example3:** find $v_c(t)$ for all t

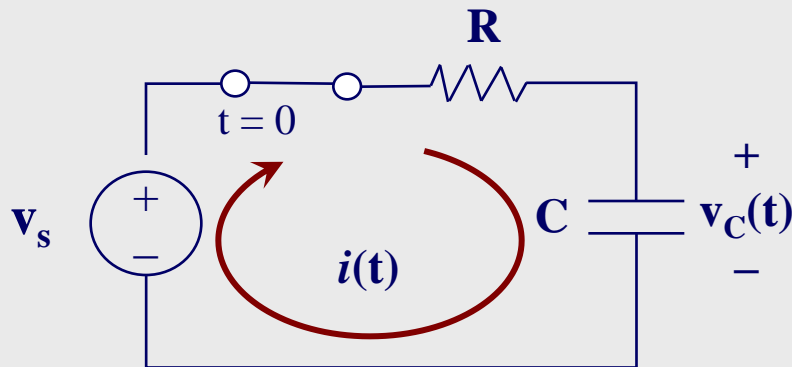$v_s = 12V$, $v_c(0^-) = 5V$, $R = 1000\Omega$, $C = 470\mu F$



4. Find the time constant τ

$$\begin{aligned}\tau &= RC \\ &= (1000)(470 \times 10^{-6}) \\ &= 0.47\end{aligned}$$


$$K_S = 1$$

$$\begin{aligned}F &= v_s \\ &= 12\end{aligned}$$

Transient Response

◆ **Example3:** find $v_C(t)$ for all t

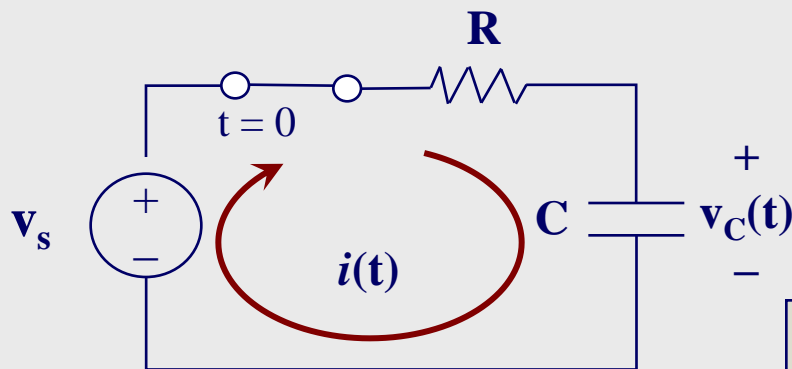$v_s = 12V$, $v_C(0^-) = 5V$, $R = 1000\Omega$, $C = 470\mu F$




5. Write the complete response
 $x(t) = x(\infty) + [x(0) - x(\infty)]e^{-t/\tau}$

$$\begin{aligned} v_C(t) &= v_C(\infty) + [v_C(0) - v_C(\infty)]e^{-t/\tau} \\ &= 12 + (5 - 12)e^{-t/0.47} \\ &= 12 - 7e^{-t/0.47} \end{aligned}$$

Transient Response

◆ **Example4:** find $v_c(t)$ for all t

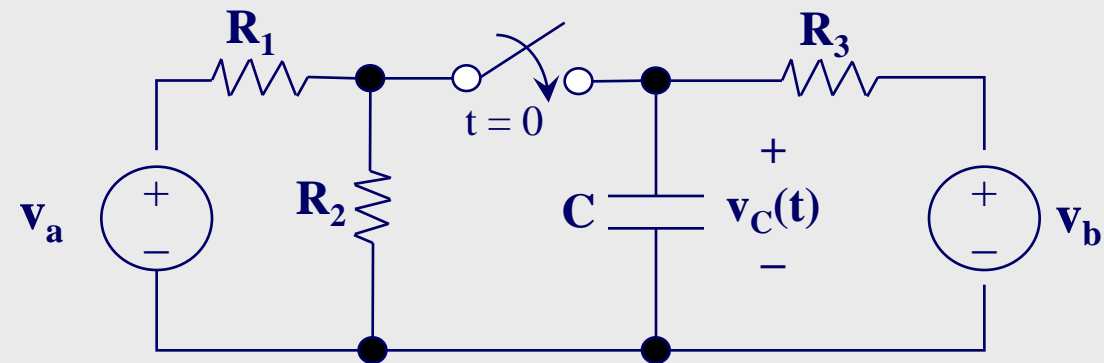
$v_a = 12V$, $v_b = 5V$, $R_1 = 10\Omega$, $R_2 = 5\Omega$, $R_3 = 10\Omega$, $C = 1\mu F$



Transient Response

◆ **Example4:** find $v_C(t)$ for all t
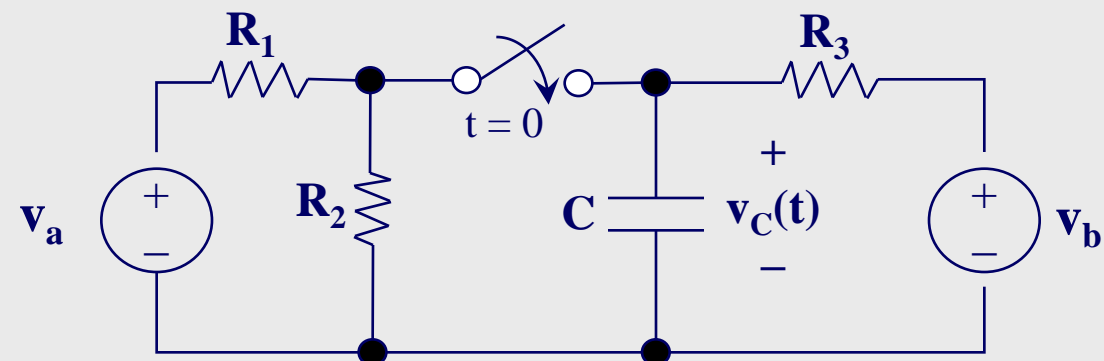
$$v_a = 12V, v_b = 5V, R_1 = 10\Omega, R_2 = 5\Omega, R_3 = 10\Omega, C = 1\mu F$$



1. DC steady-state
 - a) Initial condition: $v_C(0)$
 - b) Final condition: $v_C(\infty)$

For $t < 0$ the capacitor has been charged by v_b thus $v_C(0^-) = v_b$

$$v_C(0^-) = v_b = 5V$$


For $t \rightarrow \infty$ $v_C(\infty)$ is not so easily determined – it will be equal to v_T (the open circuited Thévenin equivalent)

$$v_C(\infty) = v_T$$

Transient Response

◆ **Example4:** find $v_C(t)$ for all t

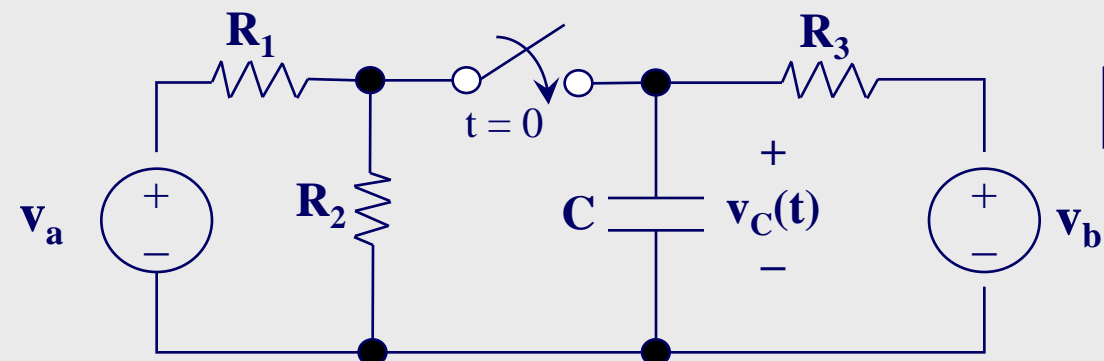$v_a = 12V$, $v_b = 5V$, $R_1 = 10\Omega$, $R_2 = 5\Omega$, $R_3 = 10\Omega$, $C = 1\mu F$



2. Circuit initial conditions: $v_C(0^+)$


$$v_C(0^+) = v_C(0^-) = 5V$$

Transient Response

◆ **Example4:** find $v_c(t)$ for all t

$v_a = 12V$, $v_b = 5V$, $R_1 = 10\Omega$, $R_2 = 5\Omega$, $R_3 = 10\Omega$, $C = 1\mu F$

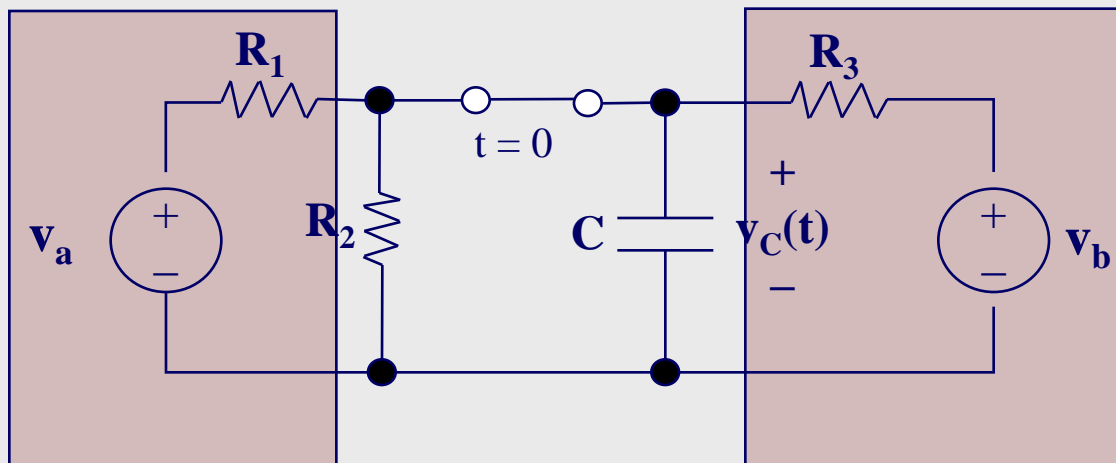3. Write differential equation at $t = 0$
a) Find Thévenin equivalent



$$\begin{aligned} i_a &= \frac{v_a}{R_1} \\ &= \frac{12}{10} \\ &= 1.2 \text{ A} \end{aligned}$$


$$\begin{aligned} i_b &= \frac{v_b}{R_3} \\ &= \frac{5}{10} \\ &= 0.5 \text{ A} \end{aligned}$$

Transient Response

◆ **Example4:** find $v_c(t)$ for all t

$v_a = 12V$, $v_b = 5V$, $R_1 = 10\Omega$, $R_2 = 5\Omega$, $R_3 = 10\Omega$, $C = 1\mu F$

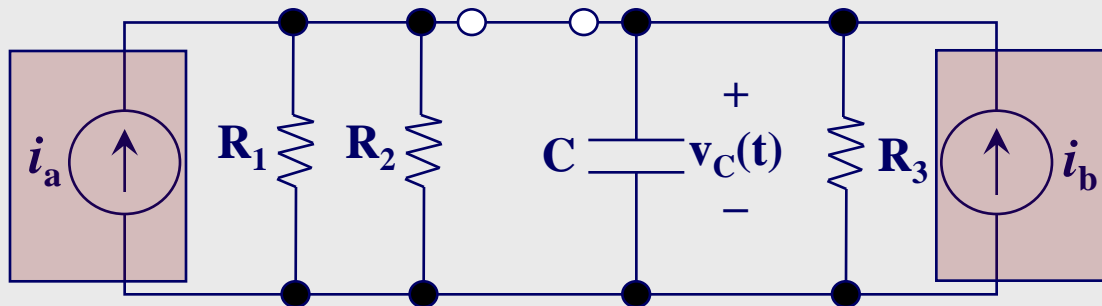3. Write differential equation at $t = 0$
 - a) Find Thévenin equivalent




$$\begin{aligned} i_T &= i_1 + i_2 \\ &= 1.2 + 0.5 \\ &= 1.7 \text{ A} \end{aligned}$$

Transient Response

◆ **Example4:** find $v_c(t)$ for all t

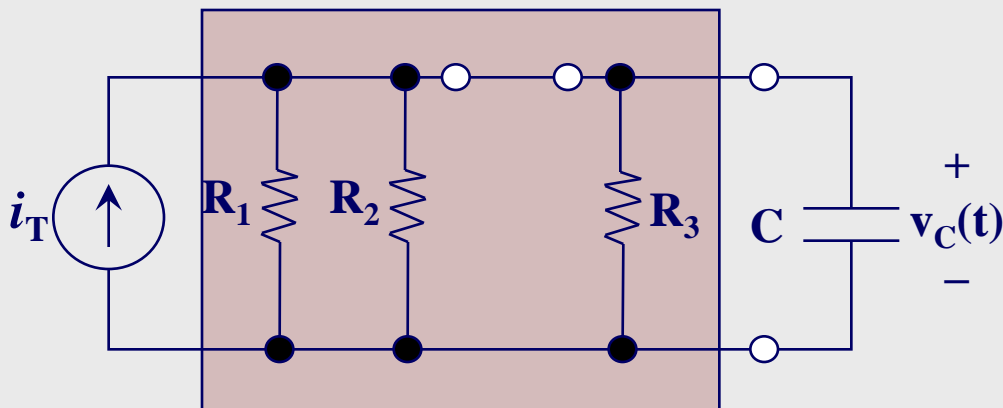$v_a = 12V$, $v_b = 5V$, $R_1 = 10\Omega$, $R_2 = 5\Omega$, $R_3 = 10\Omega$, $C = 1\mu F$



3. Write differential equation at $t = 0$
 - a) Find Thévenin equivalent


$$\begin{aligned} R_T &= R_1 \parallel R_2 \parallel R_3 \\ &= \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \\ &= \frac{(10)(5)(10)}{(10)(5) + (10)(10) + (5)(10)} \\ &= \frac{500}{200} \\ &= 2.5\Omega \end{aligned}$$

$$i_T = 1.7 A$$

Transient Response

◆ **Example4:** find $v_c(t)$ for all t

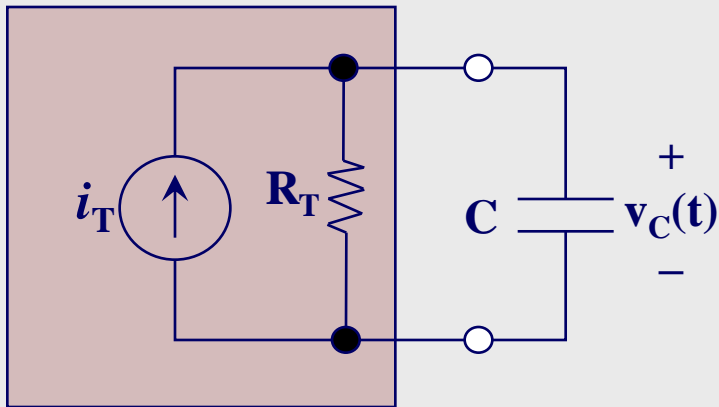$v_a = 12V$, $v_b = 5V$, $R_1 = 10\Omega$, $R_2 = 5\Omega$, $R_3 = 10\Omega$, $C = 1\mu F$



3. Write differential equation at $t = 0$
 - a) Find Thévenin equivalent


$$\begin{aligned}v_T &= i_T R_T \\&= (1.7)(2.5) \\&= 4.25 V\end{aligned}$$

$$\begin{aligned}i_T &= 1.7 A \\R_T &= 2.5\Omega\end{aligned}$$

Transient Response

◆ **Example4:** find $v_c(t)$ for all t

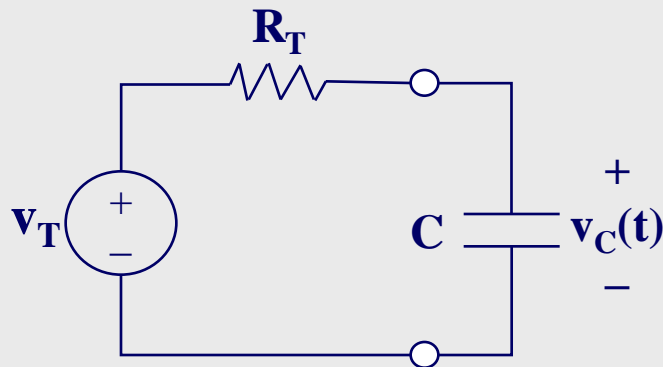$v_a = 12V$, $v_b = 5V$, $R_1 = 10\Omega$, $R_2 = 5\Omega$, $R_3 = 10\Omega$, $C = 1\mu F$



$$v_T = 4.25 V$$
$$R_T = 2.5\Omega$$

3. Write differential equation at $t = 0$
 - a) Find Thévenin equivalent
 - b) Reduce equation to standard form

KVL:

$$-v_T + v_{RT}(t) + v_C(t) = 0$$


$$i_C(t)R_T + v_C(t) = v_T$$

$$CR_T \frac{dv_C(t)}{dt} + v_C(t) = v_T$$

Transient Response

◆ **Example4:** find $v_c(t)$ for all t

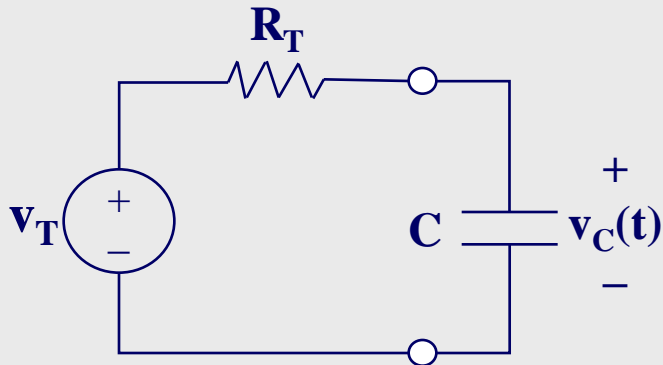$v_a = 12V$, $v_b = 5V$, $R_1 = 10\Omega$, $R_2 = 5\Omega$, $R_3 = 10\Omega$, $C = 1\mu F$



4. Find the time constant τ

$$\begin{aligned}\tau &= R_T C \\ &= (2.5)(10^{-6}) \\ &= 2.5 \times 10^{-6}\end{aligned}$$

$$\begin{aligned}v_T &= 4.25 V \\ R_T &= 2.5\Omega\end{aligned}$$


$$K_S = 1$$

$$\begin{aligned}F &= v_T \\ &= 4.25\end{aligned}$$

Transient Response

◆ **Example4:** find $v_c(t)$ for all t
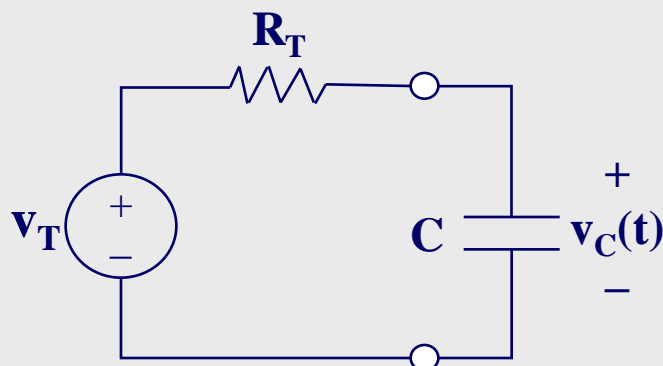
$$v_a = 12V, v_b = 5V, R_1 = 10\Omega, R_2 = 5\Omega, R_3 = 10\Omega, C = 1\mu F$$



5. Write the complete response
 $x(t) = x(\infty) + [x(0) - x(\infty)]e^{-t/\tau}$

$$v_T = 1.75 V$$
$$R_T = 2.5\Omega$$


$$\begin{aligned} v_C(t) &= v_C(\infty) + [v_C(0) - v_C(\infty)]e^{-t/\tau} \\ &= 4.25 + (5 - 4.25)e^{-t/2.5 \times 10^{-6}} \\ &= 4.25 + 0.75e^{-t/2.5 \times 10^{-6}} \end{aligned}$$

Transient Response

◆ **Example4:** find $v_c(t)$ for all t

$$v_a = 12V, v_b = 5V, R_1 = 10\Omega, R_2 = 5\Omega, R_3 = 10\Omega, C = 1\mu F$$

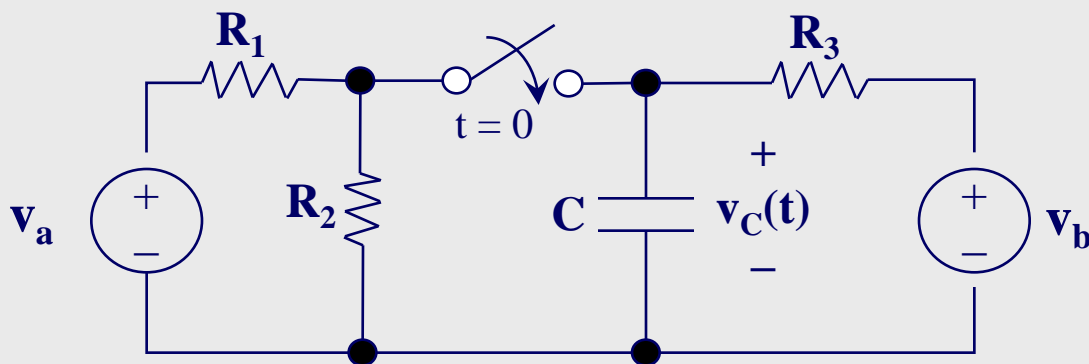5. Write the complete response
 $x(t) = x(\infty) + [x(0) - x(\infty)]e^{-t/\tau}$



$$v_c(t) = 4.25 + 0.75e^{-t/2.5 \times 10^{-6}}$$