Schedule...

Date	Day	Class No.	Title	Chapters	HW Due date	Lab Due date	Exam
29 Oct	Wed	17	Operational Amplifiers	8.1 - 8.2			
30 Oct	Thu						
31 Oct	Fri		Recitation		HW 7		
1 Nov	Sat						
2 Nov	Sun						
3 Nov	Mon	18	Operational Amplifiers	8.3 - 8.4		LAB 6	
4 Nov	Tue						
5 Nov	Wed	19	Binary Numbers	13.1 – 13.2			1



Increase

Helaman 12:2

2 Yea, and we may see at the very time when he doth prosper his people, yea, in the **increase** of their fields, their flocks and their herds, and in gold, and in silver, and in all manner of precious things of every kind and art; sparing their lives, and delivering them out of the hands of their enemies; softening the hearts of their enemies that they should not declare wars against them; yea, and in fine, doing all things for the welfare and happiness of his people; yea, then is the time that they do harden their hearts, and do forget the Lord their God, and do trample under their feet the Holy One—yea, and this because of their ease, and their exceedingly great prosperity.



Lecture 17 – Operational Amplifiers



ECEN 301

Discussion #17 – Operational Amplifiers

3

<u>Amplifier</u>: a device for **increasing** the power of a signal. ▲ Power increase is called **gain** (A)





Simplified Amplifier Model:

A The source "sees" and equivalent load (R_{in}) A The load "sees" and equivalent source (Av_{in})





Discussion #17 – Operational Amplifiers

5

The **gain** is **dependent on the source and load** (i.e. is different for different sources and loads)



$$v_L = \left(A \frac{R_{in}}{R_S + R_{in}} \frac{R_L}{R_{out} + R_L} \right) v_S$$

NB: expression for v_L depends on the source (R_S) and the load (R_L)



ECEN 301

The gain can be made to be **almost** independent of the source (\mathbf{R}_{s}) and the load $(\mathbf{R}_{\mathbf{I}})$ $\land \text{Let } \mathbf{R}_{in} \to \infty$ \land Let $\mathbf{R}_{out} \rightarrow 0$ Rout **R**_S if $R_{out} \rightarrow 0$ Av_{in} R_L< $v_{s}(t)$ **R**_{in} V_{in} $\approx Av_{in}$ $v_{\rm I} \approx A v_{\rm s}$

- **NB**: it is desirable for an amplifier to have:
 - a very large input impedance
 - a very small output impedance





Op-Amps

Operational Amplifier: originally designed (late 1960's) to perform mathematical operations (analog computer) ▲ Addition

- ▲ Subtraction
- ▲ Integration
- ▲ differentiation





Op-Amps – Open-Loop Mode

Open-Loop Model: an ideal op-amp acts like a **difference amplifier** (a device that amplifies the difference between two input voltages)



Discussion #17 – Operational Amplifiers

9

Op-Amps – Open-Loop Mode

Open-Loop Model: an ideal op-amp acts like a **difference amplifier** (a device that amplifies the difference between two input voltages)



Ideally $i_1 = i_2 = 0$ (since $\mathbf{R}_{in} \rightarrow \infty$)



ECEN 301

Op-Amps – Open-Loop Mode

Open-Loop Model: an ideal op-amp acts like a **difference amplifier** (a device that amplifies the difference between two input voltages)



Discussion #17 – Operational Amplifiers



11

The Inverting Amplifier: the signal to be amplified is connected to the inverting terminal





ECEN 301

<u>**The Inverting Amplifier</u>**: the signal to be amplified is connected to the inverting terminal</u>



Feedback current: current from the output is fed back into the input of the op-amp







KCL at Node a :

$$i_S + i_F - i_1 = 0$$

 $i_S = -i_F$



ECEN 301

The Inverting Amplifier: the signal to be amplified is connected to the inverting terminal



From Open - Loop Model :

$$v_o = A_{OL}(v^+ - v^-)$$

 $= A_{OL}(0 - v^-)$
 $= -A_{OL}v^-$
 $v^- = -\frac{v_o}{A_{OL}}$



ECEN 301

The Inverting Amplifier: the signal to be amplified is connected to the inverting terminal





15

ECEN 301

The Inverting Amplifier: the signal to be amplified is connected to the inverting terminal







ECEN 301

The Inverting Amplifier: the signal to be amplified is connected to the inverting terminal



From Open - Loop Model :

$$v^{-} = -\frac{v_{out}}{A_{OL}}$$

NB: as
$$A_{OL} \rightarrow \infty v^- \rightarrow 0$$

As
$$A_{OL} \to \infty$$

 $v^- \approx v^+$



ECEN 301

<u>**The Inverting Amplifier</u>**: the signal to be amplified is connected to the inverting terminal</u>



NB: two important results for an ideal op-amp with negative feedback

$$i_1 = i_2 = 0$$
$$v^- = v^+$$



Example1: determine \mathbf{A}_{OL} and \mathbf{v}_{o} $\mathbf{R}_{S} = 1k\Omega$, $\mathbf{R}_{F} = 10k\Omega$, $\mathbf{v}_{s}(\mathbf{t}) = A\cos(\omega t)$, A=0.015, $\omega = 50$ rads/s





ECEN 301

Example1: determine \mathbf{A}_{OL} and \mathbf{v}_{o} $\mathbf{R}_{S} = 1k\Omega$, $\mathbf{R}_{F} = 10k\Omega$, $\mathbf{v}_{s}(t) = A\cos(\omega t)$, A=0.015, $\omega = 50$ rads/s





20

ECEN 301

Example1: determine \mathbf{A}_{OL} and \mathbf{v}_{o} $\mathbf{R}_{S} = 1k\Omega$, $\mathbf{R}_{F} = 10k\Omega$, $\mathbf{v}_{s}(t) = A\cos(\omega t)$, A=0.015, $\omega = 50$ rads/s





ECEN 301

Example2: What is the min/max gain, and gain uncertainty if 5% tolerance resistors are used?

 $\mathbf{R}_{\mathbf{S}} = 1$ k Ω , $\mathbf{R}_{\mathbf{F}} = 10$ k Ω , $\mathbf{v}_{\mathbf{s}}(\mathbf{t}) = A\cos(\omega t)$, A=0.015, $\omega = 50$ rads/s





22

ECEN 301

Example2: What is the min/max gain, and gain uncertainty if 5% tolerance resistors are used? $\mathbf{R}_{\mathbf{s}} = 1 \mathrm{k} \Omega, \, \mathbf{R}_{\mathbf{F}} = 10 \mathrm{k} \Omega, \, \mathbf{v}_{\mathbf{s}}(\mathbf{t}) = \mathrm{A} \mathrm{cos}(\omega t),$ Max % Error : A=0.015, $\omega = 50$ rads/s $100 \times \frac{A_{CL nom} - A_{CL min}}{A_{CL nom}}$ $=100 \times \frac{10 - 9.05}{10}$ **R**_S =9.5% $i_{\rm S}$ Min % Error: +**V**⁺ $v_{s}(t)$ $100 \times \frac{A_{CL nom} - A_{CL max}}{A}$ V_o $=100 \times \frac{10 - 11.05}{10}$ = -10.5%



23

ECEN 301

The Summing Amplifier: sources are summed together independently of load and source impedances



ECEN 301



<u>The Summing Amplifier</u>: sources are summed together independently of load and source impedances



Discussion #17 – Operational Amplifiers

25

Electrical Engineering Computer Engineering

<u>The Summing Amplifier</u>: sources are summed together independently of load and source impedances







26

ECEN 301

The Noninverting Amplifier: the signal to be amplified is connected to the noninverting terminal





27

ECEN 301

<u>The Noninverting Amplifier</u>: the signal to be amplified is connected to the noninverting terminal





$$i_1 = 0$$

KCL at Node a :

$$-i_S + i_F - i_1 = 0$$

 $i_S = i_F$



28

ECEN 301

<u>The Noninverting Amplifier</u>: the signal to be amplified is connected to the noninverting terminal



Since $i_1 = 0$: (i.e. no current through R : no voltage drop) $v^+ = v_s = v^$ $i_1 = i_1$

$$l_F = l_S$$

$$\frac{v_o - v_S}{R_F} = \frac{v_S}{R_S}$$

$$\frac{v_o}{v_S} = 1 + \frac{R_F}{R_S}$$



ECEN 301

<u>The Noninverting Amplifier</u>: the signal to be amplified is connected to the noninverting terminal





30

ECEN 301

Voltage Follower: the voltage on the output of the op-amp is equal to the source voltage





ECEN 301

Voltage Follower: the voltage on the output of the op-amp is equal to the source voltage



NB: an ideal op-amp with negative feedback has the property









ECEN 301

Voltage Follower: the voltage on the output of the op-amp is equal to the source voltage



Loading: changing the behaviour of one circuit by connecting another circuit to it

33

Voltage Follower: the voltage on the output of the op-amp is equal to the source voltage



Voltage follower can be used to prevent **loading** $(i_b = 0)$

Loading: changing the behaviour of one circuit by connecting another circuit to it



34

ECEN 301