Schedule...

Date	Day	Class No.	Title	Chapters	HW Due date	Lab Due date	Exam
10 Nov	Mon	20	Exam Review			LAB 7	
11 Nov	Tue						
12 Nov	Wed	21	Boolean Algebra	13.2 – 13.3			EXAM 2
13 Nov	Thu						
14 Nov	Fri		Recitation				
15 Nov	Sat						
16 Nov	Sun						
17 Nov	Mon	22	Combinational Logic	13.3 – 13.5		LAR 10	
18 Nov	Tue						(



Ask

<u>Alma 5:26</u>

26 And now behold, I say unto you, my brethren, if ye have experienced a change of heart, and if ye have felt to sing the song of redeeming love, **I would ask**, can ye feel so now?



Lecture 20 – Exam 2 Review

Chapters 4 - 6, 8





Exam 2

- ♦ 12 16 November (Monday Friday)
- ♦ Chapters 4 6 and 8
- 15 questions
 - ▲ 12 multiple choice (answer on bubble sheet!)
 - 1 point each
 - ▲ 3 long answer (show your work!)
 - 4 or 5 points each
- Closed book!
 - ▲ One 3x5 card allowed
- Calculators allowed
- No time limit
- Study lecture slides and homework



Exam 2 Review...Overview

- 1. Capacitors and Inductors
- 2. Measuring Signal Strength
- 3. Phasors
- 4. Impedance
- 5. AC RLC Circuits
- 6. AC Equivalent Circuits
- 7. DC Transient Response
- 8. Frequency Response
- 9. Basic Filters
- 10. Op-Amps



	Inductors	Capacitors
Passive sign convention	$ \begin{array}{c} + L - \\ \circ \\ i \end{array} \circ \\ i \end{array} $	$\begin{array}{c c} & + \mathbf{C} - \\ & & & \\ & & & \\ & & & \\ & i \longrightarrow \end{array}$
Voltage	$v(t) = L \frac{di(t)}{dt}$	$v(t) = \frac{1}{C} \int_{0}^{t} i_{C}(\tau) d\tau + v(t_{0})$
Current	$i(t) = \frac{1}{L} \int_0^t v_L(\tau) d\tau + i(t_0)$	$i(t) = C \frac{dv(t)}{dt}$
Power	$P_L(t) = Li(t)\frac{di(t)}{dt}$	$P_{C}(t) = Cv(t)\frac{dv(t)}{dt}$



	Inductors	Capacitors
Energy	$W_L(t) = \frac{1}{2} Li(t)^2$	$W_C(t) = \frac{1}{2}Cv(t)^2$
An instantaneous change is not permitted in:	Current	Voltage
Will permit an instantaneous change in:	Voltage	Current
With DC source element acts as a:	Short Circuit	Open Circuit



1. What is the difference between the voltage and current behaviour of capacitors and inductors?



1. What is the difference between the voltage and current behaviour of capacitors and inductors?



Discussion #20 – Exam 2 Review

Electrical Engineering Computer Engineering

2. find the voltage v(t) for a capacitor C = 0.5F with the current as shown and v(0) = 0





2. find the voltage v(t) for a capacitor C = 0.5F with the current as shown and v(0) = 0



current	i(t) in 4 intervals	
i = 0	$t \leq 0$	
=t	$0 < t \leq 1$	
=1	$1 < t \leq 2$	
= 0	2 < <i>t</i>	

$$v(t) = \frac{1}{C} \int_0^t i d\tau + v(0)$$



2. find the voltage v(t) for a capacitor C = 0.5F with the current as shown and v(0) = 0



voltage v(t) in 4 intervals :

$$v = 0 t \le 0$$

$$= 2 \int_{0}^{t} \tau d\tau + 0 0 < t \le 1$$

$$= 2 \int_{0}^{t} (1) d\tau + v(1) 1 < t \le 2$$

$$= 0 + v(2) 2 < t$$

$$v(t) = \frac{1}{C} \int_0^t i d\tau + v(0)$$



2. find the voltage v(t) for a capacitor C = 0.5F with the current as shown and v(0) = 0



voltage	v(t) in 4 intervals	0
v = 0	$t \leq 0$	
$=t^2$	$0 < t \leq 1$	
= 2t -	$1 \qquad 1 < t \le 2$	
= 3	2 < t	



2. find the voltage v(t) for a capacitor C = 0.5F with the current as shown and v(0) = 0



Discussion #20 – Exam 2 Review

Electrical Engineering Computer Engineering

Measuring Signal Strength

Compute the rms value of the sinusoidal current
 i(t) = I cos(ωt)



Measuring Signal Strength

3. Compute the rms value of the sinusoidal current $i(t) = I \cos(\omega t)$





Measuring Signal Strength

3. Compute the rms value of the sinusoidal current $i(t) = I \cos(\omega t)$

The RMS value of any sinusoid signal is always equal to 0.707 times the peak value (regardless of phase or frequency)

$$i_{rms} = \sqrt{\frac{1}{T}} \int_{0}^{T} i^{2}(\tau) d\tau$$

$$= \sqrt{\frac{\omega}{2\pi}} \int_{0}^{2\pi/\omega} I^{2} \cos^{2}(2\omega\tau) d\tau$$

$$= \sqrt{\frac{\omega}{2\pi}} \int_{0}^{2\pi/\omega} I^{2} \left[\frac{1}{2} + \frac{1}{2}\cos(2\omega\tau)\right] d\tau$$

$$= \sqrt{\frac{1}{2}} I^{2} + \frac{\omega}{2\pi} \int_{0}^{2\pi/\omega} \frac{I^{2}}{2}\cos(2\omega\tau) d\tau$$

$$= \sqrt{\frac{1}{2}} I^{2} + 0$$

$$= \frac{I}{\sqrt{2}}$$



17

4. compute the phasor voltage for the equivalent voltage $v_s(t)$ $v_1(t) = 15\cos(377t + \pi/4)$ $v_2(t) = 15\cos(377t + \pi/12)$



BYU Electrical Engineering Computer Engineering

18

4. compute the phasor voltage for the equivalent voltage $v_s(t)$ $v_1(t) = 15\cos(377t + \pi/4)$ $v_2(t) = 15\cos(377t + \pi/12)$



1. Write voltages in phasor notation

$$V_{1}(j\omega) = 15e^{j\pi/4}$$
$$= 15 \angle \frac{\pi}{4} V$$
$$V_{2}(j\omega) = 15e^{j\pi/12}$$
$$= 15 \angle \frac{\pi}{12} V$$



ECEN 301

4. compute the phasor voltage for the equivalent voltage $v_s(t)$ $v_1(t) = 15\cos(377t + \pi/4)$ $v_2(t) = 15\cos(377t + \pi/12)$





4. compute the phasor voltage for the equivalent voltage $v_s(t)$ $v_1(t) = 15\cos(377t + \pi/4)$ $v_2(t) = 15\cos(377t + \pi/12)$



- 1. Write voltages in phasor notation
- 2. Convert phasor voltages from polar to rectangular form (see Appendix A)
- 3. Combine voltages

$$V_{S}(j\omega) = V_{1}(j\omega) + V_{2}(j\omega)$$
$$= 25.10 + j14.49$$



21

ECEN 301

- 4. compute the phasor voltage for the equivalent voltage $v_s(t)$
 - $v_1(t) = 15\cos(377t + \pi/4)$
 - $v_2(t) = 15\cos(377t + \pi/12)$



- 1. Write voltages in phasor notation
- 2. Convert phasor voltages from polar to rectangular form (see Appendix A)
- 3. Combine voltages
- 4. Convert rectangular back to polar

$$V_{s}(j\omega) = 25.10 + j14.49$$

Convert to polar :
$$r = \sqrt{(25.10)^{2} + (14.49)^{2}}$$
$$= 28.98$$
$$\theta = \tan^{-1} \left(\frac{14.49}{25.10}\right)$$
$$= \frac{\pi}{6}$$
$$V_{s}(j\omega) = 28.98 \angle \frac{\pi}{6}$$



22

ECEN 301

- 4. compute the phasor voltage for the equivalent voltage $v_s(t)$
 - $v_1(t) = 15\cos(377t + \pi/4)$
 - $v_2(t) = 15\cos(377t + \pi/12)$





1.

2.

3.

4.

5.

NB: the answer is **NOT** simply the addition of the amplitudes of $\mathbf{v_1}(\mathbf{t})$ and $\mathbf{v_2}(\mathbf{t})$ (i.e. 15 + 15), and the addition of their phases (i.e. $\pi/4 + \pi/12$)

Write voltages in phasor notation

rectangular form (see Appendix A)

Convert rectangular back to polar

Convert from phasor to time domain

Combine voltages

Convert phasor voltages from polar to



4. compute the phasor voltage for the equivalent voltage $v_s(t)$ $v_1(t) = 15\cos(377t + \pi/4)$ $v_2(t) = 15\cos(377t + \pi/12)$





24

ECEN 301

Impedance: complex resistance (has no physical significance)

- will allow us to use network analysis methods such as node voltage, mesh current, etc.
- Capacitors and inductors act as frequency-dependent resistors





25

Impedance of resistors, inductors, and capacitors





26

ECEN 301

5. find the equivalent impedance (\mathbf{Z}_{EQ}) $\boldsymbol{\omega} = 10^4 \text{ rads/s}, \mathbf{C} = 10 \text{uF}, \mathbf{R}_1 = 100\Omega, \mathbf{R}_2 = 50\Omega, \mathbf{L} = 10 \text{mH}$





27

ECEN 301

5. find the equivalent impedance (\mathbf{Z}_{EQ}) $\boldsymbol{\omega} = 10^4 \text{ rads/s}, \mathbf{C} = 10 \text{uF}, \mathbf{R}_1 = 100\Omega, \mathbf{R}_2 = 50\Omega, \mathbf{L} = 10 \text{mH}$



$$Z_{EQ1} = Z_{R2} || Z_C$$

= $\frac{R_2(1/j\omega C)}{R_2 + (1/j\omega C)}$
= $\frac{R_2}{1 + j\omega CR_2}$
= $\frac{50}{1 + j(10^4)(10 \times 10^{-6})(50)}$
= $\frac{50}{1 + j5}$
= $1.92 - j9.62$
= $9.81 \angle (-1.37) \Omega$



28

ECEN 301



ECEN 301

Discussion #20 – Exam 2 Review

29

Electrical Engineering Computer Engineering

AC Circuit Analysis

- 1. Identify the AC sources and note the excitation frequency (ω)
- 2. Convert all sources to the phasor domain
- 3. Represent each circuit element by its impedance
- 4. Solve the resulting phasor circuit using network analysis methods
- 5. Convert from the phasor domain back to the time domain



6. find $i_a(t)$ and $i_b(t)$ $v_s(t) = 15\cos(1500t)V$, $R_1 = 100\Omega$, $R_2 = 75\Omega$, L = 0.5H, C = 1uF





6. find $i_a(t)$ and $i_b(t)$ $v_s(t) = 15\cos(1500t)V$, $R_1 = 100\Omega$, $R_2 = 75\Omega$, L = 0.5H, C = 1uF





6. find $i_a(t)$ and $i_b(t)$ $\mathbf{v}_s(t) = 15\cos(1500t)$ V, $\mathbf{R}_1 = 100\Omega$, $\mathbf{R}_2 = 75\Omega$, $\mathbf{L} = 0.5$ H, $\mathbf{C} = 1$ uF





ECEN 301

6. find $i_a(t)$ and $i_b(t)$ $v_s(t) = 15\cos(1500t)V$, $R_1 = 100\Omega$, $R_2 = 75\Omega$, L = 0.5H, C = 1uF





ECEN 301

6. find $i_a(t)$ and $i_b(t)$ $v_s(t) = 15\cos(1500t)V$, $R_1 = 100\Omega$, $R_2 = 75\Omega$, L = 0.5H, C = 1uF







ECEN 301

6. find $i_a(t)$ and $i_b(t)$ $v_s(t) = 15\cos(1500t)V$, $R_1 = 100\Omega$, $R_2 = 75\Omega$, L = 0.5H, C = 1uF




AC RLC Circuits

6. find $i_a(t)$ and $i_b(t)$ $v_s(t) = 15\cos(1500t)V$, $R_1 = 100\Omega$, $R_2 = 75\Omega$, L = 0.5H, C = 1uF



5. Convert to Time domain

$$I_1 = 0.0032 \angle 0.917 A$$

$$i_1(t) = 3.2\cos(1500t + 0.917) mA$$

$$I_2 = 0.019 \angle -1.49 A$$

$$i_2(t) = 19 \cos(1500 t - 1.49) mA$$



Thévenin and Norton equivalent circuits apply in AC analysis
▲ Equivalent voltage/current will be complex and frequency dependent





38

ECEN 301

Computation of Thévenin and Norton Impedances:

- 1. Remove the load (open circuit at load terminal)
- 2. Zero all independent sources
 - \wedge Voltage sources \longrightarrow short circuit ($\mathbf{v} = 0$)
 - $\land \quad \text{Current sources} \longrightarrow \text{open circuit} (i = 0)$
- 3. Compute equivalent impedance **across load terminals** (with load removed)





Computing Thévenin voltage:

- 1. Remove the load (open circuit at load terminals)
- 2. Define the open-circuit voltage (V_{oc}) across the load terminals
- 3. Chose a network analysis method to find V_{oc}
 - A node, mesh, superposition, etc.
- 4. Thévenin voltage $V_T = V_{oc}$



Computing Norton current:

- Replace the load with a short circuit 1.
- Define the short-circuit current (I_{sc}) across the load terminals 2.
- 3. Chose a network analysis method to find I_{sc}
 - node, mesh, superposition, etc. \mathbf{A}
- Norton current $I_N = I_{sc}$ 4.



Discussion #20 – Exam 2 Review

Electrical Engineering **Computer Engineering**

7. find the Thévenin equivalent $\omega = 10^3$ Hz, $\mathbf{R}_s = 50\Omega$, $\mathbf{R}_L = 50\Omega$, $\mathbf{L} = 10$ mH, $\mathbf{C} = 0.1$ uF





ECEN 301

7. find the Thévenin equivalent $\omega = 10^3$ Hz, $\mathbf{R}_s = 50\Omega$, $\mathbf{R}_L = 50\Omega$, $\mathbf{L} = 10$ mH, $\mathbf{C} = 0.1$ uF





7. find the Thévenin equivalent $\omega = 10^3$ Hz, $\mathbf{R}_s = 50\Omega$, $\mathbf{R}_L = 50\Omega$, $\mathbf{L} = 10$ mH, $\mathbf{C} = 0.1$ uF



44

ECEN 301

7. find the Thévenin equivalent $\omega = 10^3$ Hz, $\mathbf{R}_s = 50\Omega$, $\mathbf{R}_L = 50\Omega$, $\mathbf{L} = 10$ mH, $\mathbf{C} = 0.1$ uF



- 1. Note frequencies of AC sources
- 2. Convert to phasor domain
- 3. Find $\mathbf{Z}_{\mathbf{T}}$

• Remove load & zero sources

$$Z_T = Z_S + Z_C \parallel Z_L$$

= $R_S + \frac{(j\omega L)(1/j\omega C)}{(j\omega L) + (1/j\omega C)}$
= $R_S + j \frac{\omega L}{1 - \omega^2 LC}$
= $50 + j65.414$
= $82.33 \angle 0.9182$



45

7. find the Thévenin equivalent $\omega = 10^3$ Hz, $\mathbf{R}_s = 50\Omega$, $\mathbf{R}_L = 50\Omega$, $\mathbf{L} = 10$ mH, $\mathbf{C} = 0.1$ uF





- 1. Note frequencies of AC sources
- 2. Convert to phasor domain
- 3. Find $\mathbf{Z}_{\mathbf{T}}$
 - Remove load & zero sources
- 4. Find $V_T(j\omega)$
 - Remove load

NB: Since no current flows in the circuit once the load is removed:





46

7. find the Thévenin equivalent $\omega = 10^3$ Hz, $\mathbf{R}_s = 50\Omega$, $\mathbf{R}_L = 50\Omega$, $\mathbf{L} = 10$ mH, $\mathbf{C} = 0.1$ uF





47

ECEN 301

Transient response of a circuit consists of 3 parts:

- Steady-state response prior to the switching on/off of a DC source
- 2. Transient response the circuit **adjusts** to the **DC source**
- 3. Steady-state response following the transient response





Initial condition x(0): DC steady state **before** a switch is first activated

 \land **x**(**0**⁻): right before the switch is closed

 \land **x**(**0**⁺): right after the switch is closed

Final condition $x(\infty)$: DC steady state a long time **after** a switch is activated



Discussion #20 – Exam 2 Review

Electrical Engineering Computer Engineering

Remember – capacitor voltages and inductor currents cannot change instantaneously

Capacitor voltages and inductor currents don't change right before closing and right after closing a switch

$$v_C(0^+) = v_C(0^-)$$

 $i_L(0^+) = i_L(0^-)$



8. find the initial and final current conditions at the inductor

 $i_s = 10 \text{mA}$





- 8. find the initial and final current conditions at the inductor
 - $i_s = 10 \text{mA}$

I. Initial conditions – assume the current across the inductor is in steady-state.



Discussion #20 – Exam 2 Review

Electrical Engineering Computer Engineering

- 8. find the initial and final current conditions at the inductor
 - $i_s = 10 \text{mA}$

1. Initial conditions – assume the current across the inductor is in steady-state.



$$i_L(0^-) = i_s$$
$$= 10 mA$$



- 8. find the initial and final current conditions at the inductor
 - $i_s = 10 \text{mA}$

- 1. Initial conditions assume the current across the inductor is in steady-state.
- 2. Throw the switch



NB: inductor current cannot change instantaneously



54

- 8. find the initial and final current conditions at the inductor
 - $i_s = 10 \text{mA}$

- 1. Initial conditions assume the current across the inductor is in steady-state.
- 2. Throw the switch





55

- 8. find the initial and final current conditions at the inductor
 - $i_s = 10 \text{mA}$



- 1. Initial conditions assume the current across the inductor is in steady-state.
- 2. Throw the switch
- 3. Final conditions



NB: in DC steady state inductors act like short circuits



56

Solving 1st order transient response:

- 1. Solve the **DC** steady-state circuit:
 - A Initial condition $\mathbf{x}(\mathbf{0}^{-})$: before switching (on/off)
 - Final condition $\mathbf{x}(\infty)$: After any transients have died out $(t \to \infty)$
- 2. Identify $x(0^+)$: the circuit initial conditions
 - Capacitors: $\mathbf{v}_{\mathbf{C}}(\mathbf{0}^+) = \mathbf{v}_{\mathbf{C}}(\mathbf{0}^-)$
 - A Inductors: $i_{\rm L}(0^+) = i_{\rm L}(0^-)$
- 3. Write a differential equation for the circuit at time $t = 0^+$
 - Reduce the circuit to its Thévenin or Norton equivalent
 - ▲ The energy storage element (capacitor or inductor) is the load
 - A The differential equation will be either in terms of $\mathbf{v}_{\mathbf{C}}(\mathbf{t})$ or $\mathbf{i}_{\mathbf{L}}(\mathbf{t})$
 - Reduce this equation to standard form
- 4. Solve for the **time constant**
 - $\land \quad \text{Capacitive circuits: } \boldsymbol{\tau} = \mathbf{R}_{\mathrm{T}}\mathbf{C}$
 - $\land Inductive circuits: \tau = L/R_T$
- 5. Write the **complete response** in the form:

 $\mathbf{x}(t) = \mathbf{x}(\infty) + [\mathbf{x}(0) - \mathbf{x}(\infty)] \mathbf{e}^{-t/\tau}$

9. find $\mathbf{v_c}(\mathbf{t})$ for all t $\mathbf{v_s} = 12V, \mathbf{v_C}(\mathbf{0}) = 5V, \mathbf{R} = 1000\Omega, \mathbf{C} = 470 \mathrm{uF}$





9. find $\mathbf{v_c}(\mathbf{t})$ for all t $\mathbf{v_s} = 12V, \mathbf{v_C}(\mathbf{0}) = 5V, \mathbf{R} = 1000\Omega, \mathbf{C} = 470 \mathrm{uF}$



NB: as $t \to \infty$ the capacitor acts like an open circuit thus $\mathbf{v}_{\mathbf{C}}(\infty) = \mathbf{v}_{\mathbf{S}}$



- a) Initial condition: $\mathbf{v}_{\mathbf{C}}(\mathbf{0})$
- b) Final condition: $\mathbf{v}_{\mathbf{C}}(\infty)$

$$v_C(t < 0) = v_C(0^-) = 5V$$

$$v_C(\infty) = v_S$$

= 12V



ECEN 301

9. find $\mathbf{v_c}(\mathbf{t})$ for all t $\mathbf{v_s} = 12V, \mathbf{v_C}(\mathbf{0}) = 5V, \mathbf{R} = 1000\Omega, \mathbf{C} = 470 \mathrm{uF}$



2. Circuit initial conditions: $v_{C}(0^{+})$

$$v_C(0^+) = v_C(0^-)$$
$$= 5V$$



9. find $\mathbf{v_c}(\mathbf{t})$ for all t $\mathbf{v_s} = 12V, \mathbf{v_C}(\mathbf{0}) = 5V, \mathbf{R} = 1000\Omega, \mathbf{C} = 470 \mathrm{uF}$



3. Write differential equation (already in Thévenin equivalent) at t = 0

$$KVL:$$

$$-v_{S} + v_{R}(t) + v_{C}(t) = 0$$

$$i_{C}(t)R + v_{C}(t) = v_{S}$$

$$RC \frac{dv_{C}(t)}{dt} + v_{C}(t) = v_{S}$$



61

ECEN 301

9. find $\mathbf{v_c}(\mathbf{t})$ for all t $\mathbf{v_s} = 12V, \mathbf{v_C}(\mathbf{0}) = 5V, \mathbf{R} = 1000\Omega, \mathbf{C} = 470 \mathrm{uF}$



4. Find the time constant τ

$$\tau = RC$$

= (1000)(470×10⁻⁶)
= 0.47

$$K_{S} = 1 \qquad F = v_{S} = 12$$



ECEN 301

9. find $\mathbf{v_c}(\mathbf{t})$ for all t $\mathbf{v_s} = 12V, \mathbf{v_C}(\mathbf{0}) = 5V, \mathbf{R} = 1000\Omega, \mathbf{C} = 470 \mathrm{uF}$





63

ECEN 301

Frequency Response H(jω): a measure of how the voltage/current/impedance of a load responds to the voltage/current of a source

$$H_{V}(j\omega) = \frac{V_{L}(j\omega)}{V_{S}(j\omega)} \qquad H_{I}(j\omega) = \frac{I_{L}(j\omega)}{I_{S}(j\omega)}$$

$$H_{Z}(j\omega) = \frac{V_{L}(j\omega)}{I_{S}(j\omega)}$$



64

ECEN 301

10. compute the frequency response $\mathbf{H}_{\mathbf{V}}(\mathbf{j}\boldsymbol{\omega})$ $\mathbf{R}_{\mathbf{1}} = 1k\Omega, \mathbf{R}_{\mathbf{L}} = 10k\Omega, \mathbf{C} = 10\mathrm{uF}$





ECEN 301

10. compute the frequency response $\mathbf{H}_{\mathbf{V}}(\mathbf{j}\boldsymbol{\omega})$ $\mathbf{R}_{\mathbf{1}} = 1k\Omega, \mathbf{R}_{\mathbf{L}} = 10k\Omega, \mathbf{C} = 10\mathrm{uF}$



1. Note frequencies of AC sources

Only one AC source so frequency response $H_V(j\omega)$ will be the function of a single frequency



10. compute the frequency response $\mathbf{H}_{\mathbf{V}}(\mathbf{j}\boldsymbol{\omega})$ $\mathbf{R}_{\mathbf{1}} = 1k\Omega, \mathbf{R}_{\mathbf{L}} = 10k\Omega, \mathbf{C} = 10\mathrm{uF}$





10. compute the frequency response $H_V(j\omega)$ $R_1 = 1k\Omega$, $R_L = 10k\Omega$, C = 10uF



- 1. Note frequencies of AC sources
- 2. Convert to phasor domain
- 3. Solve using network analysis
 - Thévenin equivalent





10. compute the frequency response $H_V(j\omega)$ $R_1 = 1k\Omega$, $R_L = 10k\Omega$, C = 10uF



- 1. Note frequencies of AC sources
- 2. Convert to phasor domain
- 3. Solve using network analysis
 - Thévenin equivalent

$$V_T(j\omega) = V_S(j\omega) \frac{Z_C}{Z_1 + Z_C}$$

$$Z_T = Z_1 \parallel Z_C$$



69

10. compute the frequency response $\mathbf{H}_{\mathbf{V}}(\mathbf{j}\boldsymbol{\omega})$ $\mathbf{R}_{\mathbf{1}} = 1 \mathrm{k}\Omega, \, \mathbf{R}_{\mathbf{L}} = 10 \mathrm{k}\Omega, \, \mathbf{C} = 10 \mathrm{uF}$



70

ECEN 301

10. compute the frequency response $\mathbf{H}_{\mathbf{V}}(\mathbf{j}\boldsymbol{\omega})$ $\mathbf{R}_{\mathbf{1}} = 1 \mathrm{k}\Omega, \, \mathbf{R}_{\mathbf{L}} = 10 \mathrm{k}\Omega, \, \mathbf{C} = 10 \mathrm{uF}$



5. Find an expression for the frequency response

$$H_{V}(j\omega) = \frac{V_{L}(j\omega)}{V_{S}(j\omega)}$$
$$= \frac{Z_{C}}{Z_{1} + Z_{C}} \cdot \frac{Z_{LD}}{\boldsymbol{\mathcal{I}}_{1} \parallel Z_{C}}$$



10. compute the frequency response $\mathbf{H}_{\mathbf{V}}(\mathbf{j}\boldsymbol{\omega})$ $\mathbf{R}_{\mathbf{1}} = 1 \mathrm{k}\Omega, \, \mathbf{R}_{\mathbf{L}} = 10 \mathrm{k}\Omega, \, \mathbf{C} = 10 \mathrm{uF}$



5. Find an expression for the frequency response

$$H_{V}(j\omega) = \frac{Z_{C}}{Z_{1} + Z_{C}} \cdot \frac{Z_{LD}}{\langle \mathbf{\ell}_{1} \parallel Z_{C} \rangle + Z_{LD}}$$

$$= \frac{Z_{LD}Z_{C}}{Z_{LD} \langle \mathbf{\ell}_{1} + Z_{C} \rangle + Z_{1}Z_{C}}$$

$$= \frac{10^{4} / (j\omega \times 10^{-5})}{10^{4} 10^{3} + 1 / (j\omega \times 10^{-5}) + 10^{3} / (j\omega \times 10^{-5})}$$

$$= \frac{100}{110 + j\omega}$$

$$= \frac{100}{\sqrt{110^{2} + \omega^{2}}} \angle -\arctan\left(\frac{\omega}{110}\right)$$



72
Frequency Response

10. compute the frequency response $\mathbf{H}_{\mathbf{V}}(\mathbf{j}\boldsymbol{\omega})$ $\mathbf{R}_{\mathbf{1}} = 1 \mathrm{k}\Omega, \, \mathbf{R}_{\mathbf{L}} = 10 \mathrm{k}\Omega, \, \mathbf{C} = 10 \mathrm{uF}$





73

Basic Filters

Electric circuit filter: attenuates (reduces) or eliminates signals at unwanted frequencies





74

ECEN 301

Basic Filters – Resonant Frequency

<u>Resonant Frequency (\omega_n)</u>: the frequency at which capacitive impedance and inductive impedance are equal and opposite (in 2nd order filters)





75

ECEN 301

Basic Filters – Resonant Frequency

<u>Resonant Frequency (\omega_n)</u>: the frequency at which capacitive impedance and inductive impedance are equal and opposite (in 2nd order filters)

Impedances in series



$$Z_L = \frac{j\sqrt{LC}}{C}$$
$$Z_C = -\frac{j\sqrt{LC}}{C}$$

$$Z_{EQ} = Z_L + Z_C$$
$$= 0$$



ECEN 301

Basic Filters – Resonant Frequency

<u>Resonant Frequency (\omega_n)</u>: the frequency at which capacitive impedance and inductive impedance are equal and opposite (in 2nd order filters)







$$Z_{EQ} = Z_L || Z_C$$
$$= \frac{Z_L Z_C}{Z_L + Z_C}$$
$$= \frac{L/C}{0}$$
$$= \infty$$



ECEN 301

Basic Filters – Low-Pass Filters

<u>**Low-pass Filters</u>**: only allow signals under the **cutoff** frequency (ω_0) to pass</u>



ECEN 301

Discussion #20 – Exam 2 Review

Electrical Engineering Computer Engineering

Basic Filters – High-Pass Filters

<u>High-pass Filters</u>: only allow signals above the cutoff frequency (ω_0) to pass



Discussion #20 – Exam 2 Review

79

Electrical Engineering Computer Engineering

Basic Filters – Band-Pass Filters

<u>Band-pass Filters</u>: only allow signals between the **passband** (ω_a to ω_b) to pass



$$v_{i}(t) = \cos(\omega_{1}t) + \cos(\omega_{2}t) \longrightarrow H_{B}(j\omega) \longrightarrow v_{o}(t) = \cos(\omega_{2}t)$$
$$+ \cos(\omega_{3}t) \longrightarrow V_{O}(t) = \cos(\omega_{2}t)$$



ECEN 301

Basic Filters – Band-Stop Filters

<u>Band-stop Filters</u>: allow signals except those between the **stopband** (ω_a to ω_b) to pass





Discussion #20 – Exam 2 Review

ECEN 301

Op-Amps – Open-Loop Mode

Open-Loop Model: an ideal op-amp acts like a **difference amplifier** (a device that amplifies the difference between two input voltages)



Discussion #20 – Exam 2 Review

82

Electrical Engineering Computer Engineering





83





84

ECEN 301





85





ECEN 301

11. find an expression for the gain $C_F = 1/6 \text{ F}, R_1 = 3\Omega, R_2 = 2\Omega, C_S = 1/6 \text{ F}$





ECEN 301





88









90



