

Schedule...

Date	Day	Class No.	Title	Chapters	HW Due date	Lab Due date	Exam
24 Nov	Mon	24	DAC	15.4			→
25 Nov	Tue		Recitation		HW 10		
26 Nov	Wed		Thanksgiving				
27 Nov	Thu		Thanksgiving				
28 Nov	Fri		Thanksgiving				
29 Nov	Sat						→
30 Nov	Sun						→
1 Dec	Mon		Final Review			LAB 8	→
2 Dec	Tue						

Conversion


Luke 22:32

32 But I have prayed for thee, that thy faith fail not: and when thou art **converted**, strengthen thy brethren.

Lecture 24 – Digital to Analog Converters (DACs)


ADC/DAC

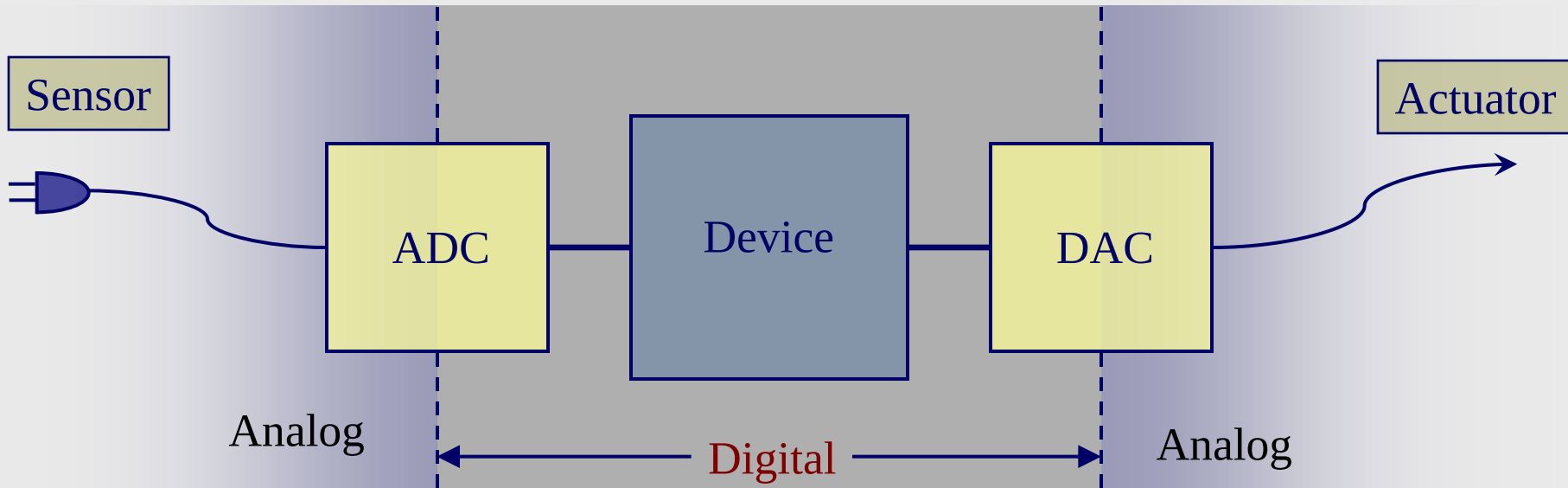- ◆ Power coming from the wall is **analog**, but most devices (appliances, computers, etc.) are **digital** thus there must be a conversion
 - ▲ **Analog to digital (ADC)** – coming into a device
 - ▲ **Digital to analog (DAC)** – going out of a device



ADC/DAC

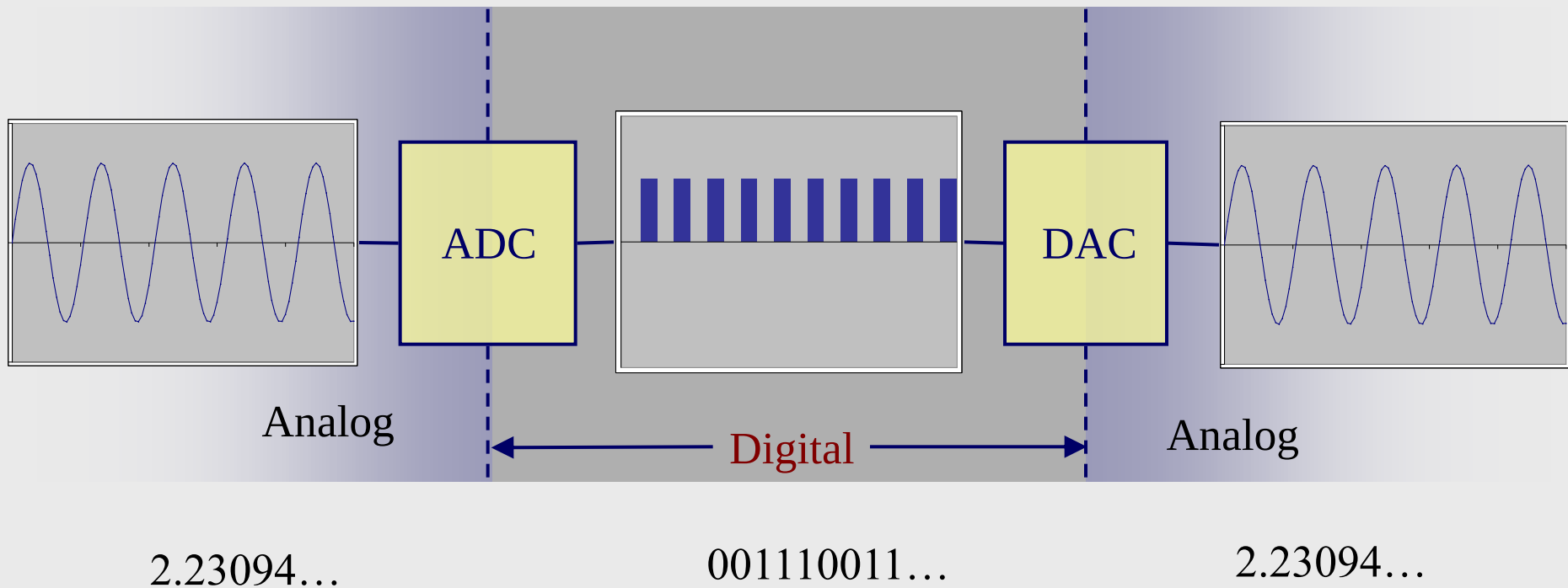- ◆ Power coming from the wall is **analog**, but most devices (appliances, computers, etc.) are **digital** thus there must be a conversion
 - ▲ **Analog to digital (ADC)** – coming into a device
 - ▲ **Digital to analog (DAC)** – going out of a device



Digital to Analog Converter (DAC)

DAC: converts a **binary word** to an analog output voltage or current

Binary word (B): a sequence of n **1s** and **0s**

$$B = b_{n-1}b_{n-2}\dots b_2b_1b_0$$

- EX:

$$B = 10100101 \quad (n = 8)$$

Word length (n): the number of bits in the sequence of **1s** and **0s** representing an output

- EX:

0110 – 4-bit word length

100101 – 6-bit word length

Digital to Analog Converter (DAC)

DAC: converts a **binary word** to an analog output voltage or current

Resolution δv : minimum step size by which the output voltage (or current) can increment

Output voltage v_a : the analog value represented by the binary word **B**

•EX: let $n=4$

$$v_a = (2^3 \cdot b_3 + 2^2 \cdot b_2 + 2^1 \cdot b_1 + 2^0 \cdot b_0) \delta v$$

Max output voltage v_{aMax} : the maximum analog value

•EX: let $n=4$

$$\begin{aligned} v_{aMax} &= (2^3 + 2^2 + 2^1 + 2^0) \delta v \\ &= (2^n - 1) \delta v \end{aligned}$$

Example: $\delta v = 1V$, **B** = 10110 ($n = 5$)
Find v_{aMax} and v_a


$$\begin{aligned} v_{aMax} &= (2^n - 1) \delta v \\ &= (2^5 - 1) \cdot 1 \\ &= 31 \end{aligned}$$

$$\begin{aligned} v_a &= (2^4 \cdot b_4 + 2^3 \cdot b_3 + 2^2 \cdot b_2 + 2^1 \cdot b_1 + 2^0 \cdot b_0) \delta v \\ &= (16 \cdot 1 + 8 \cdot 0 + 4 \cdot 1 + 2 \cdot 1 + 1 \cdot 0) \cdot 1 \\ &= (16 + 4 + 2) \\ &= 22 \end{aligned}$$



Digital to Analog Converter (DAC)

Building a DAC:

use a summing amplifier

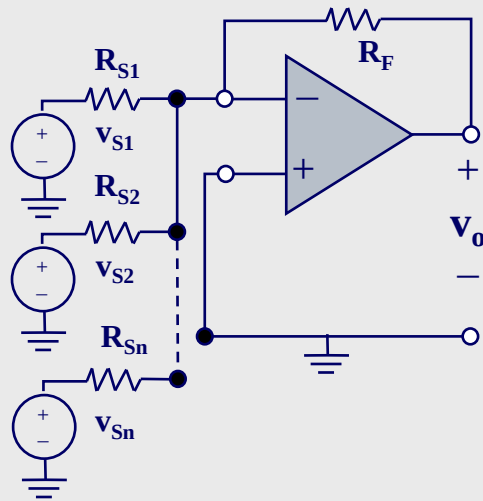

Summing amplifier

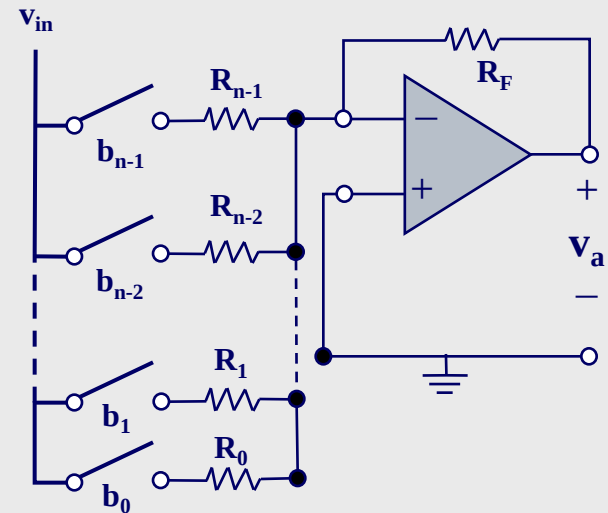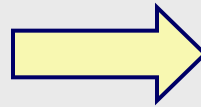


DAC

Digital to Analog Converter (DAC)

Building a DAC:

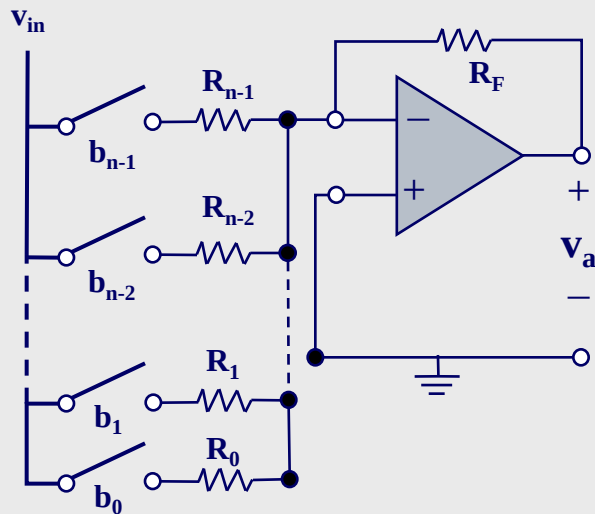the analog output (v_a) is proportional to the binary word **B**



$$v_a = - \sum_{i=0}^{n-1} \frac{R_F}{R_i} \cdot b_i \cdot v_{in}$$

Choose

$$R_i = \frac{R_0}{2^i}$$

v_{si} in summing amplifier


THUS

$$v_a = - \frac{R_F}{R_0} \cdot v_{in} \sum_{i=0}^{n-1} 2^i \cdot b_i$$

Digital to Analog Converter (DAC)

Example1: $v_{in} = 5V$, $\mathbf{B} = 1011$, $\mathbf{R}_0 = 32k\Omega$, $\mathbf{R}_F = 64k\Omega$


Find $\mathbf{R}_n$ and $\mathbf{v}_a$

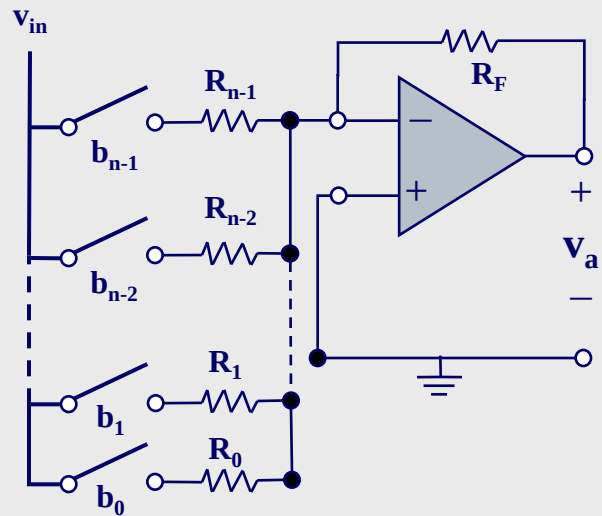

Digital to Analog Converter (DAC)

Example 1: $v_{in} = 5V$, $\mathbf{B} = 1011$, $R_0 = 32k\Omega$, $R_F = 64k\Omega$

Find R_n and v_a

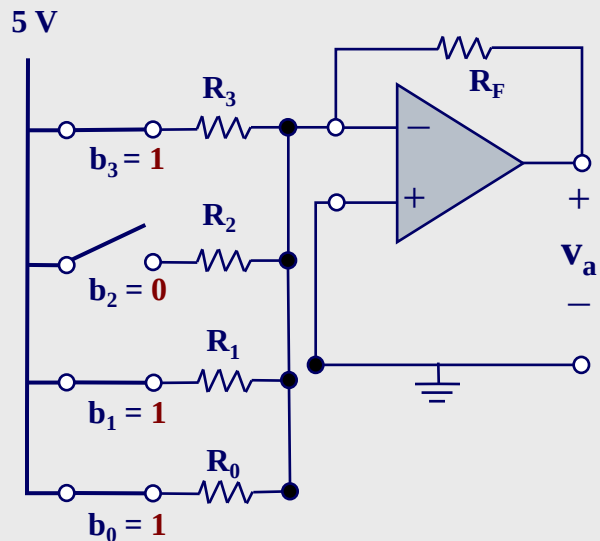

$$R_1 = \frac{R_0}{2^1} = \frac{32k\Omega}{2} = 16k\Omega$$

$$R_2 = \frac{R_0}{2^2} = \frac{32k\Omega}{4} = 8k\Omega$$


$$R_3 = \frac{R_0}{2^3} = \frac{32k\Omega}{8} = 4k\Omega$$

$$\begin{aligned} v_a &= -\frac{R_F}{R_0} \cdot v_{in} \sum_{i=0}^{n-1} 2^i \cdot b_i \\ &= -\frac{64k\Omega}{32k\Omega} \cdot 5 \cdot [2^3 \cdot b_3 + 2^2 \cdot b_2 + 2^1 \cdot b_1 + 2^0 \cdot b_0] \\ &= -10 \cdot [8 \cdot 1 + 4 \cdot 0 + 2 \cdot 1 + 1 \cdot 1] \\ &= -10 \cdot [11] \\ &= -110V \end{aligned}$$

Digital to Analog Converter (DAC)

Building a DAC:

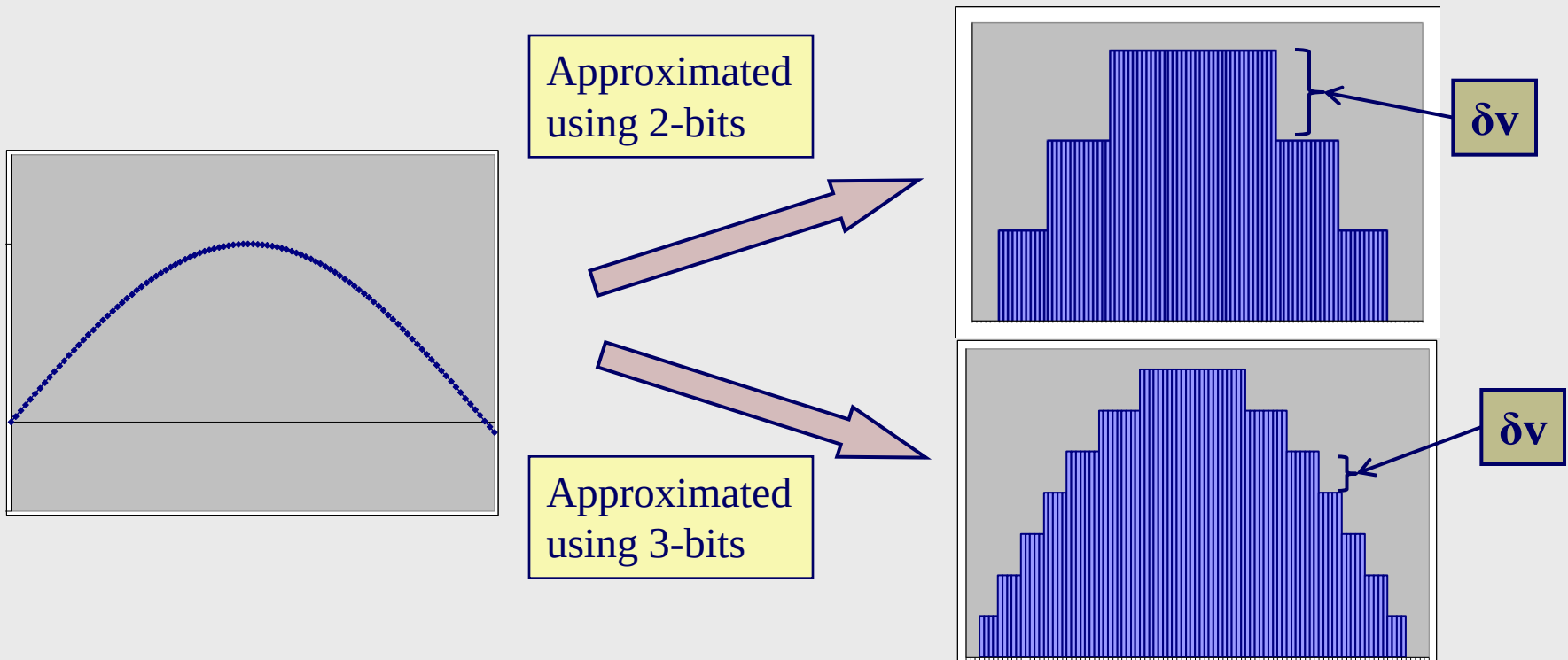
- ▶ the analog output (v_a) has a step-like appearance because of the discrete nature of a binary signal
- ▶ The **resolution** (coarseness of the “staircase”) can be adjusted by changing the **word length** (the number of bits)



Digital to Analog Converter (DAC)

Example2: find the smallest resolution δv of an 8-bit DAC


$$V_{a\text{Max}} = 12V$$

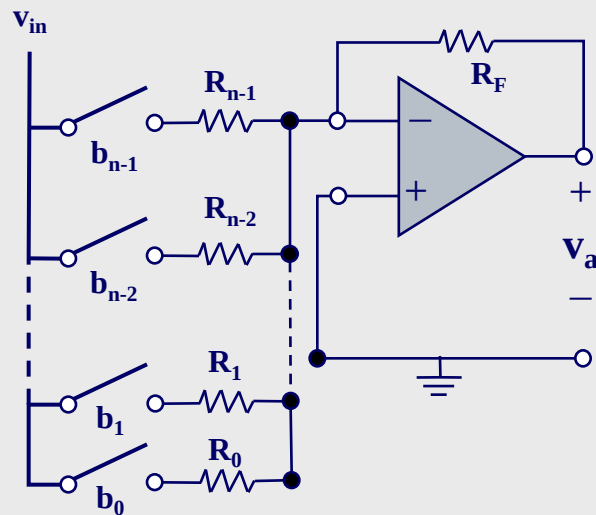

Digital to Analog Converter (DAC)

Example 2: find the smallest resolution δv of an 8-bit DAC

$$V_{a\text{Max}} = 12\text{V}$$

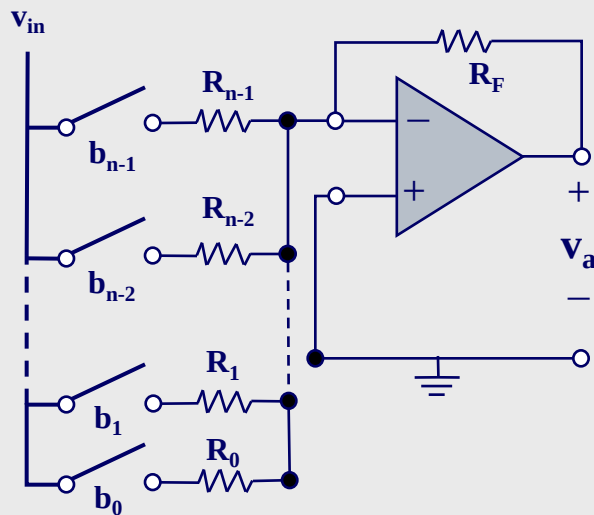


$$\begin{aligned} V_{a\text{max}} &= (2^n - 1) \delta v \\ \delta v &= \frac{V_{a\text{max}} - V_{a\text{min}}}{(2^n - 1)} \\ &= \frac{12 - 0}{(2^8 - 1)} \\ &= 47.1 \text{ mV} \end{aligned}$$

Digital to Analog Converter (DAC)

Example3: find an expression for the number of bits required in a DAC for a given **range** and **resolution**

$$\text{range} = V_{a\text{Max}} - V_{a\text{Min}}$$

$$\text{resolution} = \delta v$$

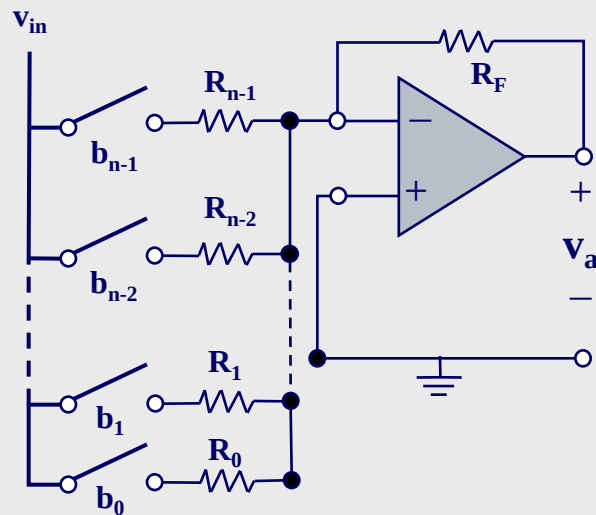


Digital to Analog Converter (DAC)

Example3: find an expression for the number of bits required in a DAC for a given **range** and **resolution**

$$\text{range} = V_{a\text{Max}} - V_{a\text{Min}}$$

$$\text{resolution} = \delta v$$

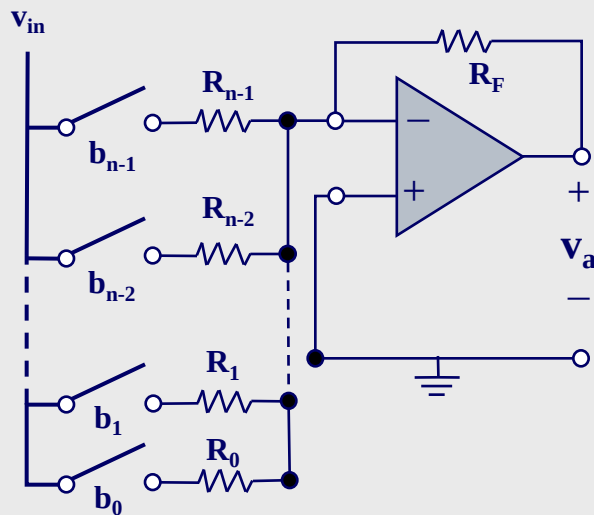

$$\delta v = \frac{V_{a\text{max}} - V_{a\text{min}}}{2^n - 1}$$

$$2^n - 1 = \frac{V_{a\text{max}} - V_{a\text{min}}}{\delta v}$$

$$2^n = \frac{V_{a\text{max}} - V_{a\text{min}}}{\delta v} + 1$$

$$n = \log_2 \left(\frac{V_{a\text{max}} - V_{a\text{min}}}{\delta v} + 1 \right)$$


$$n = \left\lceil \frac{\log_{10} (V_{a\text{max}} - V_{a\text{min}}) / \delta v + 1}{\log_{10} 2} \right\rceil$$

Digital to Analog Converter (DAC)

Example4: find the number of bits required in a DAC given that:

range = 10V

resolution = 10 mV

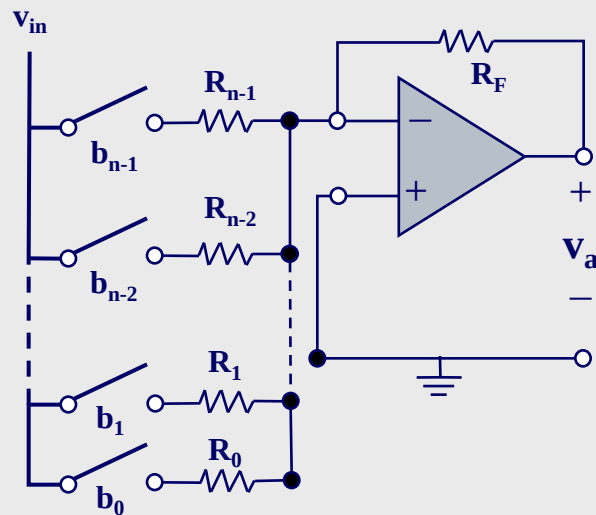


Digital to Analog Converter (DAC)

Example4: find the number of bits required in a DAC given that:

range = 10V

resolution = 10 mV

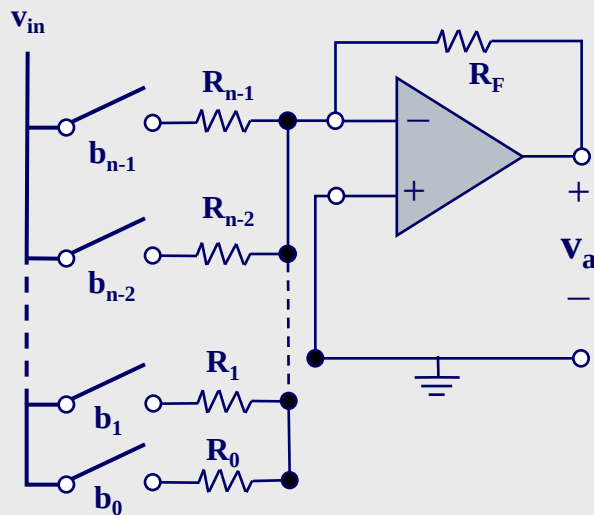

$$\begin{aligned} n &= \left\lceil \frac{\log (v_{a \max } - v_{a \min }) / \delta v + 1}{\log 2} \right\rceil \\ &= \left\lceil \frac{\log (10 / 10^{-2} + 1)}{\log 2} \right\rceil \\ &= \left\lceil \frac{\log (1001)}{\log 2} \right\rceil \\ &= \lceil 9.97 \rceil \\ &= 10 \end{aligned}$$

Digital to Analog Converter (DAC)


Example5: find the resistor values for a DAC with:

range = 15V

$\delta v = 1V$

$v_{in} = 5V$

$R_F = 2k\Omega$

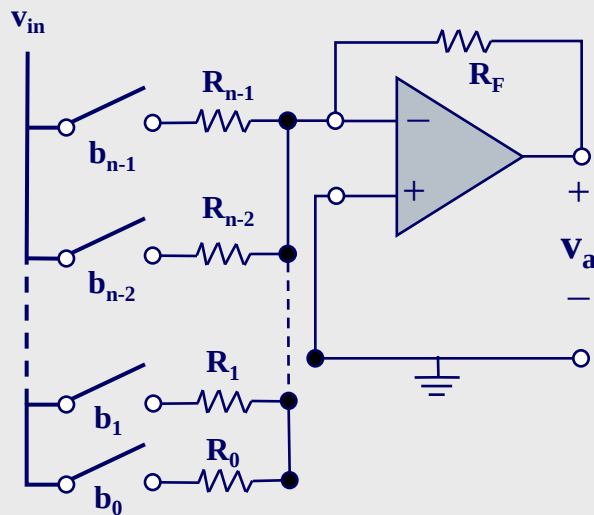

Digital to Analog Converter (DAC)


Example5: find the resistor values for a DAC with:

range = 15V

$\delta v = 1V$

$v_{in} = 5V$

$R_F = 2k\Omega$

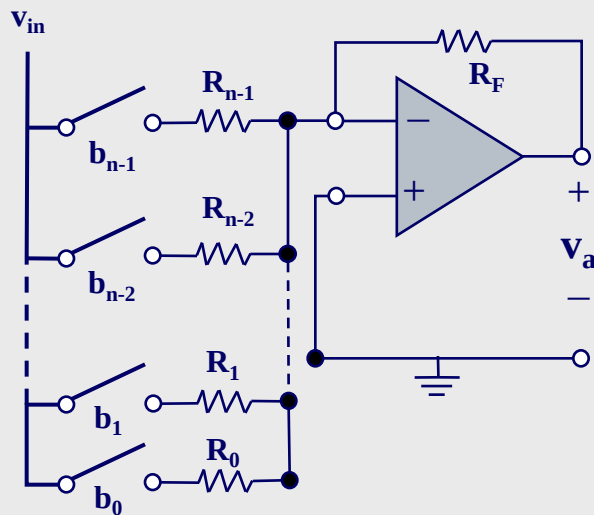

$$\begin{aligned} n &= \left\lceil \frac{\log (v_{a \max } - v_{a \min }) / \delta v + 1}{\log 2} \right\rceil \\ &= \left\lceil \frac{\log (5 / 1 + 1)}{\log 2} \right\rceil \\ &= 4 \\ &= 4 \end{aligned}$$

Digital to Analog Converter (DAC)


Example5: find the resistor values for a DAC with:

range = 15V

$\delta v = 1V$

$v_{in} = 5V$

$R_F = 2k\Omega$

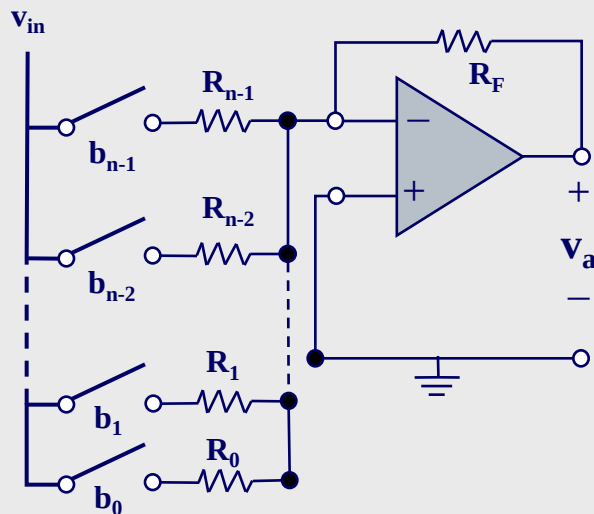

$$v_a = -\frac{R_F}{R_0} \cdot v_{in} \sum_{i=0}^{n-1} 2^i \cdot b_i$$
$$v_{a \max} = \frac{R_F}{R_0} \cdot v_{in} (2^n - 1)$$
$$R_0 = \frac{R_F \cdot v_{in} (2^n - 1)}{v_{a \max}}$$
$$= \frac{2}{15} (2^4 - 1)$$
$$= 10 \text{ k}\Omega$$

Digital to Analog Converter (DAC)


Example5: find the resistor values for a DAC with:

range = 15V

$\delta v = 1V$

$v_{in} = 5V$

$R_F = 2k\Omega$

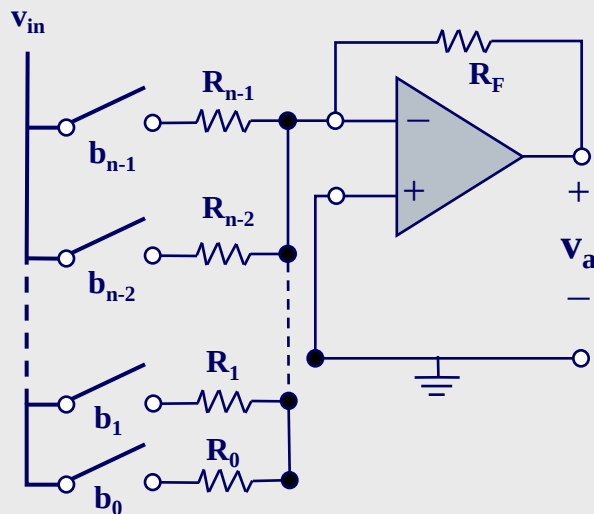

$$R_i = \frac{R_0}{2^i}$$

$$\begin{aligned} R_1 &= \frac{R_0}{2^1} \\ &= \frac{10^3}{2} \\ &= 5k\Omega \end{aligned}$$

$$\begin{aligned} R_2 &= \frac{R_0}{2^2} \\ &= \frac{10^3}{4} \\ &= 2.5k\Omega \end{aligned}$$

$$\begin{aligned} R_3 &= \frac{R_0}{2^3} \\ &= \frac{10^3}{8} \\ &= 1.25k\Omega \end{aligned}$$