

Schedule...

Date	Day	Class No.	Title	Chapters	HW Due date	Lab Due date	Exam
1 Dec	Mon	25	Final Review			LAB 8	
2 Dec	Tue						
3 Dec	Wed	26	Final Review				
4 Dec	Thu						
5 Dec	Fri		Recitation		HW 11		
6 Dec	Sat						
7 Dec	Sun						
8 Dec	Mon	27	Final Review			LAB 9	
9 Dec	Tue						

Summary

Jacob 6:12

12 O be wise; what can I say more?

Lecture 25 – Final Review

Final Exam

- ◆ 17 – 21 December
- ◆ Chapters 2 – 6, 8, 13 – 15
- ◆ 30 questions
 - ▲ 30 multiple choice (answer on bubble sheet!)
 - 1 point each
 - ▲ 0 long answer (show your work!)
 - 4 or 5 points each
- ◆ Closed book!
 - ▲ Three 3x5 cards allowed
- ◆ Calculators allowed
- ◆ No time limit
- ◆ Study lecture slides and homework

Final Exam Review...Overview

1. Exam 1 Review
2. Exam 2 Review
3. Binary Numbers
 - ▲ Signed & Unsigned
 - ▲ Conversions
4. Logic Functions
 - ▲ Conversions among 3 representations
5. Boolean Algebra
6. Combinational Logic
7. Sequential Logic
8. Digital to Analog Converters (DACs)

Binary Numbers – Unsigned

Binary word (B): a sequence of n 1s and 0s

$$B = b_{n-1}b_{n-2}\dots b_2b_1b_0.b_{-1}b_{-2}\dots b_{-(m-1)}b_{-m}$$

Binary point

▲ EX:

- B = 10100101.1001 (n = 8, m=4)

Converting from binary (B) to decimal (D)

$$B = b_{n-1}b_{n-2}\dots b_2b_1b_0.b_{-1}b_{-2}\dots b_{-(m-1)}b_{-m}$$

$$D = b_{n-1} \cdot 2^{n-1} + b_{n-2} \cdot 2^{n-2} + \dots + b_1 \cdot 2^1 + b_0 \cdot 2^0 \\ + b_{-1} \cdot 2^{-1} + b_{-2} \cdot 2^{-2} + \dots + b_{-(m-1)} \cdot 2^{-(m-1)} + b_{-m} \cdot 2^{-m}$$

Binary Numbers – Unsigned

Example1: What is 0110101.0101_2 in decimal?

Binary Numbers – Unsigned


Example 1: What is 0110101.0101_2 in decimal?

$$\begin{array}{cccccccccccc} 6 & 5 & 4 & 3 & 2 & 1 & 0 & -1 & -2 & -3 & -4 & \\ \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \\ 0110101.0101_2 & = & 0 \cdot 2^6 & + & 1 \cdot 2^5 & + & 1 \cdot 2^4 & + & 0 \cdot 2^3 & + & 1 \cdot 2^2 & + & 0 \cdot 2^1 \\ & & & & & & & & & & + & 1 \cdot 2^0 & + & 0 \cdot 2^{-1} & + & 1 \cdot 2^{-2} & + & 0 \cdot 2^{-3} & + & 1 \cdot 2^{-4} \\ & & & & & & & & & & = & 32 & + & 16 & + & 4 & + & 1 & + & 0.25 & + & 0.0625 \\ & & & & & & & & & & = & 53.3125_{10} \end{array}$$

Binary Numbers – Signed

3 common representations for **signed** integers:

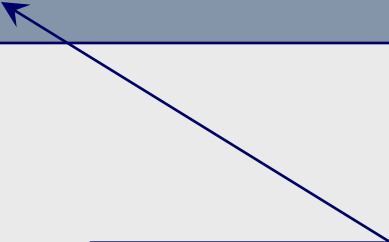1. Sign magnitude
2. 1's compliment
3. 2's compliment



Most common for computers

Binary Numbers – Sign-Magnitude

Range:

$$- (2^{n-1} - 1) \longrightarrow (2^{n-1} - 1)$$

Representations

▲ 01111_{binary} \Rightarrow 15_{decimal}

▲ 11111 \Rightarrow -15

▲ 00000 \Rightarrow 0

▲ 10000 \Rightarrow -0

The **MSB** encodes the sign:

$$0 = +$$

$$1 = -$$

Problem

▲ Difficult addition/subtraction

- check signs
- convert to positive
- use adder or subtractor as required

▲ How to add two sign-magnitude numbers?

- Ex: 1 + (-4)

Binary Numbers – 1's Complement

Range:

$$- \left(2^{n-1} - 1 \right) \longrightarrow \left(2^{n-1} - 1 \right)$$

Representations

▲ 00110 _{binary}	⇒ 6 _{decimal}
▲ 11001	⇒ -6
▲ 00000	⇒ 0
▲ 11111	⇒ -0

Problem

- ▲ Difficult addition/subtraction
 - no need to check signs as before
 - cumbersome logic circuits
 - *end-around-carry*
- ▲ How to add to one's complement numbers?
 - Ex: 4 + (-3)

To negate a number,
Invert it, bit-by-bit.

MSB still encodes
the sign:

$$\begin{aligned} 0 &= + \\ 1 &= - \end{aligned}$$

Binary Numbers – Two's Complement

Range: $-\left(2^{n-1}\right) \rightarrow \left(2^{n-1} - 1\right)$





Representation:

- ▲ If number is **positive** or **zero**,
 - normal binary representation, zeroes in upper bit(s)
- ▲ If number is **negative**,
 - start with positive number
 - flip every bit (i.e., take the one's complement)
 - then add one

MSB still encodes the sign:

$$0 = +$$

$$1 = -$$

	00101	(5)		01001	(9)
	11010	(1's comp)		10110	(1's comp)
+	1		+	1	
	<hr/>			<hr/>	
	11011	(-5)		10111	(-9)

Binary Numbers – Signed

Example2: What is the 2's complement of **0110101_2** ?

Binary Numbers – Signed

Example2: What is the 2's complement of 0110101_2 ?

0110101	(53)
1001010	(1's comp)
$+ \quad \quad \quad 1$	(add 1)
<hr/>	
1001011	(-53)

Binary Numbers – Decimal to Binary

Positive numbers

- ① start with empty result
- ② if decimal number is odd, prepend '1' to result
else prepend '0'
- ③ divide number by 2, throw away fractional part
(INTEGER divide)
- ④ if number is non-zero, go back to ② else you are done

Negative numbers

- ▲ do above for **positive version** of number and **negate result**.

Binary Numbers – Decimal to Binary

Example3: convert -195 to 2's complement binary notation

Binary Numbers – Decimal to Binary

Example3: convert -195 to 2's complement binary notation

1. First find positive version (195) in binary – then take 2's complement

	Is it odd?
195	1

Binary Numbers – Decimal to Binary

Example 3: convert -195 to 2's complement binary notation

1. First find positive version (195) in binary – then take 2's complement

Integer division by 2:
 $195/2 = 97.5 \rightarrow 97$

	Is it odd?
195	1
97	1

Binary Numbers – Decimal to Binary

Example 3: convert -195 to 2's complement binary notation

1. First find positive version (195) in binary – then take 2's complement

Integer division by 2:
 $97/2 = 48.5 \rightarrow 48$

	Is it odd?
195	1
97	1
48	0

Binary Numbers – Decimal to Binary

Example 3: convert -195 to 2's complement binary notation

1. First find positive version (195) in binary – then take 2's complement

Integer division by 2:
 $48/2 = 24$

	Is it odd?
195	1
97	1
48	0
24	0

Binary Numbers – Decimal to Binary

Example 3: convert -195 to 2's complement binary notation

1. First find positive version (195) in binary – then take 2's complement

Integer division by 2:
 $24/2 = 12$

	Is it odd?
195	1
97	1
48	0
24	0
12	0

Binary Numbers – Decimal to Binary

Example 3: convert -195 to 2's complement binary notation

1. First find positive version (195) in binary – then take 2's complement

Integer division by 2:
 $12/2 = 6$

	Is it odd?
195	1
97	1
48	0
24	0
12	0
6	0


Binary Numbers – Decimal to Binary

Example 3: convert -195 to 2's complement binary notation

1. First find positive version (195) in binary – then take 2's complement

	Is it odd?
195	1
97	1
48	0
24	0
12	0
6	0
3	1

Integer division by 2:
 $6/2 = 3$




Binary Numbers – Decimal to Binary

Example 3: convert -195 to 2's complement binary notation

1. First find positive version (195) in binary – then take 2's complement

	Is it odd?
195	1
97	1
48	0
24	0
12	0
6	0
3	1
1	1

Integer division by 2:
 $3/2 = 1.5 \rightarrow 1$



Binary Numbers – Decimal to Binary

Example 3: convert -195 to 2's complement binary notation

1. First find positive version (195) in binary – then take 2's complement

Integer division by 2:
 $1/2 = 0.5 \rightarrow 0$

	Is it odd?
195	1
97	1
48	0
24	0
12	0
6	0
3	1
1	1
0	0

Binary Numbers – Decimal to Binary

Example 3: convert -195 to 2's complement binary notation

1. First find positive version (195) in binary – then take 2's complement

	Is it odd?
195	1
97	1
48	0
24	0
12	0
6	0
3	1
1	1
0	0



011000011₂



2's complement

100111101₂

Hexadecimal Notation

- ◆ Binary is hard to read and write by hand
- ◆ Hexadecimal is a common alternative
 - ▲ 16 digits are **0123456789ABCDEF**

0100 0111 1000 1111 = 0x478F
1101 1110 1010 1101 = 0xDEAD
1011 1110 1110 1111 = 0xBEEF
1010 0101 1010 0101 = 0xA5A5

1. Separate binary code into groups of 4 bits (starting from the right)
2. Translate each group into a single hex digit

0x is a common prefix for writing numbers which means *hexadecimal*


Binary	Hex	Dec
0000	0	0
0001	1	1
0010	2	2
0011	3	3
0100	4	4
0101	5	5
0110	6	6
0111	7	7
1000	8	8
1001	9	9
1010	A	10
1011	B	11
1100	C	12
1101	D	13
1110	E	14
1111	F	15

Binary Numbers – Hexadecimal

Example4: convert $011101010001111010011010111_2$ to hexadecimal notation


Binary Numbers – Hexadecimal

 Example 4: convert $011101010001111010011010111_2$ to hexadecimal notation




Binary Numbers – Hexadecimal

 Example 4: convert $011101010001111010011010111_2$ to hexadecimal notation




Binary Numbers – Hexadecimal

 Example 4: convert $011101010001111010011010111_2$ to hexadecimal notation




Binary Numbers – Hexadecimal

 Example 4: convert $011101010001111010011010111_2$ to hexadecimal notation




Binary Numbers – Hexadecimal

 Example 4: convert $011101010001111010011010111_2$ to hexadecimal notation




Binary Numbers – Hexadecimal

 Example 4: convert $011101010001111010011010111_2$ to hexadecimal notation



Binary Numbers – Hexadecimal

 Example 4: convert $011101010001111010011010111_2$ to hexadecimal notation



NB: add a leading zero to complete 4 bits

Binary Numbers – Hexadecimal

Example4: convert **011101010001111010011010111**₂ to hexadecimal notation

011101010001111010011010111

0x3A8F4D7

Binary Numbers

Example5: Complete the following table

	Unsigned	Sign-magnitude	1's complement	2's complement	HEX
01100110					
11101011					
93					
-93					

Binary Numbers

Example5: Complete the following table

	Unsigned	Sign-magnitude	1's complement	2's complement	HEX
01100110	102	102	102	102	0x66
11101011	235	-107	-20	-21	0xEB
93	01011101	01011101	01011101	01011101	0x5D
-93	NA	11011101	10100010	10100011	0xA3



Logic Functions

3 different ways to represent logic functions:

1. **Equation**: a mathematical representation of a logic function

A bar over a variable represent an inverting or a **NOT** operation

$$out = \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab$$

Final logic output


Each letter variable represents a top-level input to the logic function

Mathematical operations (i.e. addition and multiplication) are boolean algebra operations

Logic Functions

3 different ways to represent logic functions:

2. **Gates**: a visual block representation of the function

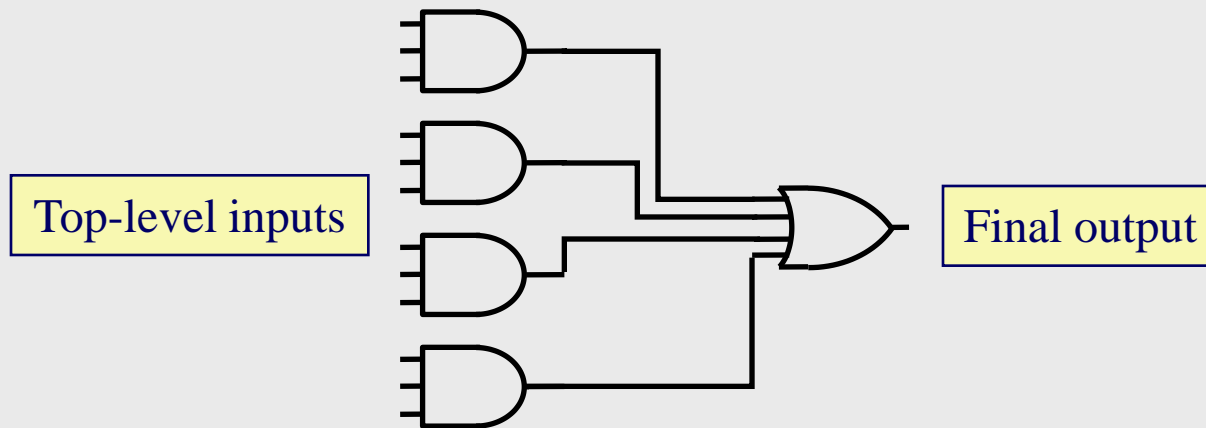

Four 3-input **AND** gates feeding into one 4-input **OR** gate

Logic Functions

3 different ways to represent logic functions:

3. **Truth Table:** indicates what the output will be for every possible input combination

If there are n inputs (left-hand columns) there will be 2^n entries (rows) in the table




EX: 3 inputs require $2^3 = 8$ rows

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



There will always be at least one output (right-hand columns)

For each input combination (row) output(s) will be either **0** or **1**

Logic Functions – Gates

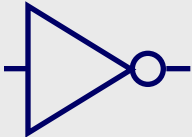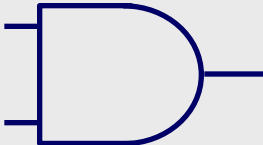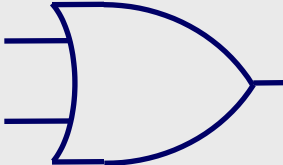Type	Symbol	Equation	Truth Table															
NOT		$OUT = \overline{IN}$	<table border="1"> <thead> <tr> <th>IN</th> <th>OUT</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> </tr> </tbody> </table>	IN	OUT	0	1	1	0									
IN	OUT																	
0	1																	
1	0																	
AND		$OUT = A \cdot B$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>OUT</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	A	B	OUT	0	0	0	0	1	0	1	0	0	1	1	1
A	B	OUT																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$OUT = A + B$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>OUT</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	A	B	OUT	0	0	0	0	1	1	1	0	1	1	1	1
A	B	OUT																
0	0	0																
0	1	1																
1	0	1																
1	1	1																

Logic Functions – Gates



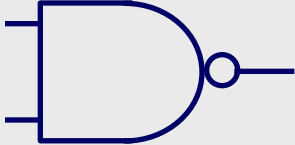
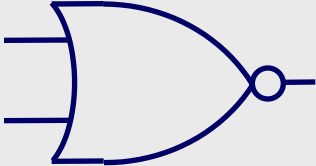
Type	Symbol	Equation	Truth Table															
NAND		$OUT = \overline{A \cdot B}$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>OUT</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	B	OUT	0	0	1	0	1	1	1	0	1	1	1	0
A	B	OUT																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$OUT = \overline{A + B}$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>OUT</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	B	OUT	0	0	1	0	1	0	1	0	0	1	1	0
A	B	OUT																
0	0	1																
0	1	0																
1	0	0																
1	1	0																

Logic Functions – Translation

These are three different ways of representing logical information

You can convert any one of them to any other

$$\overline{A \cdot B}$$

 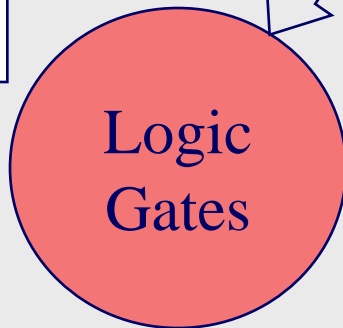 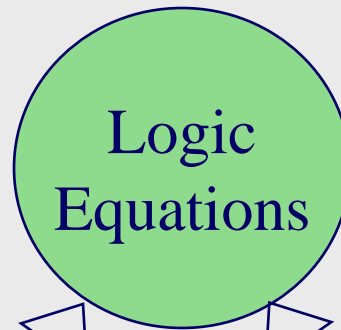



A	B	OUT
0	0	0
0	1	1
1	0	1
1	1	1

Equations to Gates


$$y = \text{NOT}(s) \text{ AND } a \text{ AND NOT}(b)$$

OR


$$y = \bar{s} \cdot a \cdot \bar{b}$$

  

OR

 

Logic Functions – Gates to Equations

 

$$out = (\bar{s} \cdot a \cdot \bar{b}) + (\bar{s} \cdot a \cdot b) + (s \cdot \bar{a} \cdot b) + (s \cdot a \cdot b)$$


OR

$$out = \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab$$

Logic Functions – Truth Tables to Gates

- ◆ Each row of truth table is an **AND** gate
- ◆ Each output column is an **OR** gate

S	A	B	OUT
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

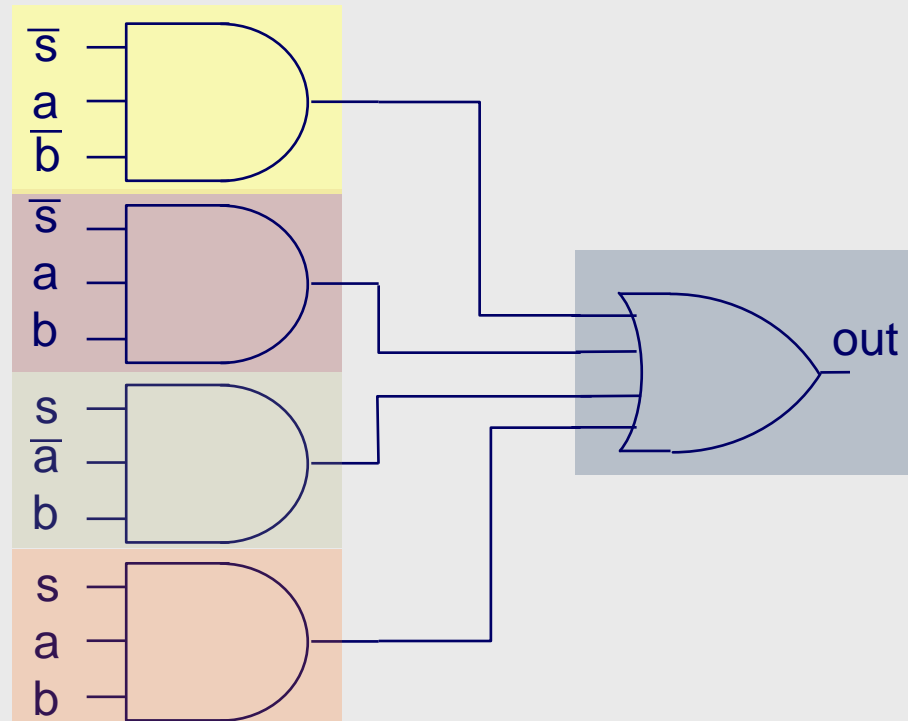

Logic Functions – Truth Table to Equations

- ◆ Write out truth table a combination of **AND**'s and **OR**'s
 - ▲ equivalent to gates
 - ▲ easily converted to gates

S	A	B	OUT
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$out = \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab$$

Logic Functions – Equations to Truth Tables

◆ For each **AND** term

▲ fill in the proper row on the truth table

$$out = \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab$$

S	A	B	OUT
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Boolean Algebra – Rules

$$1. \quad 0 + X = X$$

$$2. \quad 1 + X = 1$$

$$3. \quad X + X = X$$

$$4. \quad X + \bar{X} = 1$$

$$5. \quad 0 \cdot X = 0$$

$$6. \quad 1 \cdot X = X$$

$$7. \quad X \cdot X = X$$

$$8. \quad X \cdot \bar{X} = 0$$

$$9. \quad \bar{\bar{X}} = X$$

$$10. \quad X + Y = Y + X$$

$$11. \quad X \cdot Y = Y \cdot X$$

$$12. \quad X + (Y + Z) = (X + Y) + Z$$

$$13. \quad X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$$

$$14. \quad X \cdot (Y + Z) = X \cdot Y + X \cdot Z$$

$$15. \quad X + X \cdot Z = X$$

$$16. \quad X \cdot (X + Y) = X$$

$$17. \quad (X + Y) \cdot (X + Z) = X + Y \cdot Z$$



$$18. \quad X + \bar{X} \cdot Y = X + Y$$

$$19. \quad X \cdot Y + Y \cdot Z + \bar{X} \cdot Z = X \cdot Y + \bar{X} \cdot Z$$

Boolean Algebra – DeMorgan's Law

To distribute the bar,
change the operation.
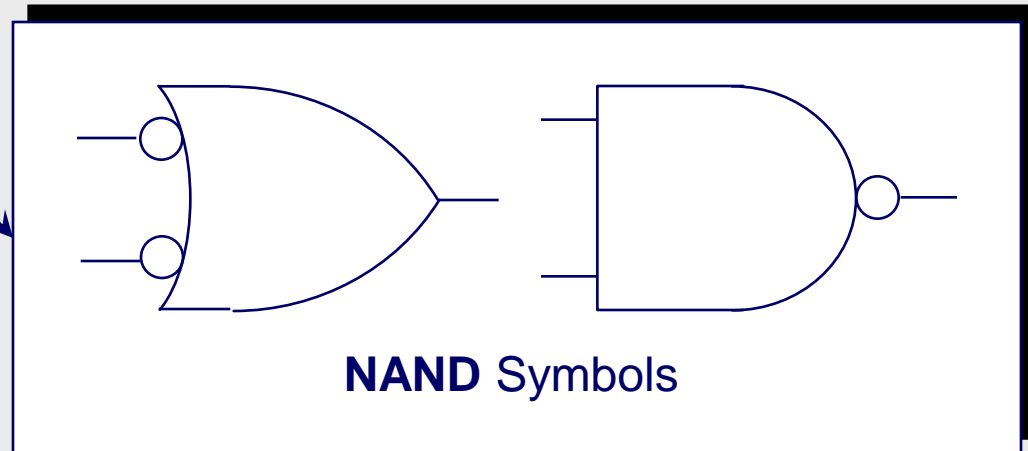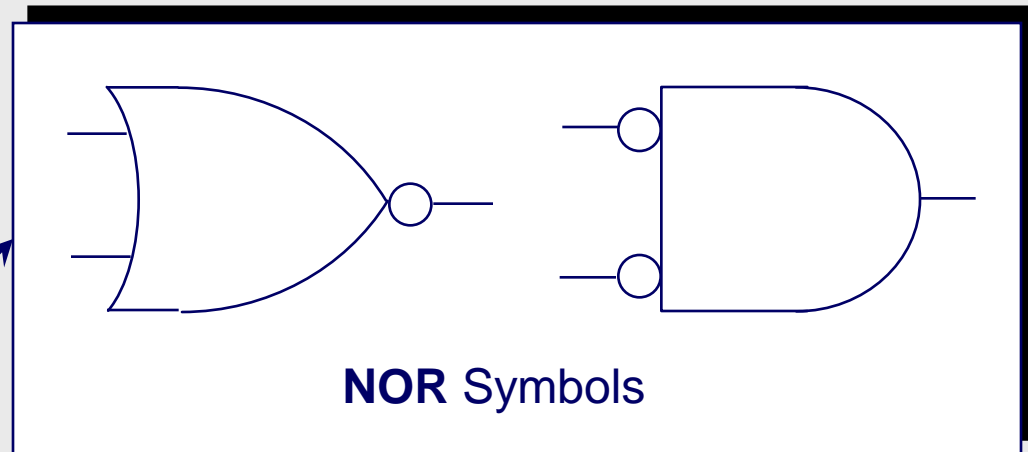
$$\overline{A + B} = \overline{A} \cdot \overline{B}$$
$$\overline{A \cdot B} = \overline{A} + \overline{B}$$



Boolean Algebra

Example 6: simplify the following function

$$OUT = \overline{A}\overline{B}D + \overline{A}BD + BCD + ACD$$

Boolean Algebra

Example 6: simplify the following function

$$OUT = \overline{A}\overline{B}D + \overline{A}BD + BCD + ACD \quad \text{Rule 14}$$

$$OUT = \overline{A}D(\overline{B} + B) + BCD + ACD \quad \text{Rule 4}$$

$$OUT = \overline{A}D + BCD + ACD \quad \text{Rule 14}$$

$$OUT = D(\overline{A} + AC) + BCD \quad \text{Rule 18}$$

$$OUT = D(\overline{A} + C) + BCD \quad \text{Rule 14}$$

$$OUT = \overline{A}D + CD + BCD \quad \text{Rule 14}$$

$$OUT = CD(1 + B) + \overline{A}D \quad \text{Rule 2}$$

$$OUT = CD + \overline{A}D \quad \text{Rule 14}$$

$$OUT = D(\overline{A} + C)$$

Boolean Algebra

Example7: Simplify the equation created by the following truth table

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Boolean Algebra

Example 7: Simplify the equation created by the following truth table

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$Z = \overline{A}\overline{B}C + \overline{A}BC + A\overline{B}\overline{C} + A\overline{B}C + AB\overline{C} + ABC$$

Boolean Algebra


Example 7: Simplify the equation created by the following truth table

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$\begin{aligned} Z &= \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + ABC\bar{C} + ABC \\ Z &= \bar{A}C(\bar{B} + B) + A\bar{B}(\bar{C} + C) + AB(\bar{C} + C) \\ Z &= \bar{A}C + A\bar{B} + AB \\ Z &= \bar{A}C + A(\bar{B} + B) \\ Z &= \bar{A}C + A \\ Z &= A + C \end{aligned}$$

Boolean Algebra


Example 8: Determine the truth table

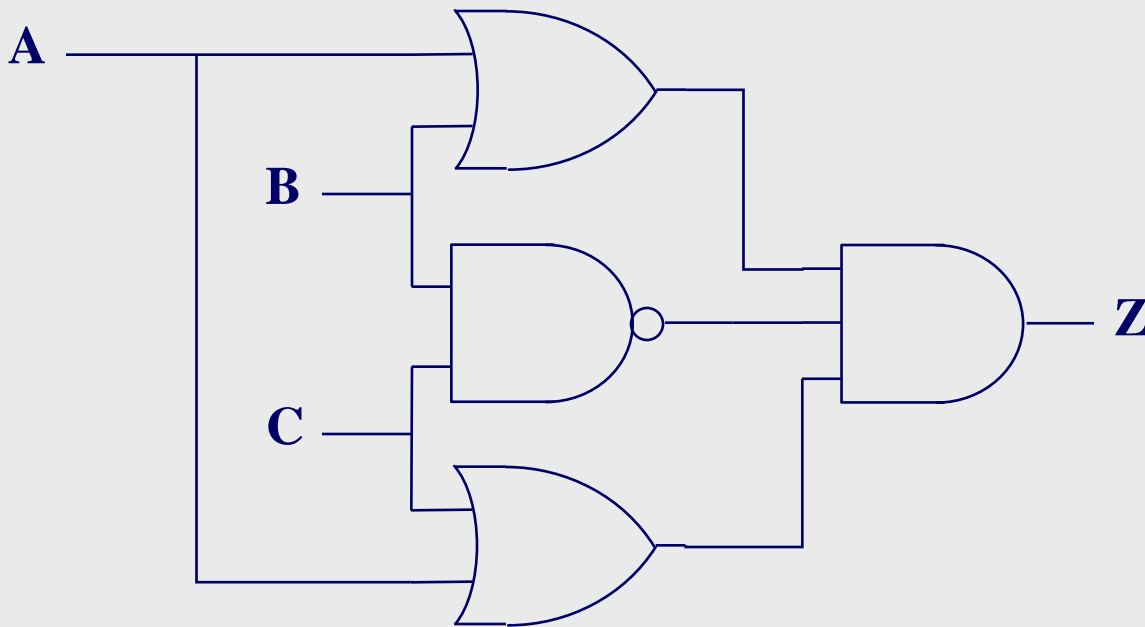

A	B	C	Z
0	0	0	?
0	0	1	?
0	1	0	?
0	1	1	?
1	0	0	?
1	0	1	?
1	1	0	?
1	1	1	?

Boolean Algebra


Example 8: Determine the truth table

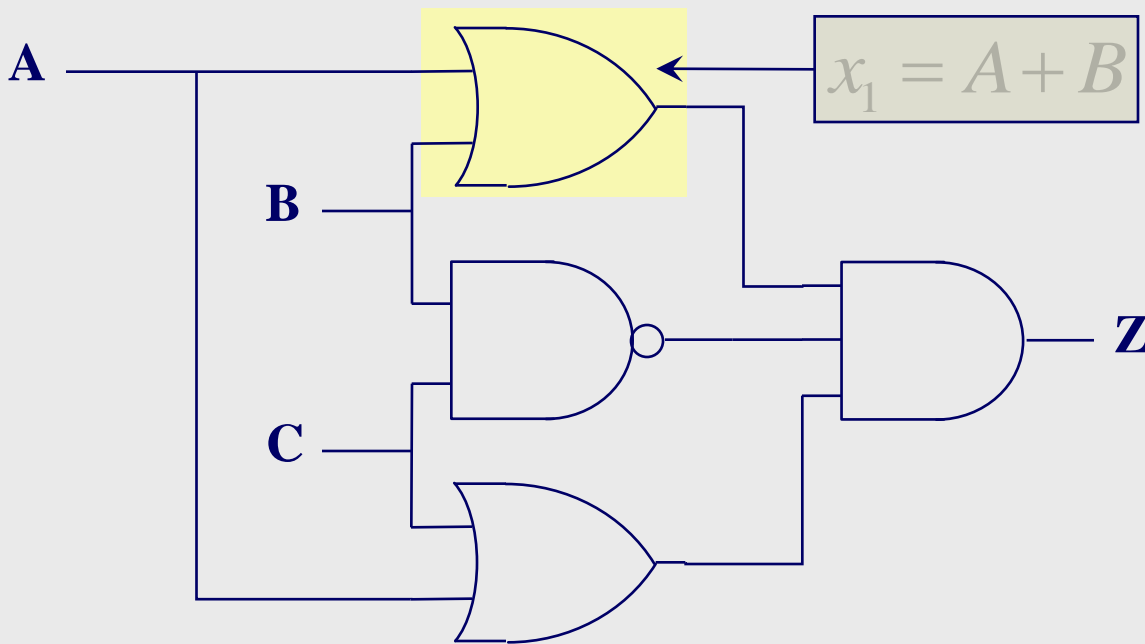

A	B	C	x_1	Z
0	0	0	0	?
0	0	1	0	?
0	1	0	1	?
0	1	1	1	?
1	0	0	1	?
1	0	1	1	?
1	1	0	1	?
1	1	1	1	?

Boolean Algebra


Example 8: Determine the truth table

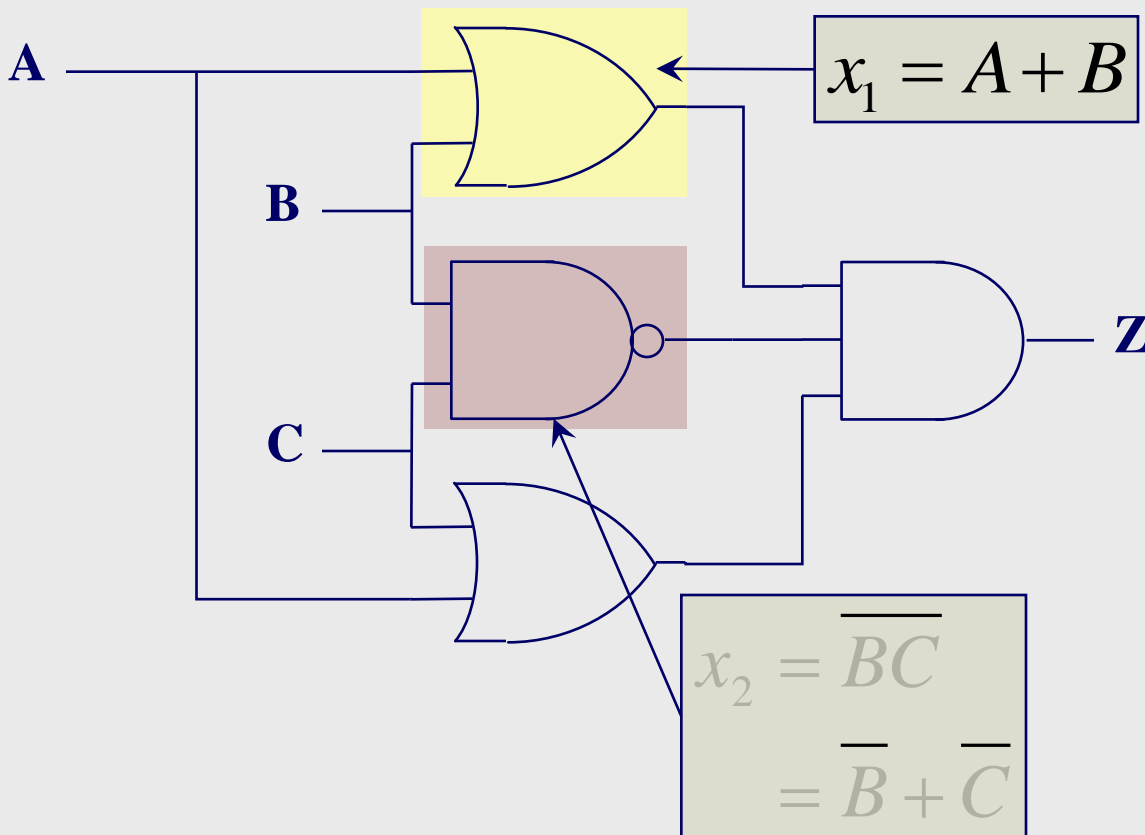

A	B	C	x_1	x_2	Z
0	0	0	0	1	?
0	0	1	0	1	?
0	1	0	1	1	?
0	1	1	1	0	?
1	0	0	1	1	?
1	0	1	1	1	?
1	1	0	1	1	?
1	1	1	1	0	?

Boolean Algebra

Example 8: Determine the truth table

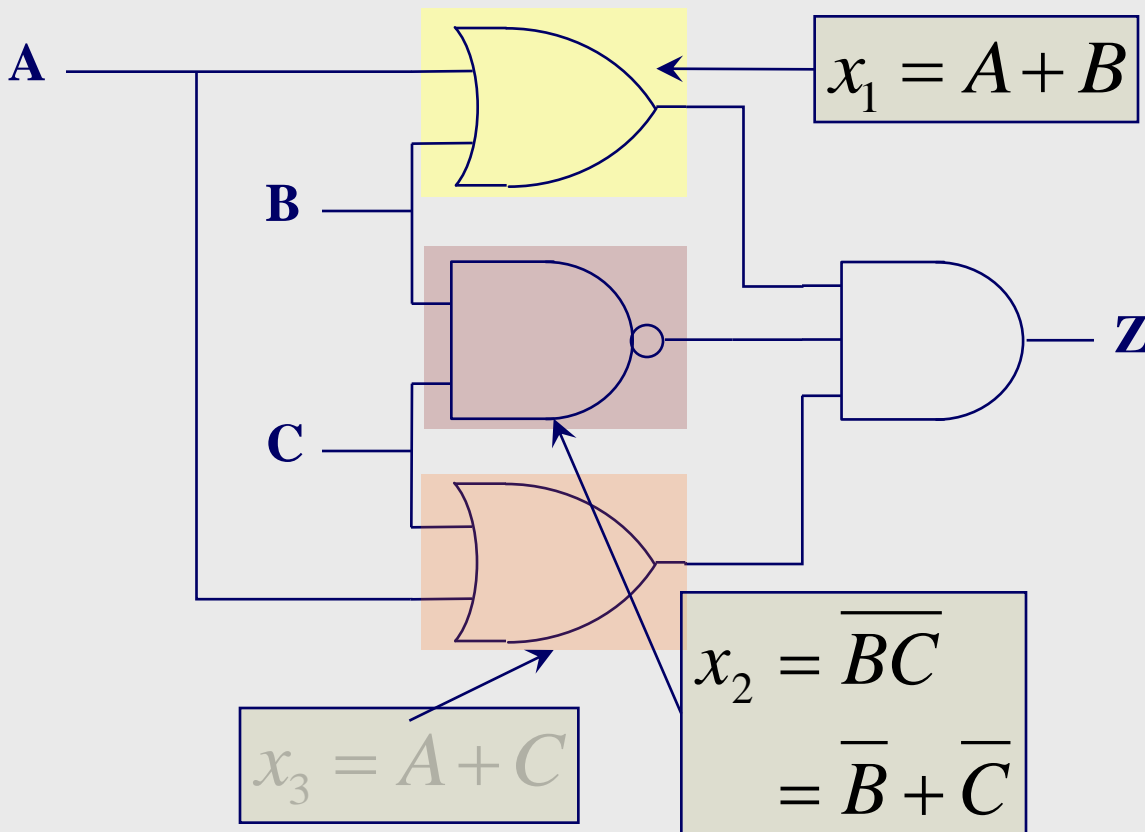


A	B	C	x_1	x_2	x_3	Z
0	0	0	0	1	0	?
0	0	1	0	1	1	?
0	1	0	1	1	0	?
0	1	1	1	0	1	?
1	0	0	1	1	1	?
1	0	1	1	1	1	?
1	1	0	1	1	1	?
1	1	1	1	0	1	?

Boolean Algebra

Example 8: Determine the truth table

A	B	C	x_1	x_2	x_3	Z
0	0	0	0	1	0	0
0	0	1	0	1	1	0
0	1	0	1	1	0	0
0	1	1	1	0	1	0
1	0	0	1	1	1	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	0	1	0

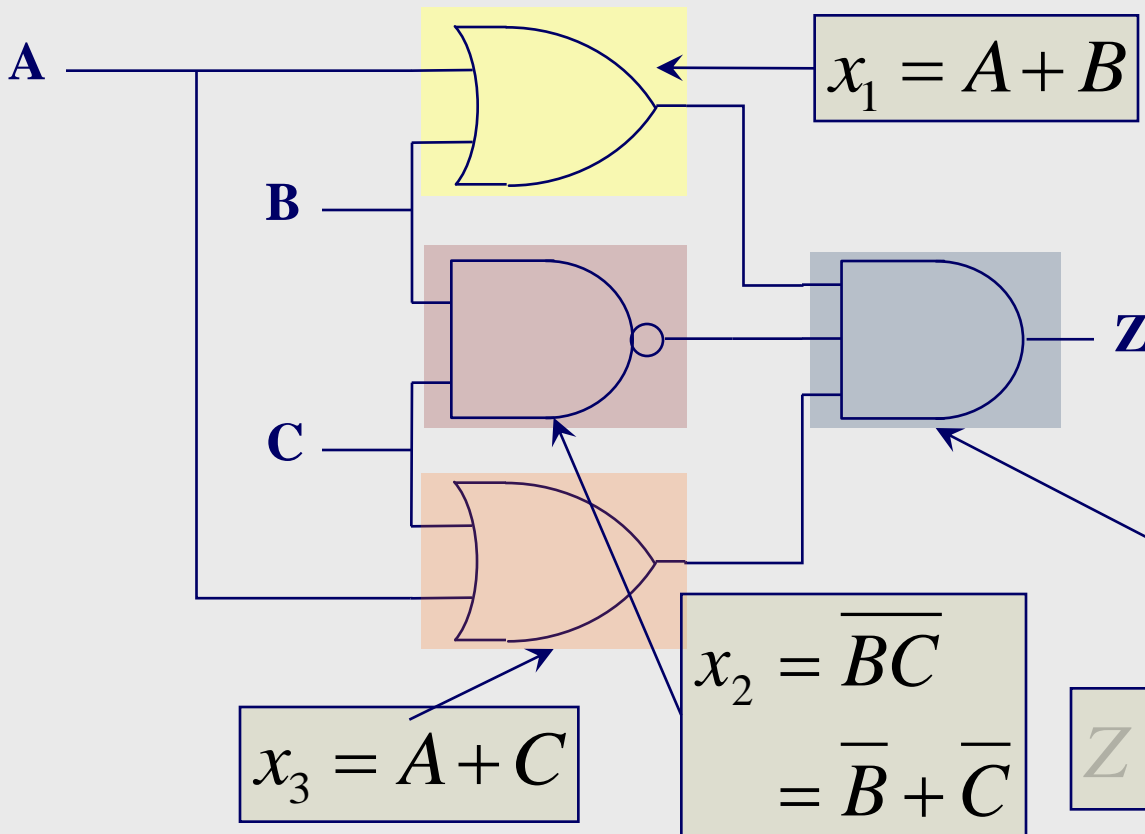

Boolean Algebra



Example 8: Determine the truth table

$$\begin{aligned}
 Z &= (A + B) \overline{BC} (A + C) \\
 &= \overline{A} \overline{B} \overline{C} + \overline{A} B \overline{C} + A \overline{B} \overline{C} \\
 &= A \overline{C} (\overline{B} + B) + \overline{A} \overline{B} \overline{C} \\
 &= A \overline{C} + \overline{A} \overline{B} \overline{C} \\
 &= A (\overline{C} + \overline{B} \overline{C}) \\
 &= A (\overline{C} + \overline{B})
 \end{aligned}$$

A	B	C	x ₁	x ₂	x ₃	Z
0	0	0	0	1	0	0
0	0	1	0	1	1	0
0	1	0	1	1	0	0
0	1	1	1	0	1	0
1	0	0	1	1	1	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	0	1	0


Combinational Logic – Decoders

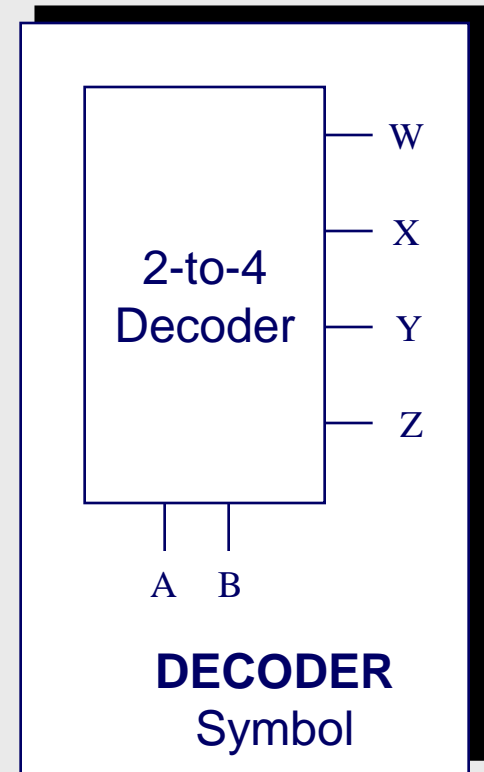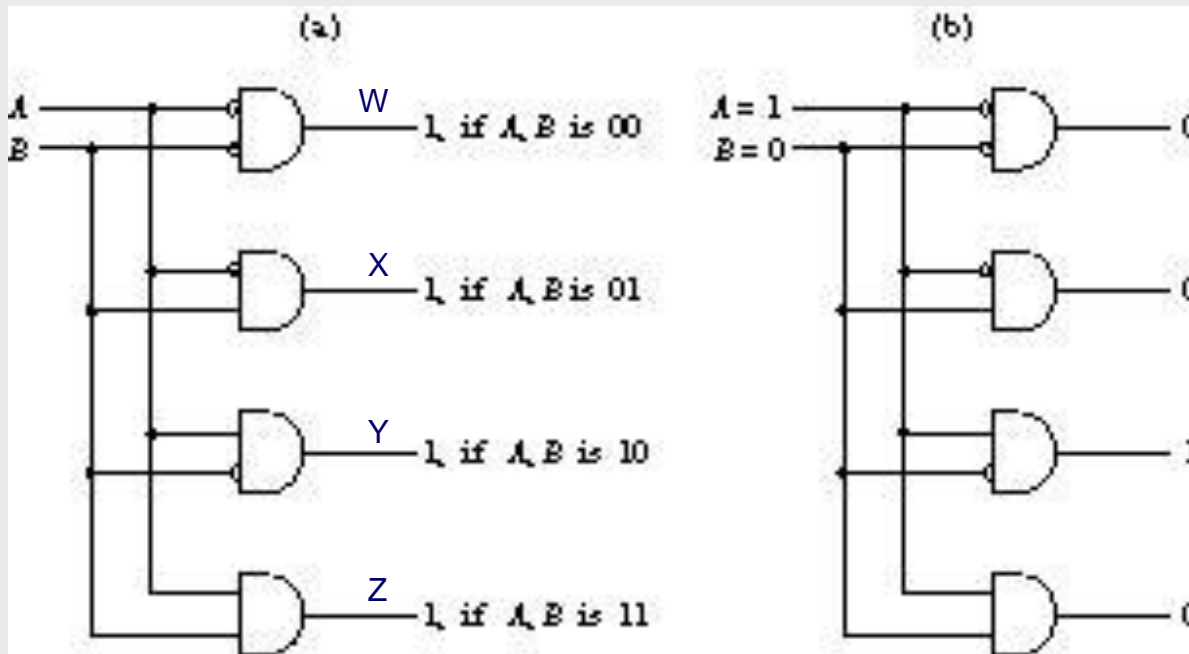- ◆ Decode the input and signify its value by raising **just one** of its outputs.
- ◆ A decoder with **n** inputs has **2^n** outputs



Combinational Logic – Decoders



◆ Write the truth table

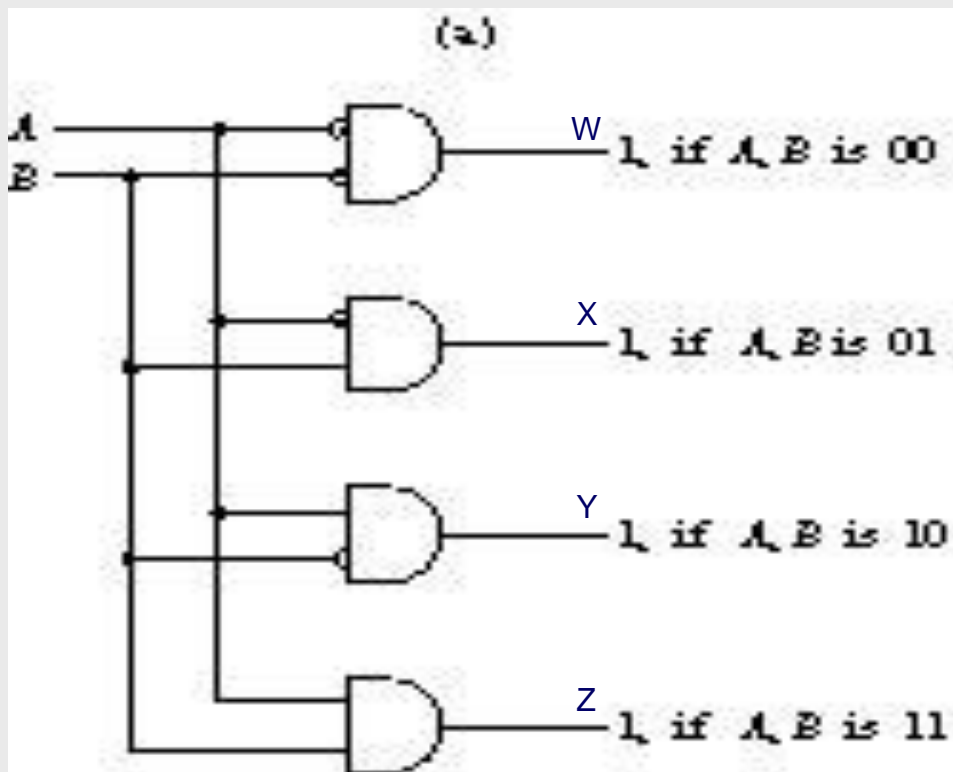

A	B	W	X	Y	Z
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Combinational Logic – Multiplexors

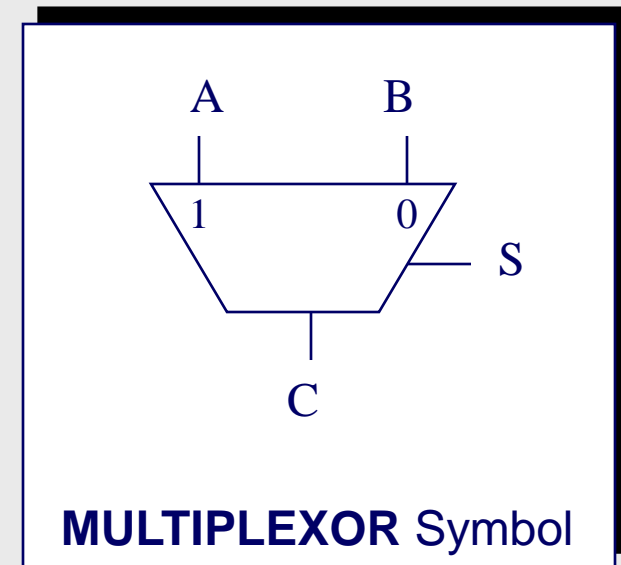 - ◆ Connect one of its inputs to its output according to select signals




- ◆ Useful for *selecting* one from a collection of data inputs.
- ◆ Usually has 2^n inputs and n select lines.

Combinational Logic – Multiplexors

◆ Write the truth table


A	B	S	C
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

Sequential Logic – SR Latch


SR Latch with additional inputs:

 - ▲ **Enable (E)** – S and R can only change Q when E is 1
- ▲ **Preset (PRE)** – regardless of S, R, or E, put Q to 1 when PRE is 1
- ▲ **Clear (CLR)** – regardless of S, R, E, or PRE, put Q to 0 when CLR is 1



Precedence:

 1. If CLR = 1, Q = 0
2. If PRE = 1, Q = 1
3. If E = 1, Q is set based on SR:
 - If S = 0 and R = 0, Q = held
 - If S = 0 and R = 1, Q = 0
 - If S = 1 and R = 0, Q = 1
 - If S = 1 and R = 1, Q = unstable
4. Else Q is held



SR can only change Q only in blue regions (where E = 1) BUT CLR and PRE will change Q ANYTIME


Sequential Logic – D Latch

D Latch has only 2 states:


- ▶ **Set** (set Q to 1): $D = 1$
- ▶ **Reset** (reset Q to 0): $D = 0$

D Latch with enable (E):

- ▶ Q can only change when $E = 1$

 


E	D	Q_{new}
0	0	Q_{old}
0	1	Q_{old}
1	0	0
1	1	1

 



D can only change Q only in blue regions (where $E = 1$)

Sequential Logic – D Flip-Flop

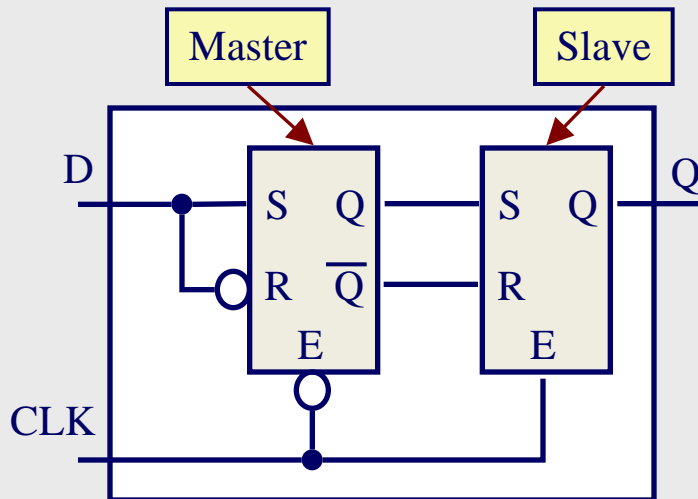D FF: 2 SR latches in master/slave configuration. The output (Q) changes on the **rising clock edge**



D	CLK	Q_{new}
0	↑	0
1	↑	1

  

D can only change Q only on rising clock edge (arrows)


Sequential Logic – JK Flip-Flop

JK FF: 2 SR latches in master/slave configuration.
The output (Q) changes on the **falling clock edge**

JK FF has 4 allowed states:

- ▲ **Present state** (keep Q as is): J = 0, K = 0
- ▲ **Reset** (reset Q to 0): J = 0, K = 1
- ▲ **Set** (set Q to 1): J = 1, K = 0
- ▲ **Toggle** (set Q to \bar{Q}): J = 1, K = 1

J	K	CLK	Q_{new}
0	0	↓	Q_{old}
0	1	↓	0
1	0	↓	1
1	1	↓	\bar{Q}_{old}

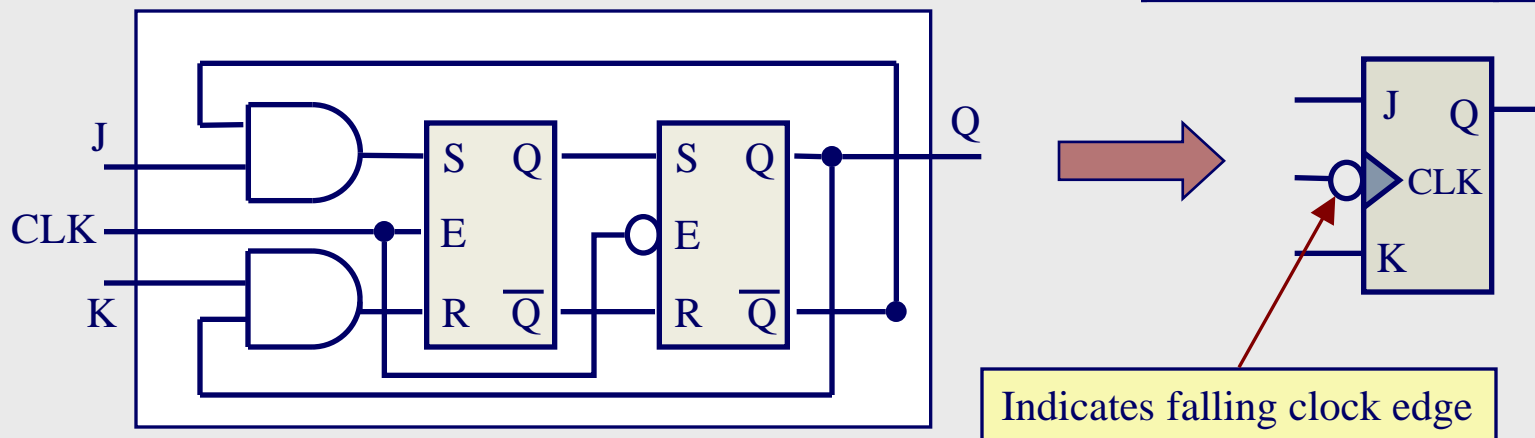


Sequential Logic – T Flip-Flop

T FF: JK FF with J and K inputs connected

T FF has 2 allowed states:

- ▶ **Present state** (keep Q as is): $T = 0$
- ▶ **Toggle** (set Q to \bar{Q}): $T = 1$


T	CLK	Q_{new}
0	↓	Q_{old}
1	↓	$\overline{Q_{\text{old}}}$

 


Sequential Logic – Digital Counters

Ripple counter: with N bits, cycles through the numbers from 0 to $2^N - 1$

 ▲ N JK FFs cascaded together to produce an N-bit up counter




NB: for 3-bit counter we need 3 FFs

 

Sequential Logic – Digital Counters


Synchronous counter: with N bits, cycles through the numbers from 0 to $2^N - 1$

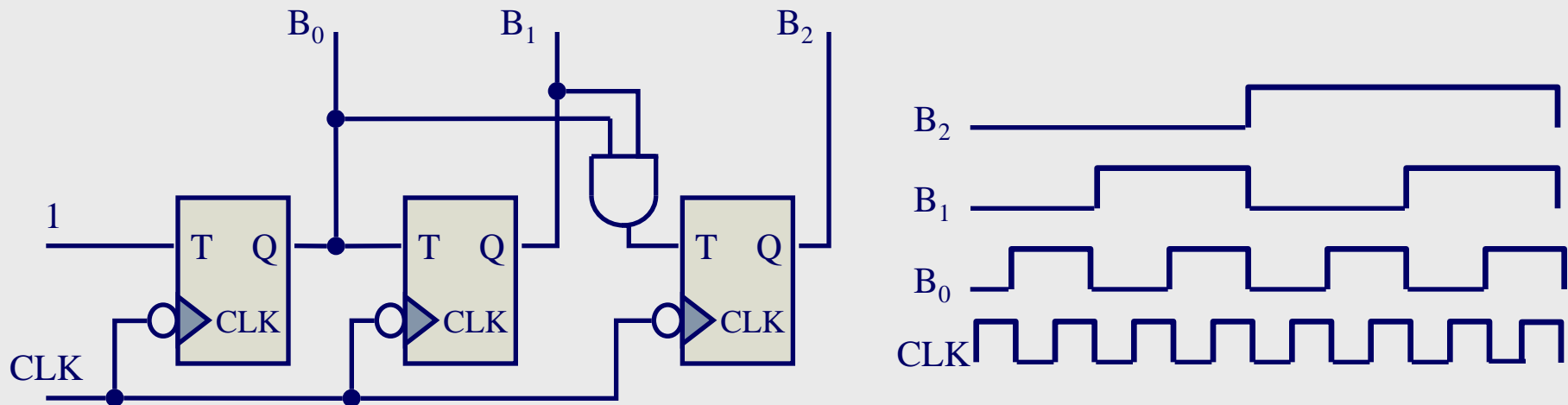▲ Input clock drives all FFs simultaneously



Sequential Logic

 
Example9: Assuming the outputs of the following circuit start in a 000 state, determine the outputs for 4 clock cycles



Sequential Logic

Example9: Assuming the outputs of the following circuit start in a 000 state, determine the outputs for 4 clock cycles

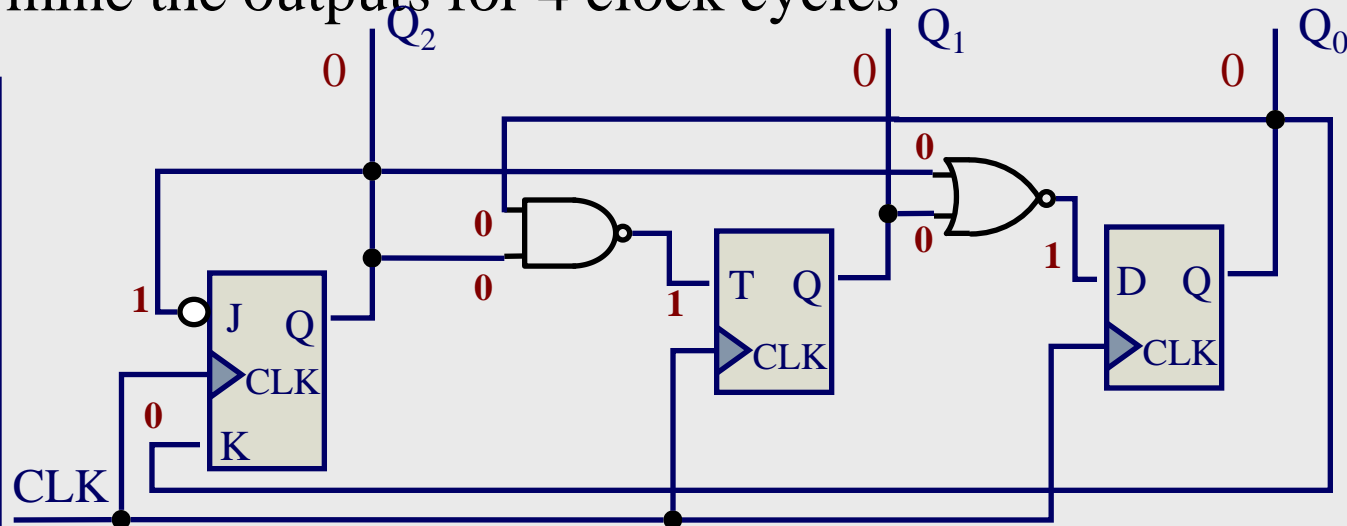1. Set outputs to 000
2. Based on output values change FF inputs
3. On each clock cycle:
 - a) change FF outputs based on inputs
 - b) Change FF inputs based on new outputs



J	K	CLK	Q_{new}
0	0	↑	Q_{old}
0	1	↑	0
1	0	↑	1
1	1	↑	$\overline{Q_{old}}$


T	CLK	Q_{new}
0	↑	Q_{old}
1	↑	$\overline{Q_{old}}$

D	CLK	Q_{new}
0	↑	0
1	↑	1

Sequential Logic

Example9: Assuming the outputs of the following circuit start in a 000 state, determine the outputs for 4 clock cycles

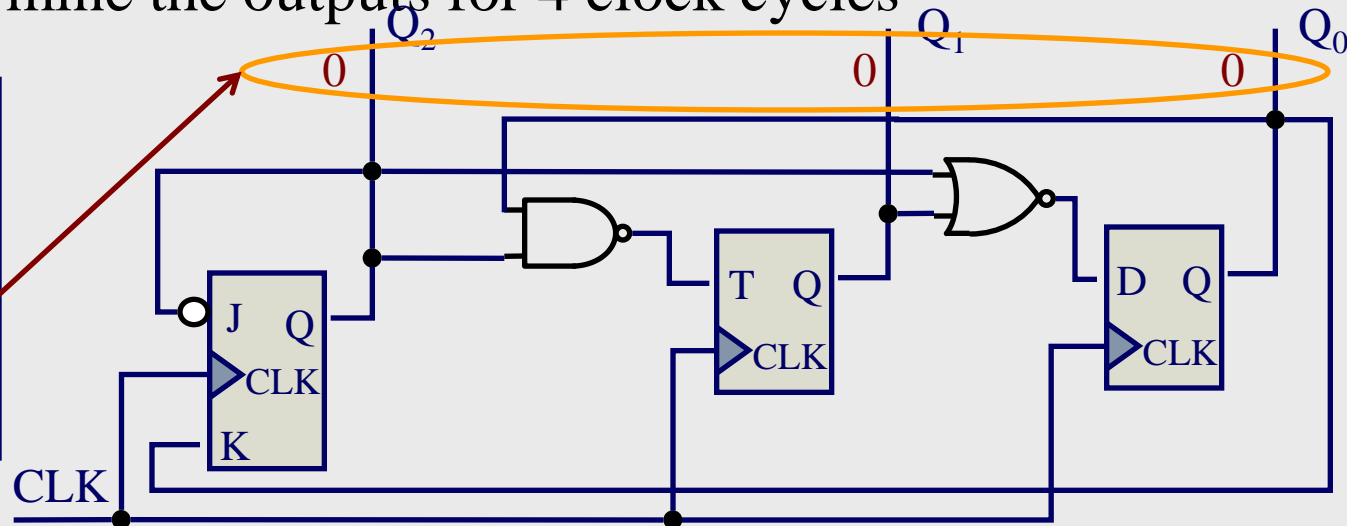1. Set outputs to 000
2. Based on output values change FF inputs
3. On each clock cycle:
 - a) change **ALL** FF outputs based on inputs



J	K	CLK	Q _{new}
0	0	↑	Q _{old}
0	1	↑	0
1	0	↑	1
1	1	↑	$\overline{Q_{old}}$


T	CLK	Q _{new}
0	↑	Q _{old}
1	↑	$\overline{Q_{old}}$

D	CLK	Q _{new}
0	↑	0
1	↑	1

Sequential Logic

Example 9: Assuming the outputs of the following circuit start in a 000 state, determine the outputs for 4 clock cycles

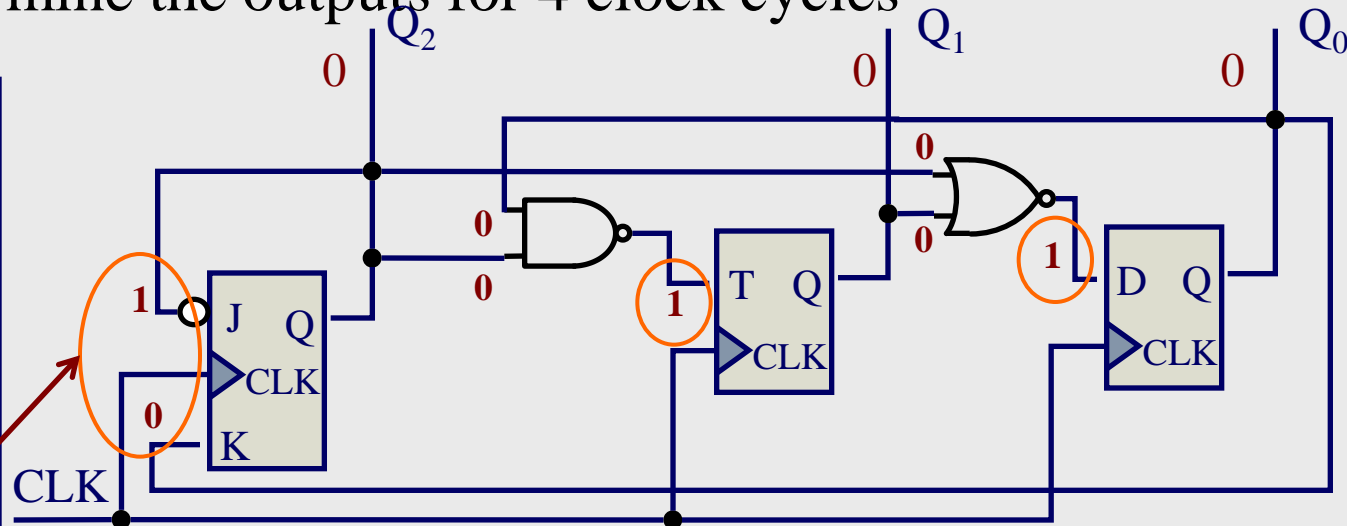1. Set outputs to 000
2. Based on output values change FF inputs
3. On each clock cycle:
 - a) change **ALL** FF outputs based on inputs
 - b) Change **ALL** FF inputs based on new outputs



J	K	CLK	Q _{new}
0	0	↑	Q _{old}
0	1	↑	0
1	0	↑	1
1	1	↑	$\overline{Q_{old}}$


T	CLK	Q _{new}
0	↑	Q _{old}
1	↑	$\overline{Q_{old}}$

D	CLK	Q _{new}
0	↑	0
1	↑	1

Sequential Logic

Example 9: Assuming the outputs of the following circuit start in a 000 state, determine the outputs for 4 clock cycles

Cycle	Q_2	Q_1	Q_0
start	0	0	0

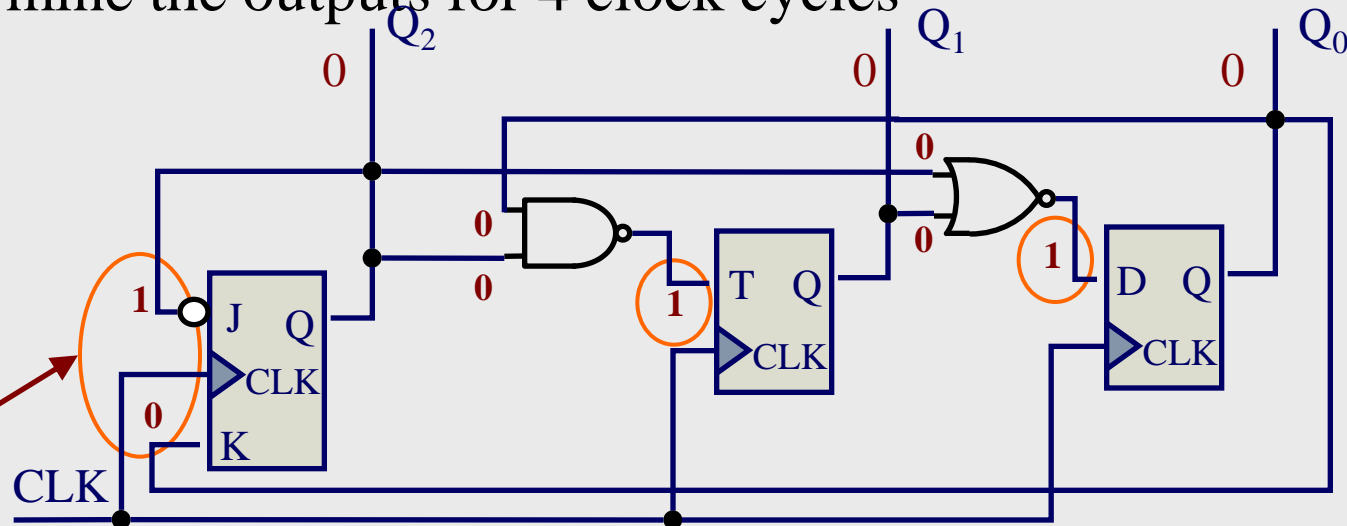

J	K	CLK	Q_{new}
0	0	↑	Q_{old}
0	1	↑	0
1	0	↑	1
1	1	↑	$\overline{Q_{old}}$

T	CLK	Q_{new}
0	↑	Q_{old}
1	↑	$\overline{Q_{old}}$


D	CLK	Q_{new}
0	↑	0
1	↑	1

Sequential Logic

Example9: Assuming the outputs of the following circuit start in a 000 state, determine the outputs for 4 clock cycles

Cycle	Q_2	Q_1	Q_0
start	0	0	0
1	0	1	1

Outputs change on new clock cycle

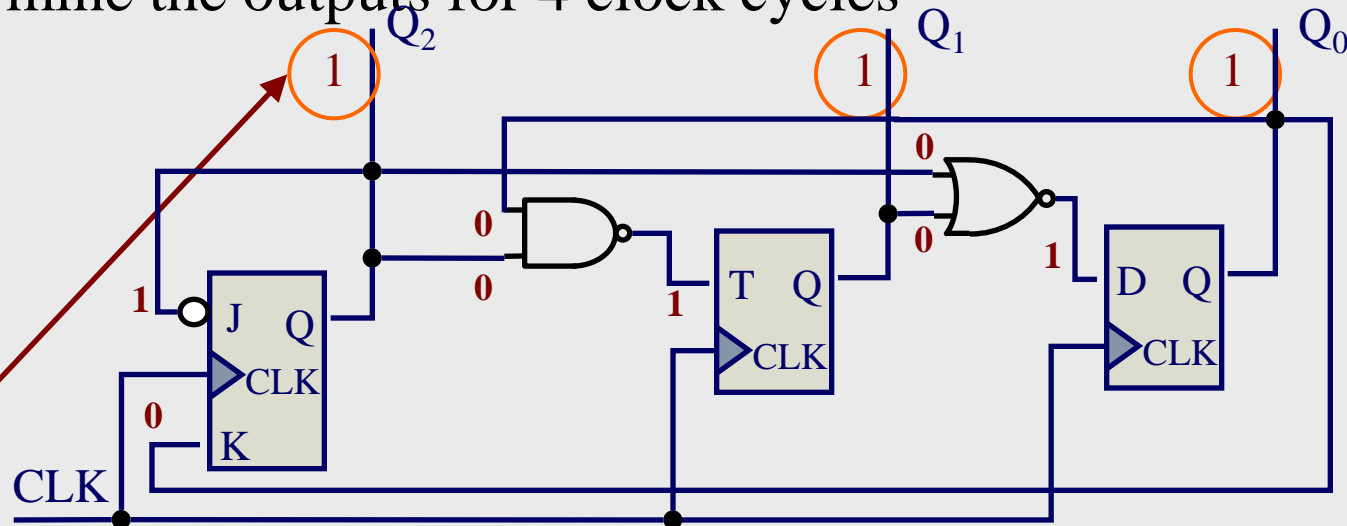

J	K	CLK	Q_{new}
0	0	↑	Q_{old}
0	1	↑	0
1	0	↑	1
1	1	↑	$\overline{Q_{old}}$


T	CLK	Q_{new}
0	↑	Q_{old}
1	↑	$\overline{Q_{old}}$

D	CLK	Q_{new}
0	↑	0
1	↑	1

Sequential Logic

Example9: Assuming the outputs of the following circuit start in a 000 state, determine the outputs for 4 clock cycles

Cycle	Q_2	Q_1	Q_0
start	0	0	0
1	1	1	1

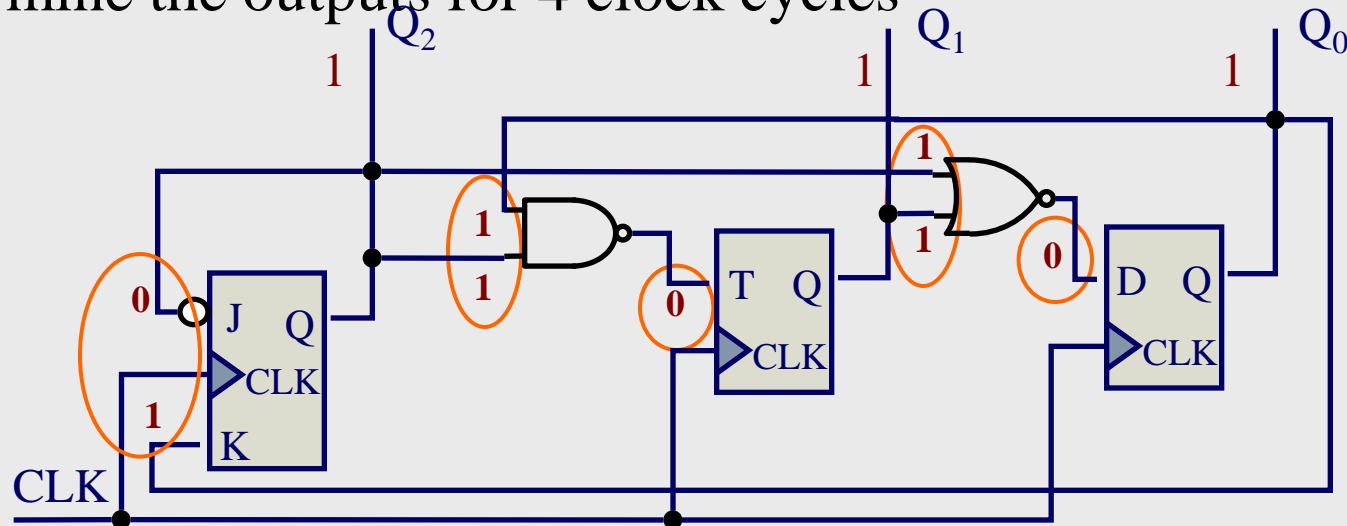

Inputs changed due to outputs

J	K	CLK	Q_{new}
0	0	↑	Q_{old}
0	1	↑	0
1	0	↑	1
1	1	↑	$\overline{Q_{old}}$


T	CLK	Q_{new}
0	↑	Q_{old}
1	↑	$\overline{Q_{old}}$

D	CLK	Q_{new}
0	↑	0
1	↑	1

Sequential Logic

Example 9: Assuming the outputs of the following circuit start in a 000 state, determine the outputs for 4 clock cycles

Cycle	Q_2	Q_1	Q_0
start	0	0	0
1	0	1	1
2	0	1	0

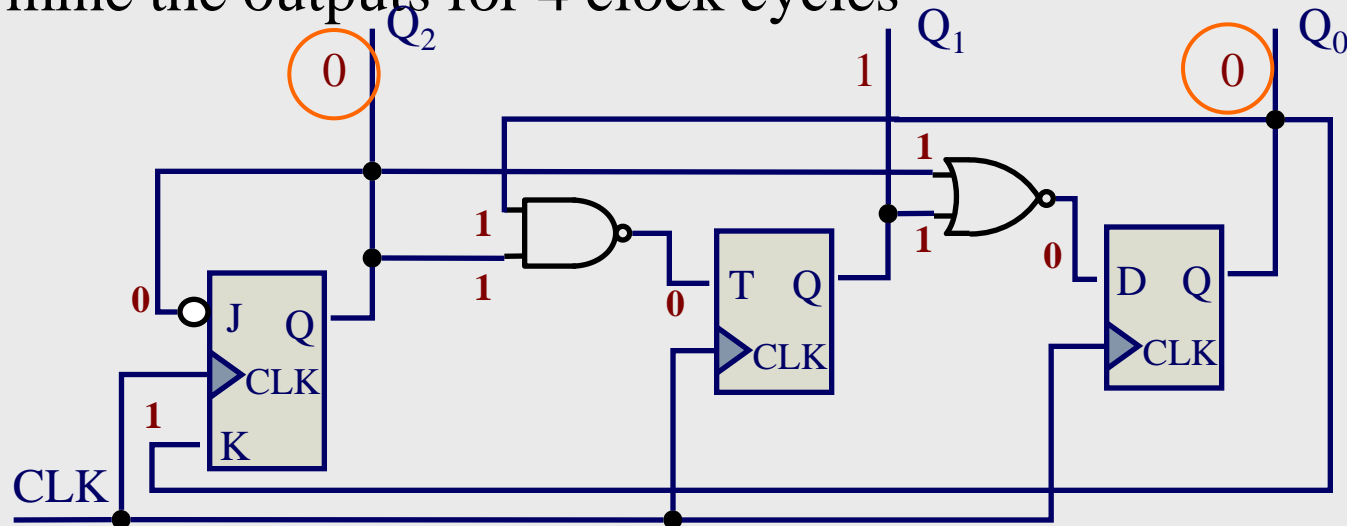

Outputs change on new clock cycle

J	K	CLK	Q_{new}
0	0	↑	Q_{old}
0	1	↑	0
1	0	↑	1
1	1	↑	$\overline{Q_{old}}$


T	CLK	Q_{new}
0	↑	Q_{old}
1	↑	$\overline{Q_{old}}$

D	CLK	Q_{new}
0	↑	0
1	↑	1

Sequential Logic

Example 9: Assuming the outputs of the following circuit start in a 000 state, determine the outputs for 4 clock cycles

Cycle	Q_2	Q_1	Q_0
start	0	0	0
1	0	1	1
2	0	1	0

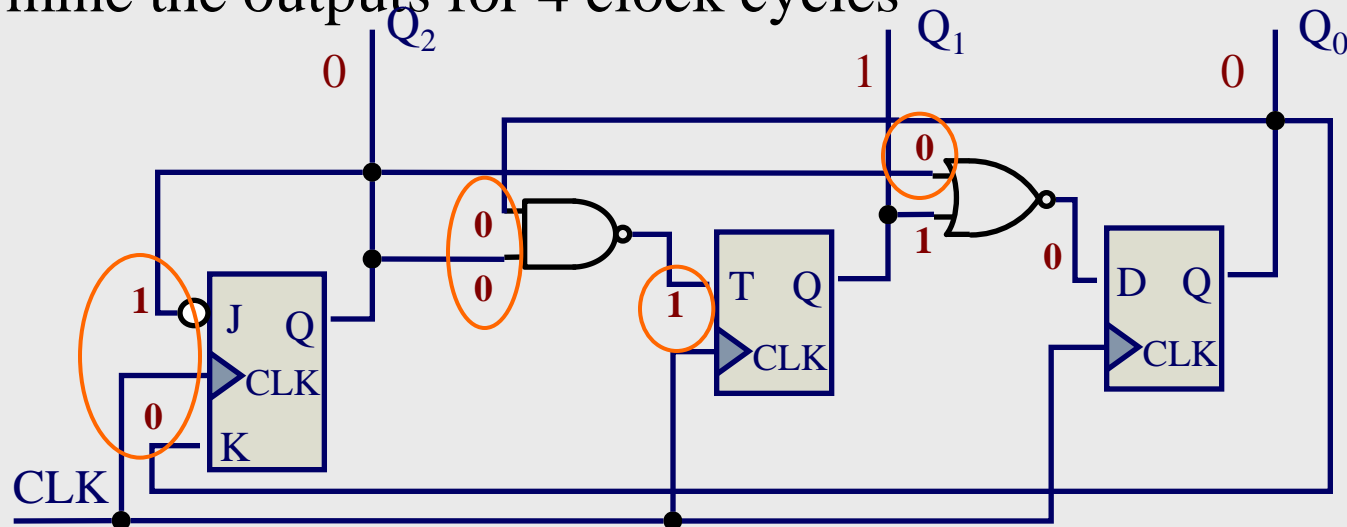

Inputs changed due to outputs

J	K	CLK	Q_{new}
0	0	↑	Q_{old}
0	1	↑	0
1	0	↑	1
1	1	↑	$\overline{Q_{old}}$


T	CLK	Q_{new}
0	↑	Q_{old}
1	↑	$\overline{Q_{old}}$

D	CLK	Q_{new}
0	↑	0
1	↑	1

Sequential Logic

Example 9: Assuming the outputs of the following circuit start in a 000 state, determine the outputs for 4 clock cycles

Cycle	Q_2	Q_1	Q_0
start	0	0	0
1	0	1	1
2	0	1	0
3	1	0	0

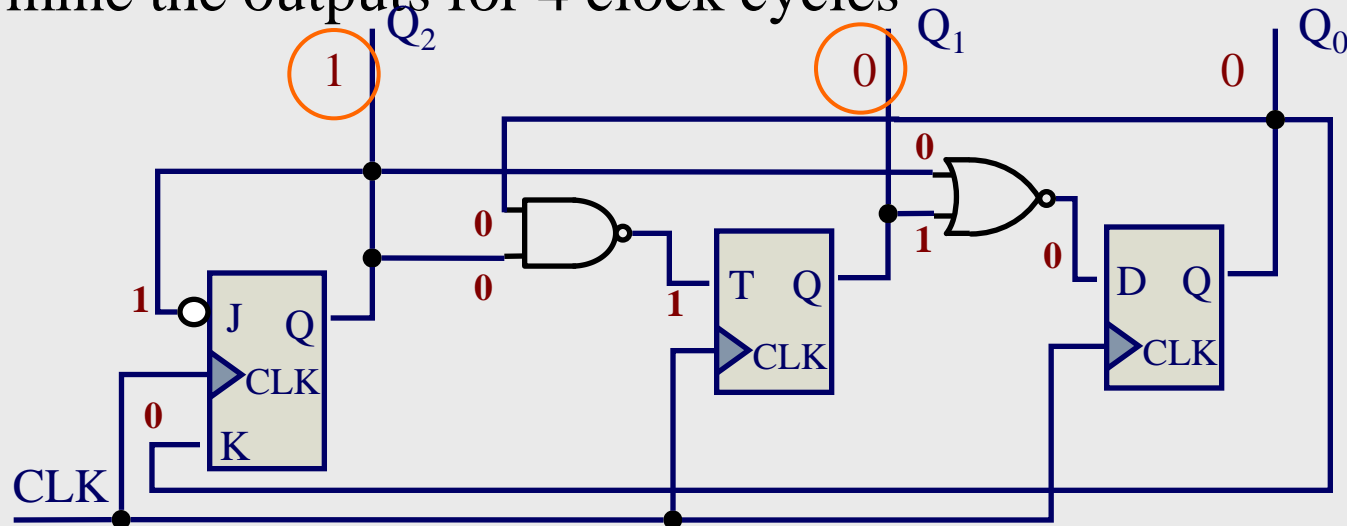

Outputs change on new clock cycle

J	K	CLK	Q_{new}
0	0	↑	Q_{old}
0	1	↑	0
1	0	↑	1
1	1	↑	$\overline{Q_{old}}$


T	CLK	Q_{new}
0	↑	Q_{old}
1	↑	$\overline{Q_{old}}$

D	CLK	Q_{new}
0	↑	0
1	↑	1

Sequential Logic

Example9: Assuming the outputs of the following circuit start in a 000 state, determine the outputs for 4 clock cycles

Cycle	Q_2	Q_1	Q_0
start	0	0	0
1	0	1	1
2	0	1	0
3	1	0	0

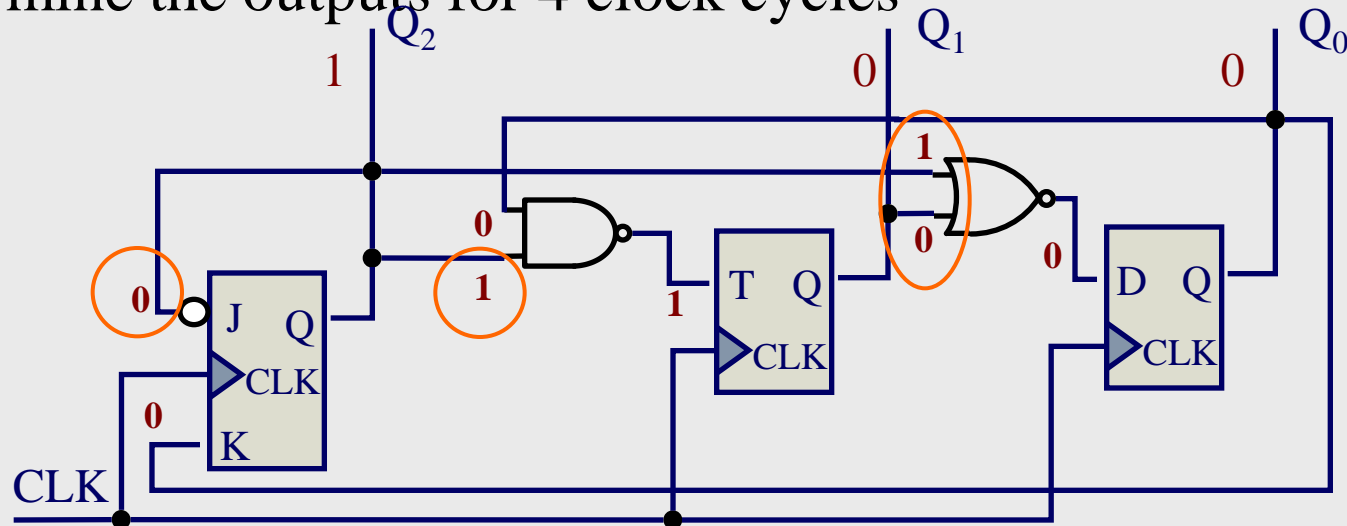

Inputs changed due to outputs

J	K	CLK	Q_{new}
0	0	↑	Q_{old}
0	1	↑	0
1	0	↑	1
1	1	↑	$\overline{Q_{old}}$


T	CLK	Q_{new}
0	↑	Q_{old}
1	↑	$\overline{Q_{old}}$

D	CLK	Q_{new}
0	↑	0
1	↑	1

Sequential Logic

Example 9: Assuming the outputs of the following circuit start in a 000 state, determine the outputs for 4 clock cycles

Cycle	Q_2	Q_1	Q_0
start	0	0	0
1	0	1	1
2	0	1	0
3	1	0	0
4	1	1	0

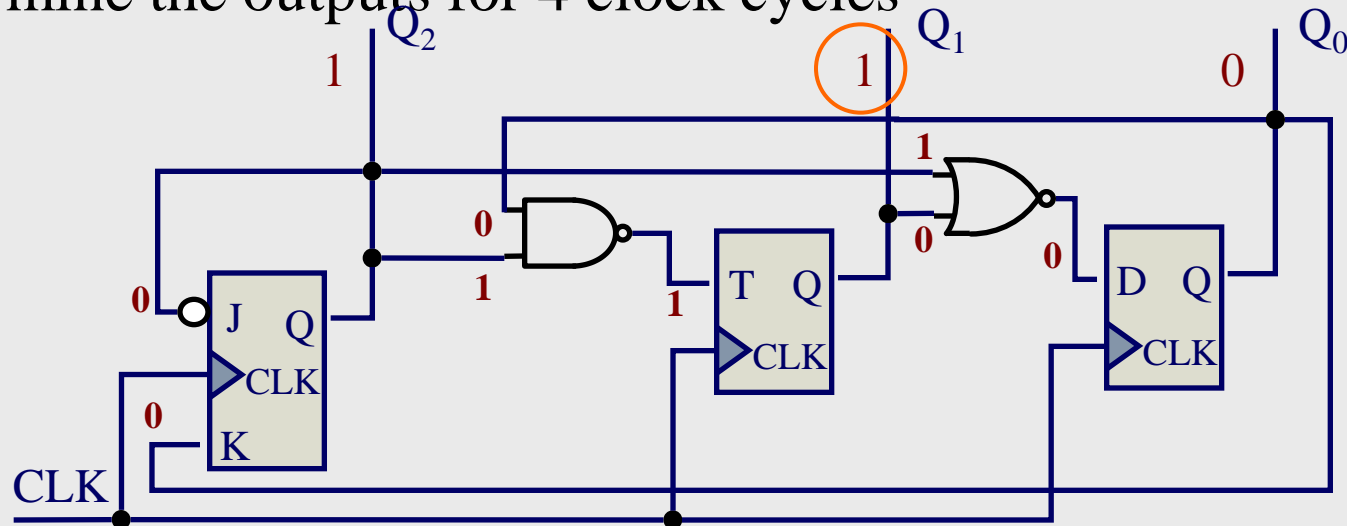

Outputs change on new clock cycle

J	K	CLK	Q_{new}
0	0	↑	Q_{old}
0	1	↑	0
1	0	↑	1
1	1	↑	$\overline{Q_{old}}$

T	CLK	Q_{new}
0	↑	Q_{old}
1	↑	$\overline{Q_{old}}$

D	CLK	Q_{new}
0	↑	0
1	↑	1

Digital to Analog Converter (DAC)

DAC: converts an **unsigned binary word** to an analog output voltage or current

Resolution δv : minimum step size by which the output voltage (or current) can increment

Output voltage v_a : the analog value represented by the binary word B

•EX: let $n=4$

$$v_a = (2^3 \cdot b_3 + 2^2 \cdot b_2 + 2^1 \cdot b_1 + 2^0 \cdot b_0) \delta v$$

Max output voltage v_{aMax} : the maximum analog value


•EX: let $n=4$

$$\begin{aligned} v_{aMax} &= (2^3 + 2^2 + 2^1 + 2^0) \delta v \\ &= (2^n - 1) \delta v \end{aligned}$$



Digital to Analog Converter (DAC)

Building a DAC:

use a summing amplifier

 

Summing amplifier

  


DAC

Digital to Analog Converter (DAC)

Building a DAC:

 the analog output (v_a) is proportional to the binary word **B**



$$v_a = - \sum_{i=0}^{n-1} \frac{R_F}{R_i} \cdot b_i \cdot v_{in}$$

Choose

$$R_i = \frac{R_0}{2^i}$$

v_{si} in summing amplifier


THUS

$$v_a = - \frac{R_F}{R_0} \cdot v_{in} \sum_{i=0}^{n-1} 2^i \cdot b_i$$

Digital to Analog Converter (DAC)

Example 10: find the smallest resolution δv of an 8-bit DAC


$$V_{a\text{Max}} = 12\text{V}$$

 

Digital to Analog Converter (DAC)

Example 10: find the smallest resolution δv of an 8-bit DAC

$$V_{a\text{Max}} = 12\text{V}$$

 

$$\begin{aligned} v_{a\text{max}} &= (2^n - 1) \delta v \\ \delta v &= \frac{v_{a\text{max}} - v_{a\text{min}}}{(2^n - 1)} \\ &= \frac{12 - 0}{(2^8 - 1)} \\ &= 47.1 \text{ mV} \end{aligned}$$

Digital to Analog Converter (DAC)


Example11: find the resistor values for a DAC with:

$$\text{range} = 15\text{V}$$

$$\delta v = 1\text{V}$$

$$v_{\text{in}} = 5\text{V}$$

$$R_F = 2\text{k}\Omega$$

 

Digital to Analog Converter (DAC)


Example11: find the resistor values for a DAC with:

range = 15V

$\delta v = 1V$

$v_{in} = 5V$

$R_F = 2k\Omega$

 

$$\begin{aligned} n &= \left\lceil \frac{\log \left(\frac{v_{a \max} - v_{a \min}}{\delta v} + 1 \right)}{\log 2} \right\rceil \\ &= \left\lceil \frac{\log (5 / 1 + 1)}{\log 2} \right\rceil \\ &= \lceil 4 \rceil \\ &= 4 \end{aligned}$$

Digital to Analog Converter (DAC)


Example11: find the resistor values for a DAC with:

range = 15V

$\delta v = 1V$

$v_{in} = 5V$

$R_F = 2k\Omega$

 

$$v_a = -\frac{R_F}{R_0} \cdot v_{in} \sum_{i=0}^{n-1} 2^i \cdot b_i$$

$$v_{a \max} = \frac{R_F}{R_0} \cdot v_{in} (2^n - 1)$$

$$R_0 = \frac{R_F}{v_{a \max}} \cdot v_{in} (2^n - 1)$$

$$= \frac{2 \times 10^3}{15} (2^4 - 1)$$

$$= 10 \text{ k}\Omega$$

Digital to Analog Converter (DAC)


Example11: find the resistor values for a DAC with:

range = 15V

$\delta v = 1V$

$v_{in} = 5V$

$R_F = 2k\Omega$

 

$$R_i = \frac{R_0}{2^i}$$

$$\begin{aligned} R_1 &= \frac{R_0}{2^1} \\ &= \frac{10^3}{2} \\ &= 5k\Omega \end{aligned}$$

$$\begin{aligned} R_2 &= \frac{R_0}{2^2} \\ &= \frac{10^3}{4} \\ &= 2.5k\Omega \end{aligned}$$

$$\begin{aligned} R_3 &= \frac{R_0}{2^3} \\ &= \frac{10^3}{8} \\ &= 1.25k\Omega \end{aligned}$$