

Schedule...

Date	Day	Class No.	Title	Chapters	HW Due date	Lab Due date	Exam
22 Sept	Mon	6	Things Practical	2.6 – 2.8		LAB 2	
23 Sept	Tue						
24 Sept	Wed	7	Network Analysis	3.1 – 3.3			
25 Sept	Thu						
26 Sept	Fri		Recitation		HW 3		
27 Sept	Sat						
28 Sept	Sun						
29 Sept	Mon	8	Equivalent Circuits	3.4 – 3.5		LAB 3	
30 Sept	Tue						

Spiritual – Temporal

1 Nephi 15:32

32 And it came to pass that I said unto them that it was a representation of things both **temporal** and **spiritual**; for the day should come that they must be judged of their works, yea, even the works which were done by the temporal body in their days of probation.

Mosiah 2:41



41 And moreover, I would desire that ye should consider on the blessed and happy state of those that keep the commandments of God. For behold, they are blessed in all things, both **temporal** and **spiritual**; and if they hold out faithful to the end they are received into heaven, that thereby they may dwell with God in a state of never-ending happiness. O remember, remember that these things are true; for the Lord God hath spoken it.

Lecture 6 – The Wheatstone Bridge

An Applications of Things Electrical


Wheatstone Bridge

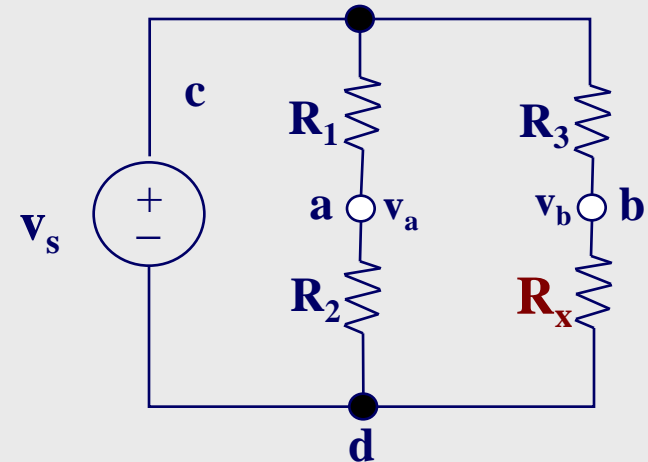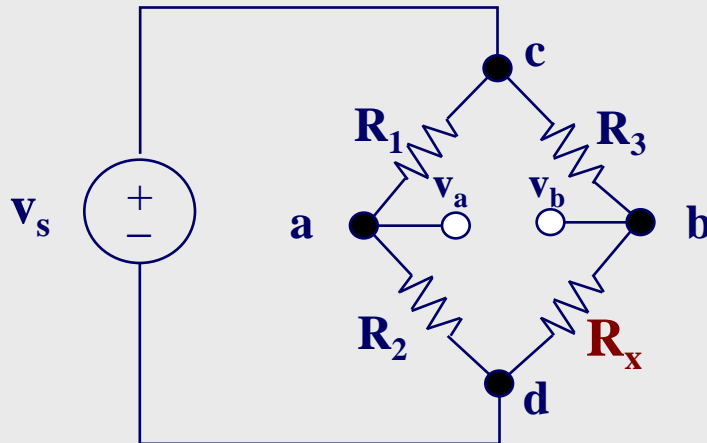◆ R_x is an unknown resistance to be determined



Wheatstone Bridge

- ◆ The circuit consists of the parallel combination of 3 subcircuits with the same voltage:
 - a) The voltage source
 - b) Series combination of $\mathbf{R_1}$ and $\mathbf{R_2}$
 - c) Series combination of $\mathbf{R_3}$ and $\mathbf{R_x}$
- ◆ Voltage divider between:
 - a) $\mathbf{R_1}$ and $\mathbf{R_2}$
 - $\mathbf{v_2 = v_{ad}}$
 - b) $\mathbf{R_3}$ and $\mathbf{R_x}$
 - $\mathbf{v_x = v_{bd}}$

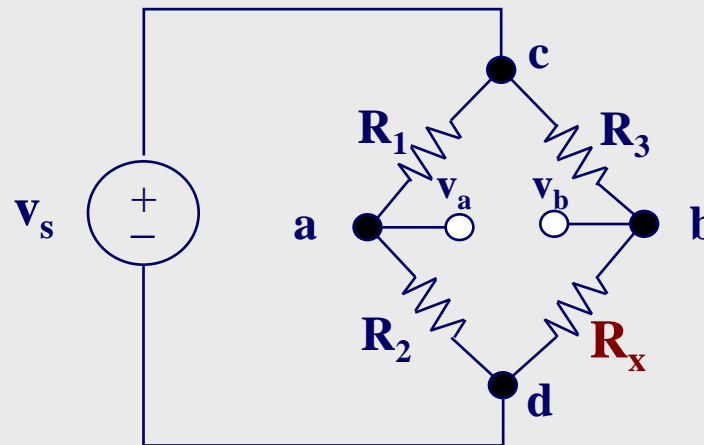


$$v_{ad} = v_s \frac{R_2}{R_1 + R_2}$$

$$v_{bd} = v_s \frac{R_x}{R_3 + R_x}$$

Wheatstone Bridge


- ◆ KVL around the bottom loop:
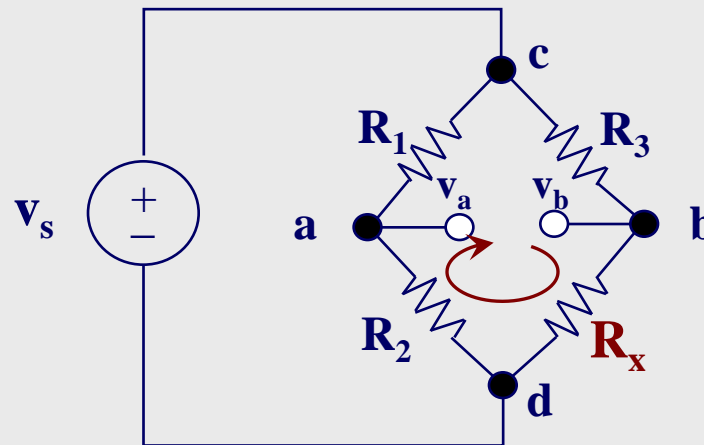
$$\begin{aligned} v_{ab} &= v_{ad} - v_{bd} \\ &= v_s \left(\frac{R_2}{R_1 + R_2} - \frac{R_x}{R_3 + R_x} \right) \end{aligned}$$




Wheatstone Bridge

◆ **Example1**: when is $v_{ab} = 0$?

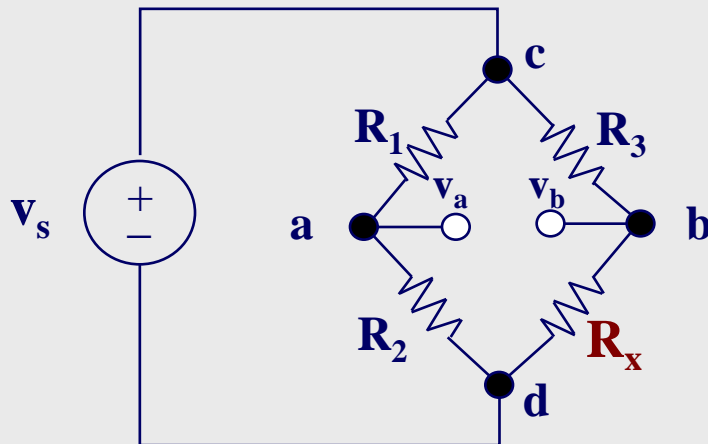

Wheatstone Bridge


◆ Example 1: when is $v_{ab} = 0$?

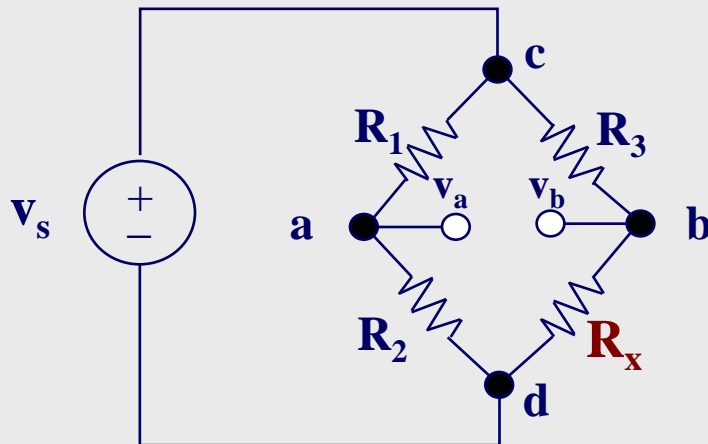

$$v_{ab} = v_s \left(\frac{R_2}{R_1 + R_2} - \frac{R_x}{R_3 + R_x} \right)$$
$$v_s \left(\frac{R_2}{R_1 + R_2} - \frac{R_x}{R_3 + R_x} \right) = 0$$
$$\frac{R_2}{R_1 + R_2} = \frac{R_x}{R_3 + R_x}$$
$$R_2 \cdot (R_3 + R_x) = R_x \cdot (R_1 + R_2)$$
$$R_2 R_3 + R_2 R_x = R_x R_1 + R_2 R_x$$
$$R_2 R_3 = R_x R_1$$

Wheatstone Bridge

◆ Find R_x :

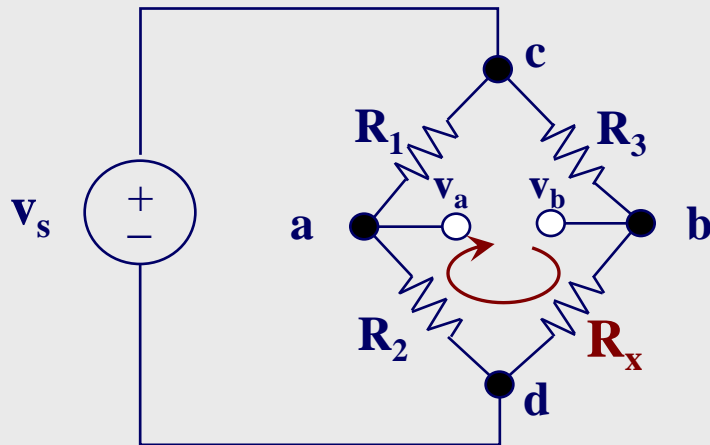


$$v_{ab} = v_s \left(\frac{R_2}{R_1 + R_2} - \frac{R_x}{R_3 + R_x} \right)$$
$$\vdots$$
$$R_x = \frac{R_3 \left(\frac{R_2}{R_1 + R_2} - \frac{v_{ab}}{v_s} \right)}{\left(1 - \frac{R_2}{R_1 + R_2} + \frac{v_{ab}}{v_s} \right)}$$

Wheatstone Bridge

◆ **Example2:** find R_x

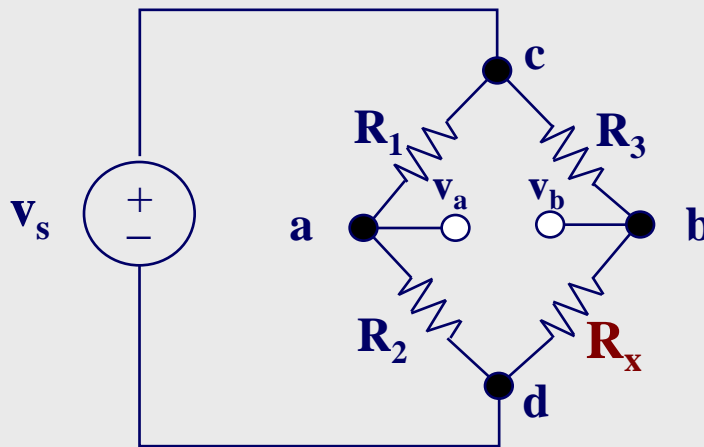▲ $R_1 = R_2 = R_3 = 1\text{k}\Omega$, $v_s = 12\text{V}$, $v_{ab} = 12\text{mV}$




$$R_x = \frac{R_3 \left(\frac{R_2}{R_1 + R_2} - \frac{v_{ab}}{v_s} \right)}{\left(1 - \frac{R_2}{R_1 + R_2} + \frac{v_{ab}}{v_s} \right)}$$

Wheatstone Bridge

◆ **Example2:** find R_x

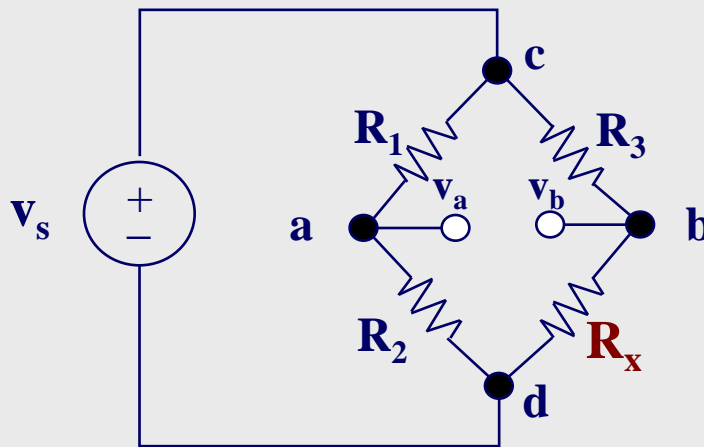▲ $R_1 = R_2 = R_3 = 1\text{k}\Omega$, $v_s = 12\text{V}$, $v_{ab} = 12\text{mV}$



$$\begin{aligned}
 R_x &= \frac{R_3 \left(\frac{R_2}{R_1 + R_2} - \frac{v_{ab}}{v_s} \right)}{\left(1 - \frac{R_2}{R_1 + R_2} + \frac{v_{ab}}{v_s} \right)} \\
 &= \frac{10^3 \left(\frac{10^3}{2 \times 10^3} - \frac{12 \times 10^{-3}}{12} \right)}{\left(1 - \frac{10^3}{2 \times 10^3} - \frac{12 \times 10^{-3}}{12} \right)} \\
 &= \frac{10^3 \left(\frac{1}{2} - 10^{-3} \right)}{\left(1 - \frac{1}{2} - 10^{-3} \right)} \\
 &= \frac{499}{0.501} \\
 &= 996\Omega
 \end{aligned}$$

Resistance Strain Gauges

◆ **Strain gauge**: device bonded to the surface of an object and whose resistance varies as a function of surface strain

▲ Used to perform measurements of:

- Strain
- Stress,
- Force
- Torque
- Pressure

◆ **NB**: cylindrical resistance: $R = \frac{L}{\sigma A}$

L – length of cylindrical resistor
 σ – conductivity of the resistor
 A – resistor cross-sectional area

▲ Compression/elongation will change resistance

Compression → lower resistance

Stretch → higher resistance

Resistance Strain Gauges

- ◆ **Gauge factor (GF)**: the relationship between change in resistance and change in length

- ▲ value of about 2 is common

$$GF = \frac{\Delta R / R_0}{\Delta L / L}$$

R_0 – the zero strain resistance

- ◆ **Strain (ϵ)**: the fractional change in length of an object

- ▲ Max strain that can be measured is about 0.4 – 0.5 percent


- i.e. $\epsilon = 0.004$ to 0.005
- For a **120 Ω** resistor: **+/- 1.2 Ω**

$$\epsilon = \frac{\Delta L}{L}$$

Resistance Strain Gauges

◆ Change in resistance due to strain:

$$\Delta R = R_0 GF \varepsilon$$

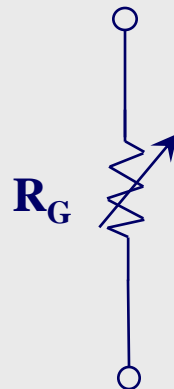



Circuit symbol for a strain gauge

Wheatstone Bridge

◆ Wheatstone bridge commonly used to measure force using strain gauge resistors

▲ **Example:** force applied to a cantilever beam

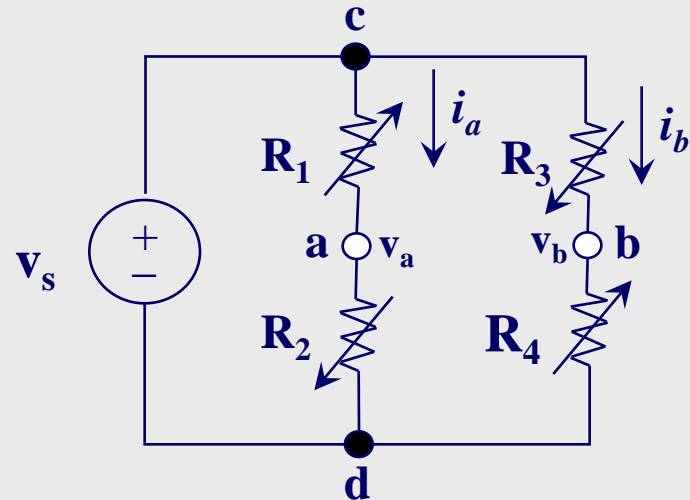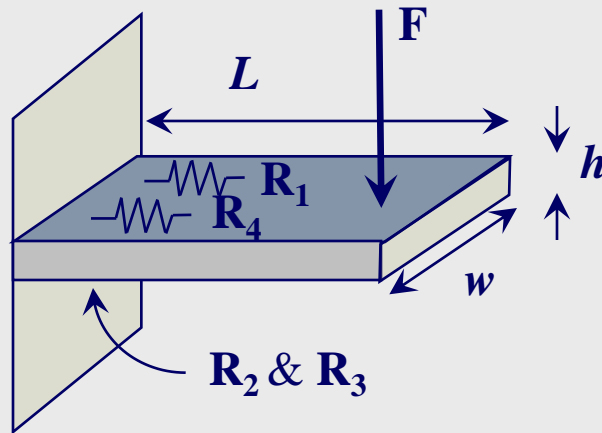- Two strain gauges (R_1 and R_4) on top
- Two strain gauges (R_2 and R_3) on bottom





Wheatstone Bridge

◆ Under the strain of force **F** we have:

$$R_1 = R_4 = R_0 + \Delta R$$

$$R_2 = R_3 = R_0 - \Delta R$$

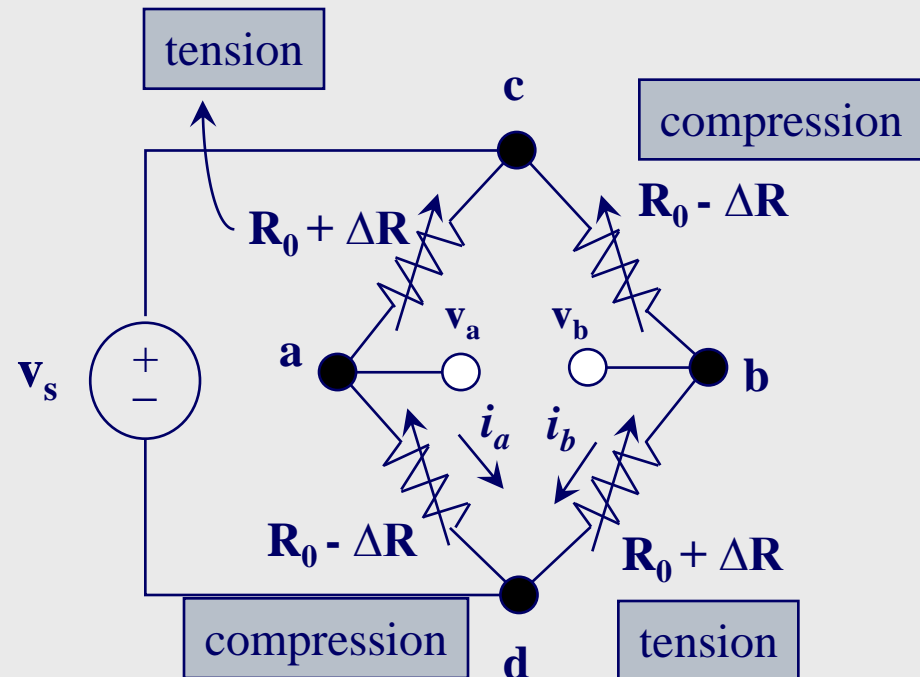
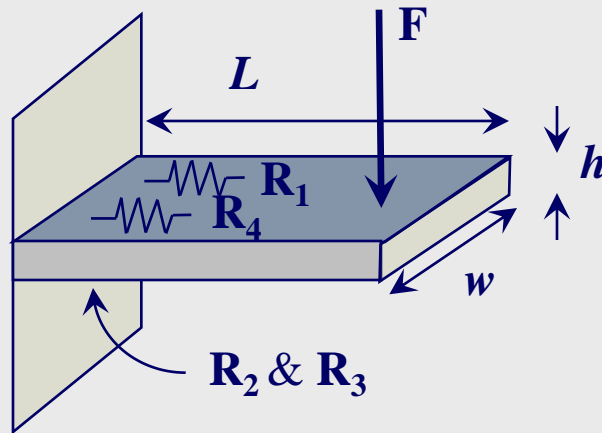


Wheatstone Bridge

◆ From elementary statics it can be shown that:

$$\varepsilon = \frac{6LF}{wh^2Y}$$

Y is the beam's modulus of elasticity

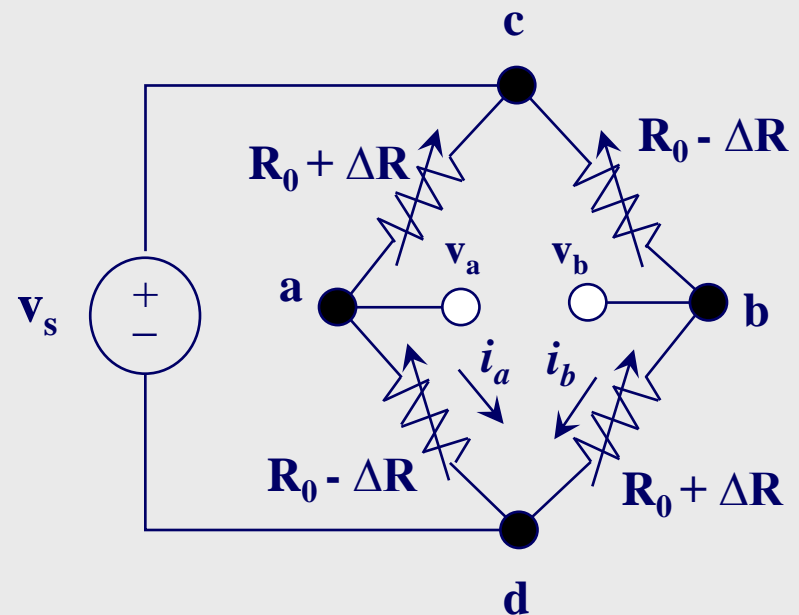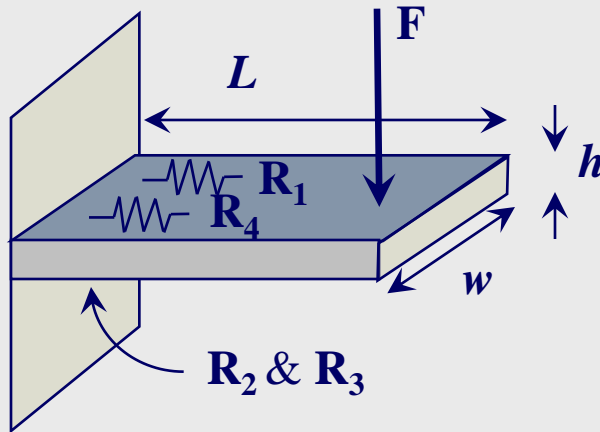


Wheatstone Bridge

◆ Using Ohm's Law:


$$i_a = \frac{v_s}{R_1 + R_2}$$

$$i_b = \frac{v_s}{R_3 + R_4}$$

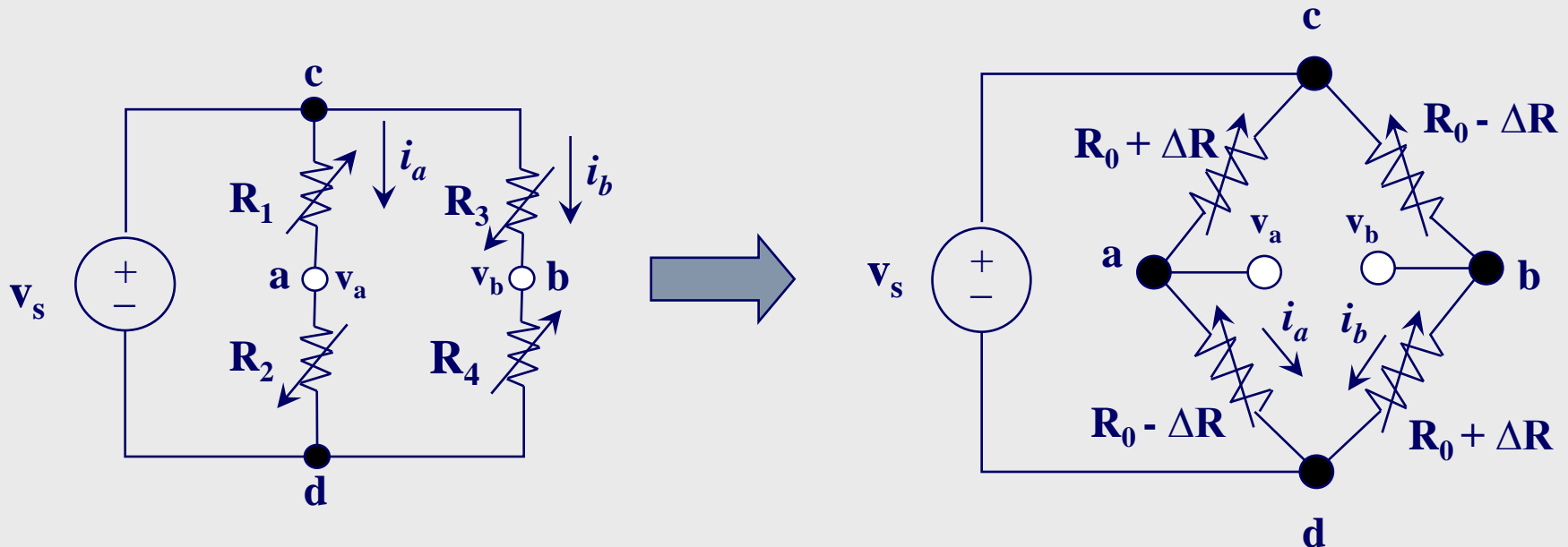

Wheatstone Bridge


◆ Using Ohm's Law:

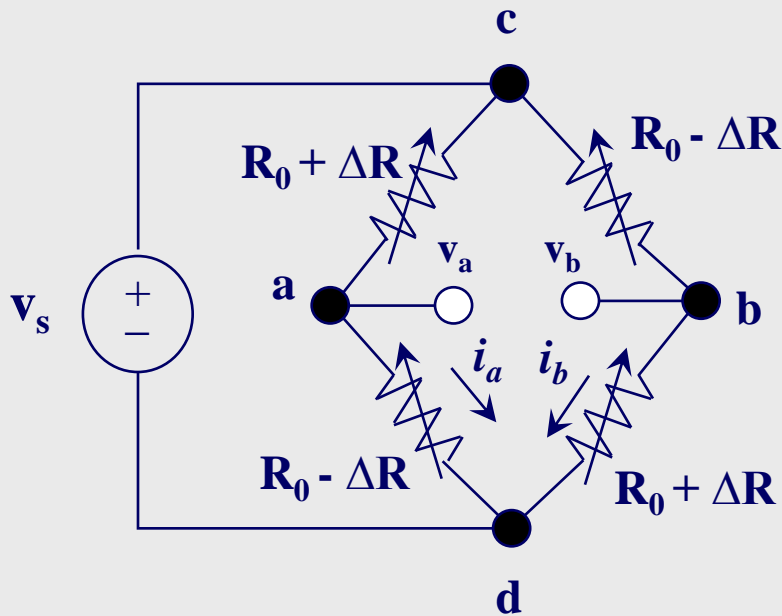

$$\begin{aligned} v_{out} &= v_{ba} = v_b - v_a \\ &= i_b R_4 - i_a R_2 \\ &= \frac{v_s R_4}{R_3 + R_4} - \frac{v_s R_2}{R_1 + R_2} \\ &= v_s \frac{R_0 + \Delta R}{R_0 + \Delta R + R_0 - \Delta R} - v_s \frac{R_0 - \Delta R}{R_0 + \Delta R + R_0 - \Delta R} \\ &= v_s \frac{\Delta R}{R_0} \\ &= v_s GF \varepsilon \end{aligned}$$

Wheatstone Bridge

◆ Find v_o in terms of force F :

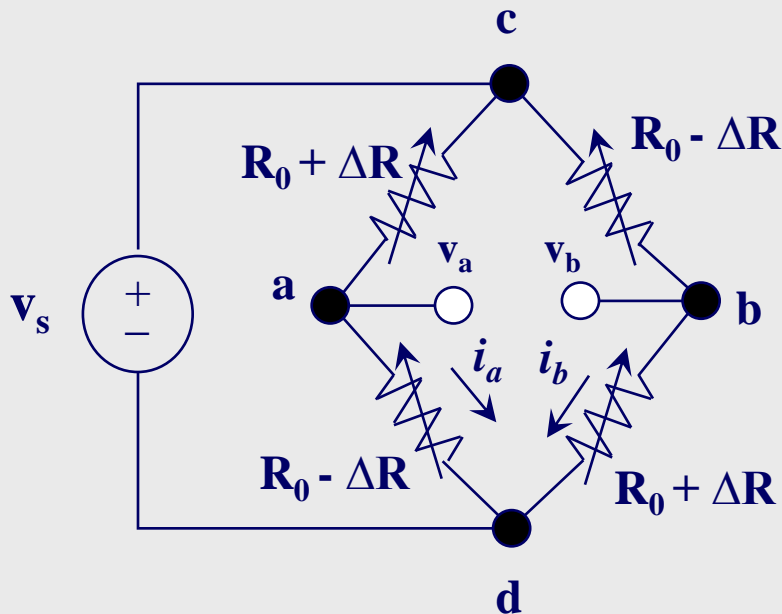


$$\begin{aligned} v_o &= v_s GF \varepsilon \\ &= v_s GF \frac{6LF}{wh^2Y} \\ &= \left(\frac{6v_s GFL}{wh^2Y} \right) F \\ &= kF \end{aligned}$$

k is a calibration constant

Wheatstone Bridge

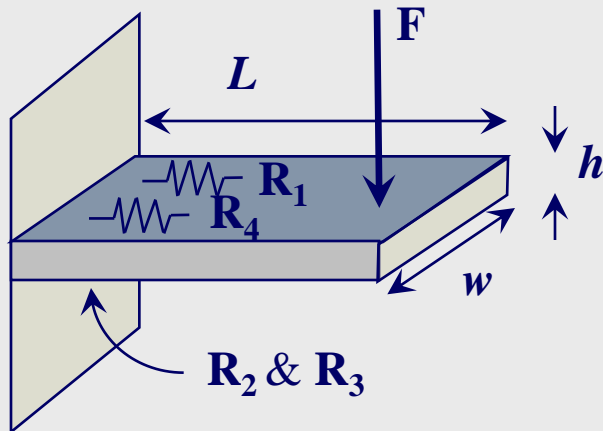
- ◆ **Example3:** using the Wheatstone bridge as a strain measurement tool find v_o
- ▲ the bridge measures forces ranging from 0 to 500 N
 - ▲ $L = 0.3\text{m}$, $w = 0.05\text{m}$, $h = 0.01\text{m}$, $\mathbf{GF} = 2$, $Y = 69 \times 10^9 \text{N/m}^2$, $v_s = 12\text{V}$



$$\begin{aligned} v_o &= kF \\ &= \left(\frac{6v_s GFL}{wh^2Y} \right) F \\ &= \left(\frac{6(12)(2)(0.3)}{(0.05)(0.01)^2 69 \times 10^9} \right) F \\ &= 1.25 F \times 10^{-4} \text{ V / N} \\ &= 0.125 F \text{ mV / N} \end{aligned}$$

Wheatstone Bridge

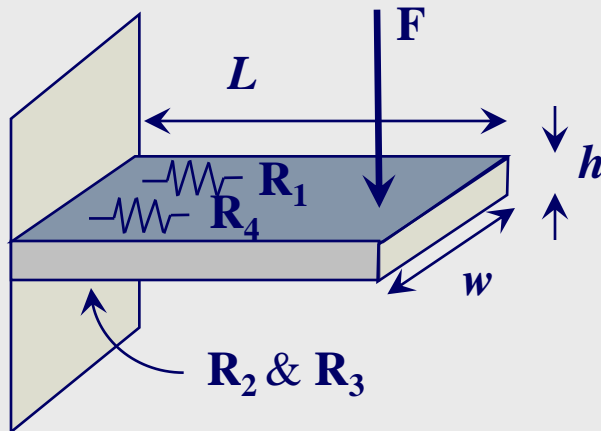- ◆ **Example3:** using the Wheatstone bridge as a strain measurement tool find v_o
- ▲ the bridge measures forces ranging from 0 to 500 N
 - ▲ $L = 0.3\text{m}$, $w = 0.05\text{m}$, $h = 0.01\text{m}$, $GF = 2$, $Y = 69 \times 10^9 \text{N/m}^2$, $v_s = 12\text{V}$



Maximum voltage :


$$\begin{aligned} v_o &= 0.125 F \text{ mV} / \text{N} \\ &= 1.25 \times 10^{-4} (500) \\ &= 62.5 \text{ mV} \end{aligned}$$

Practical Sources

Ideal Sources

◆ Ideal current source


▲ 3A source

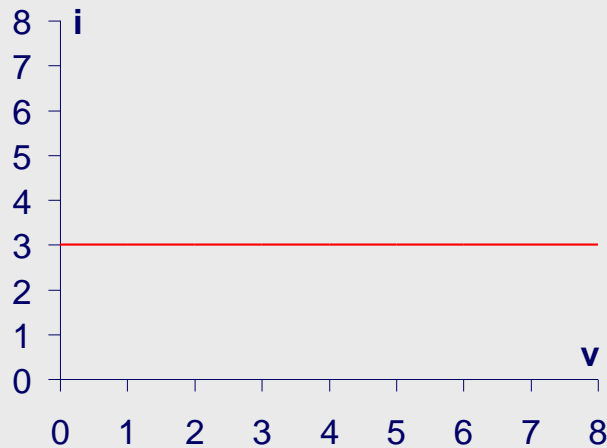

Provides a prescribed voltage across its terminals irrespective of the current flowing through it.

◆ Ideal voltage source

▲ 6V source

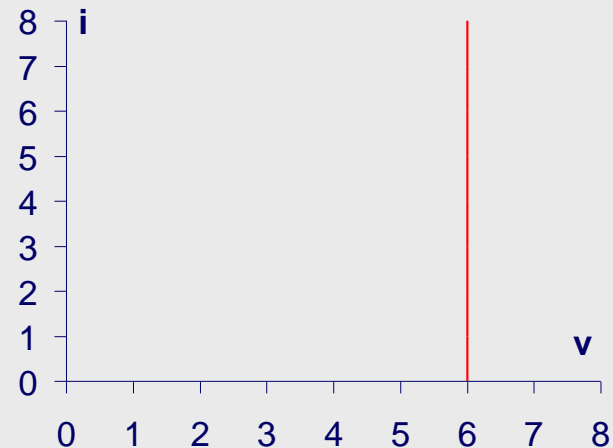

Provides a prescribed current irrespective of the voltage across it.

Practical Sources

◆ Actual voltage sources have limitations

▲ There is a limit to the number of total electrons any battery can motivate through a circuit

- How to measure limitations?
 - Total number of electrons? (huge number)
 - Use coulombs? (also too huge)
 - **amp-hour** – unit invented for this purpose
- 1 amp-hour = 1 amp for 1 hour
 - = 2 amps for ½ hour
 - = 1/3 amp for 3 hours

$$\begin{aligned}1 \text{ amp} &= 1 \text{ coulombs/second} \\1 \text{ amp-hour} &= 3600 \text{ coulombs}\end{aligned}$$

▲ Batteries have ratings indicating their current limitations


- Car battery – 12V, 70 amp-hours (A-h) @ 3.5 A (for 20 hours)
- D – cell (1.5V) carbon-zinc battery – 4.6 amp-hours @ 100mA (for 46 hours)
- 9 – volt carbon-zinc battery – 400 mA-hours @ 8mA (for 50 hours)

Practical Sources

◆ Actual voltage sources have limitations

- ▶ As the load resistance ($\mathbf{R_L}$) decreases, the voltage source ($\mathbf{v_s}$) is required to provide increasing amounts of current (\mathbf{i}) in order to maintain $\mathbf{v_s}$

$$i = \frac{v_s}{R_L}$$

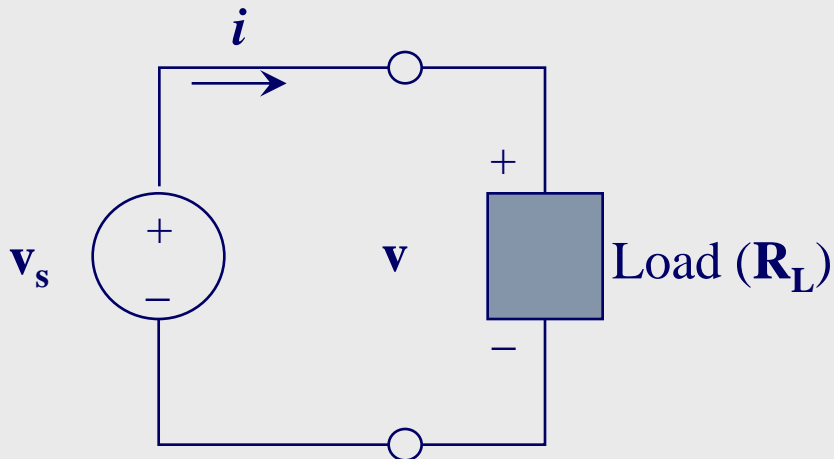


As $\mathbf{R_L} \rightarrow 0$, $\mathbf{v_s}$ has to provide an **infinite** amount of current!

Practical Sources

◆ Actual voltage sources have limitations

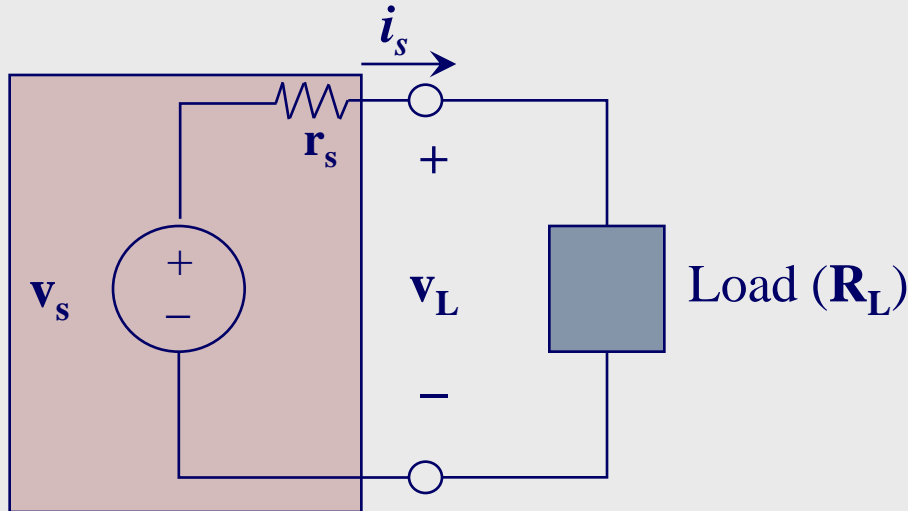A series resistance r_s poses a limit to the maximum current the voltage source can provide




$$i_s = \frac{v_s}{r_s + R_L}$$

Practical voltage source

Practical Sources

◆ Actual voltage sources have limitations

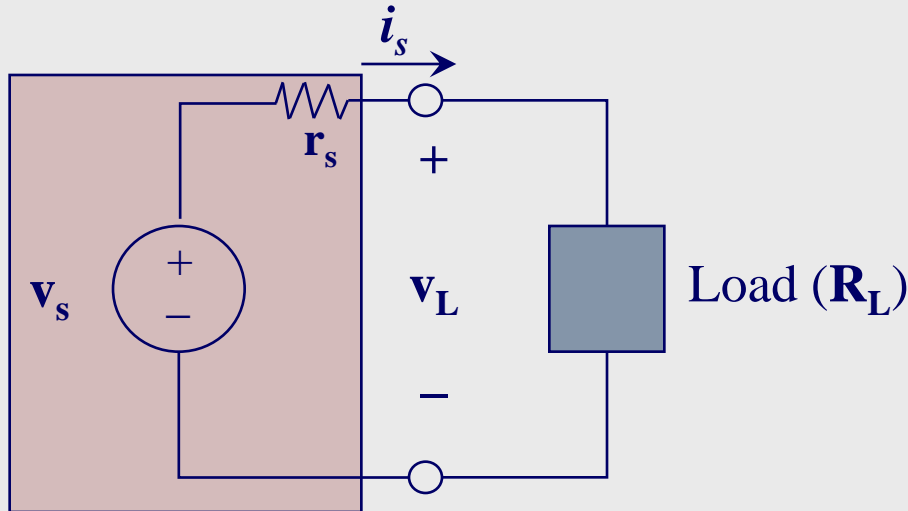A series resistance r_s poses a limit to the maximum current the voltage source can provide



$$\begin{aligned} v_L &= i_s R_L \\ &= v_s \frac{R_L}{r_s + R_L} \end{aligned}$$


NB: $v_s \neq v_L$

Practical voltage source

Practical Sources

◆ Actual voltage sources have limitations

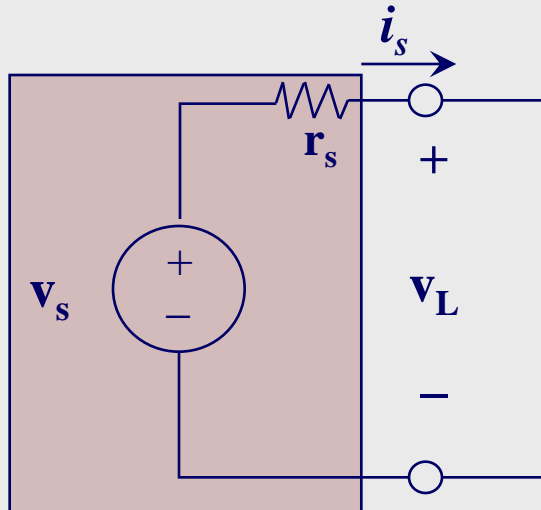A series resistance r_s poses a limit to the maximum current the voltage source can provide



Practical voltage source


$$i_s = \frac{v_s}{r_s + R_L}$$
$$\lim_{R_L \rightarrow 0} i_s = \frac{v_s}{r_s}$$
$$i_{S \max} = \frac{v_s}{r_s}$$

Practical Sources

◆ Actual current sources have limitations

- ▲ As the load resistance ($\mathbf{R_L}$) increases, the current source ($\mathbf{i_s}$) is required to provide increasing amounts of current (\mathbf{v}) in order to maintain $\mathbf{i_s}$

$$v_s = i \cdot R_L$$

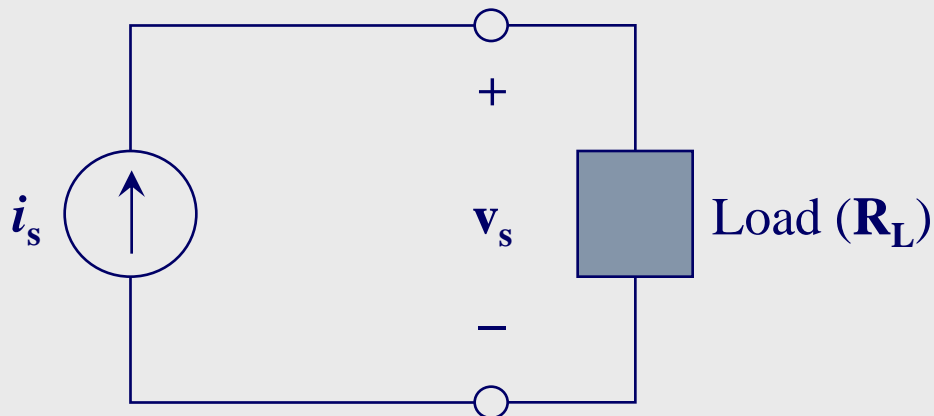


As $\mathbf{R_L} \rightarrow \infty$, $\mathbf{i_s}$ has to provide an **infinite** amount of voltage!

Practical Sources

◆ Actual current sources have limitations

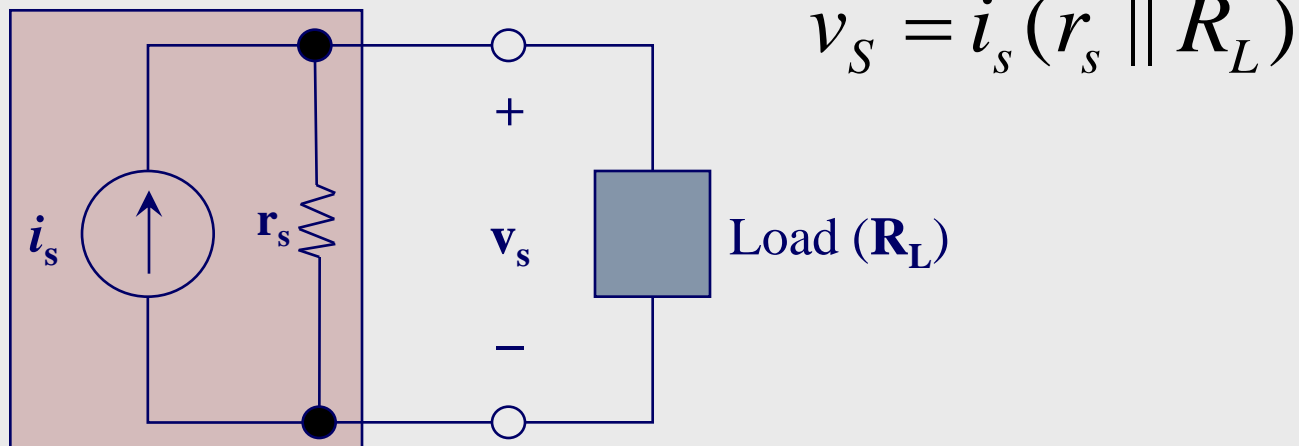A series resistance r_s poses a limit to the maximum voltage the current source can provide




Practical current source

Practical Sources

◆ Actual current sources have limitations

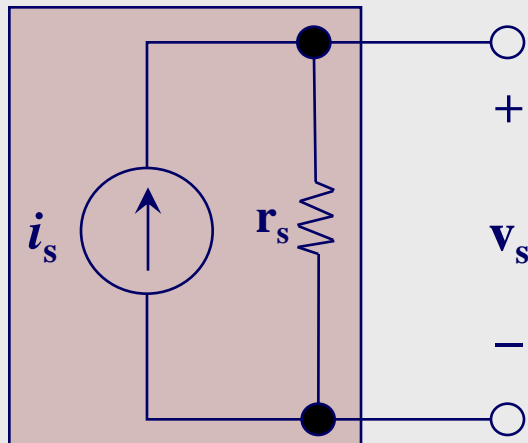A series resistance r_s poses a limit to the maximum voltage the current source can provide




Practical current source

$$v_s = i_s (r_s \parallel R_L)$$
$$\lim_{R_L \rightarrow \infty} v_s = i_s r_s$$
$$v_{s \max} = i_s r_s$$


Practical Sources

- ◆ Actual current and voltage sources have limitations

Ideal 3A current source

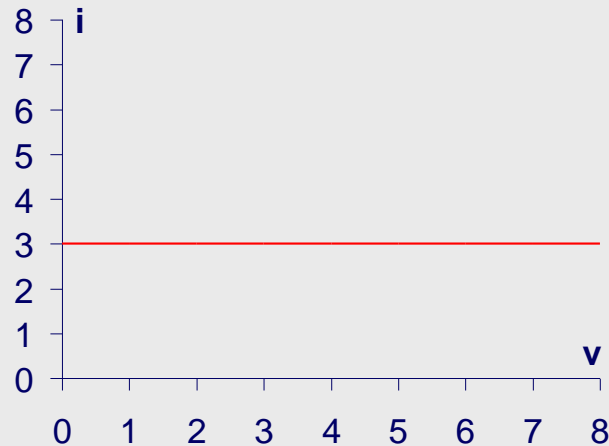


Ideal 6V voltage source

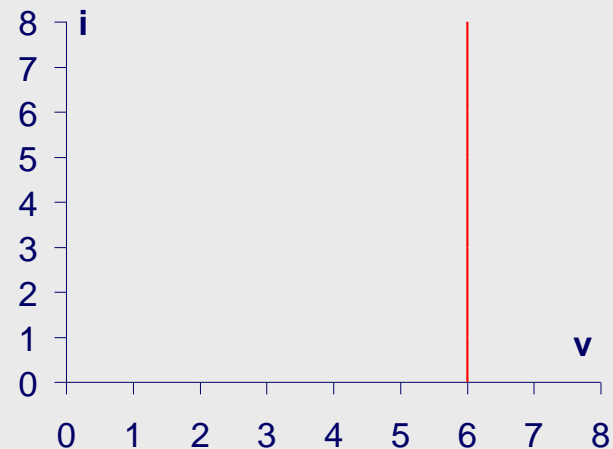


Practical Sources

- ◆ Actual current and voltage sources have limitations

Practical 3A current source

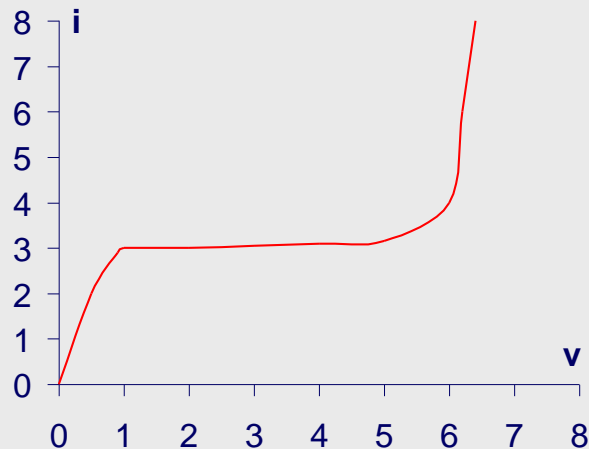

Practical 6V voltage source


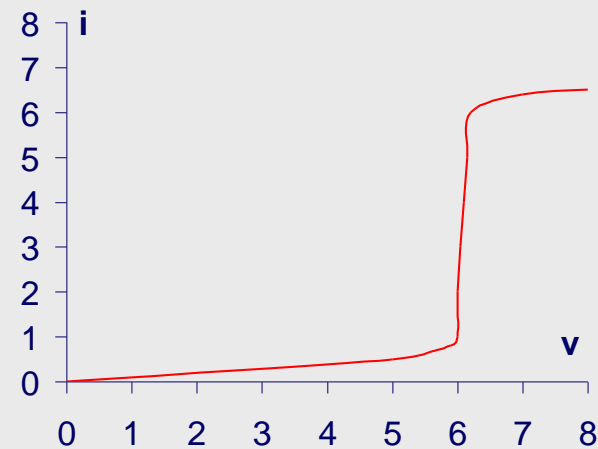


Measuring Devices

Ohmmeter

◆ **Ohmmeter**: measures the resistance of a circuit element

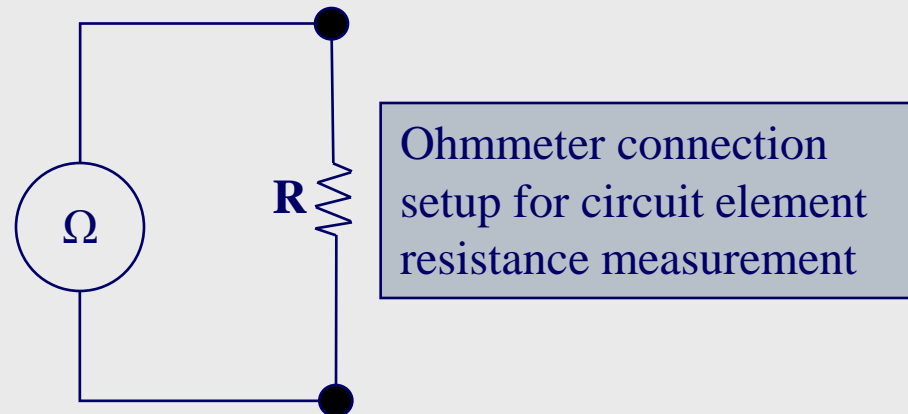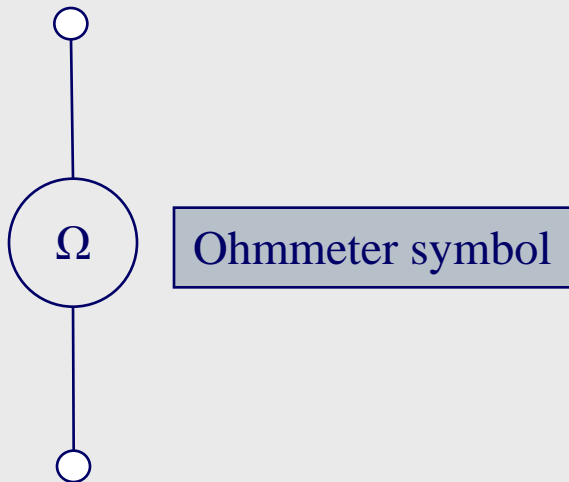
NB: the resistance of an element can only be measured when the element is **disconnected** from **all** other circuit elements



Ammeter

- ◆ **Ammeter**: a device that can measure the current flowing through a circuit element when connected in **series** with that circuit element

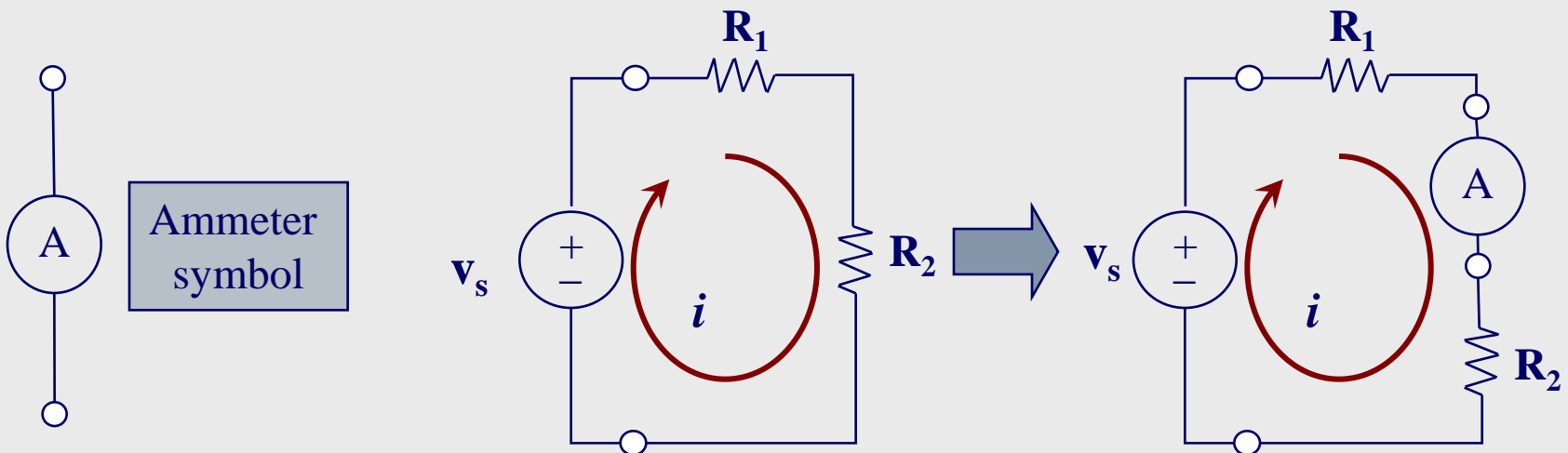
NB: 1. the ammeter must be connected in **series** with the circuit element
2. the ammeter should not restrict the flow of current (i.e. cause a voltage drop)
– an ideal ammeter has **zero** resistance



Voltmeter

- ◆ **Voltmeter**: a device that can measure the voltage across a circuit element when connected in **parallel** with that circuit element

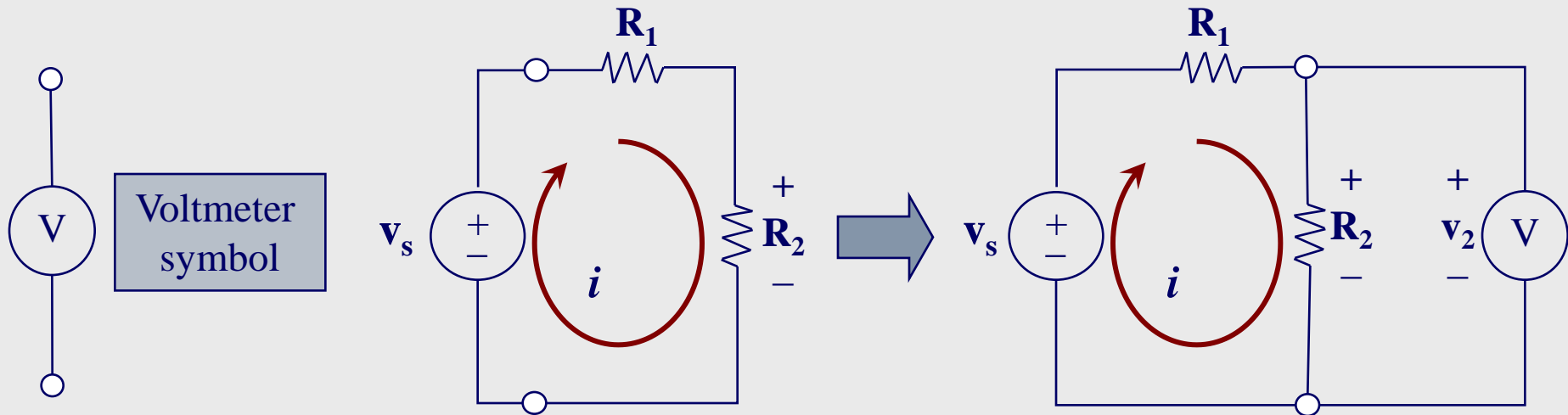
NB: 1. the voltmeter must be connected in **parallel** with the circuit element
2. the voltmeter should not draw any current away from the element
– an ideal voltmeter has **infinite** resistance



Wattmeter

- ◆ **Wattmeter**: a device that can measure the power dissipated by a circuit element

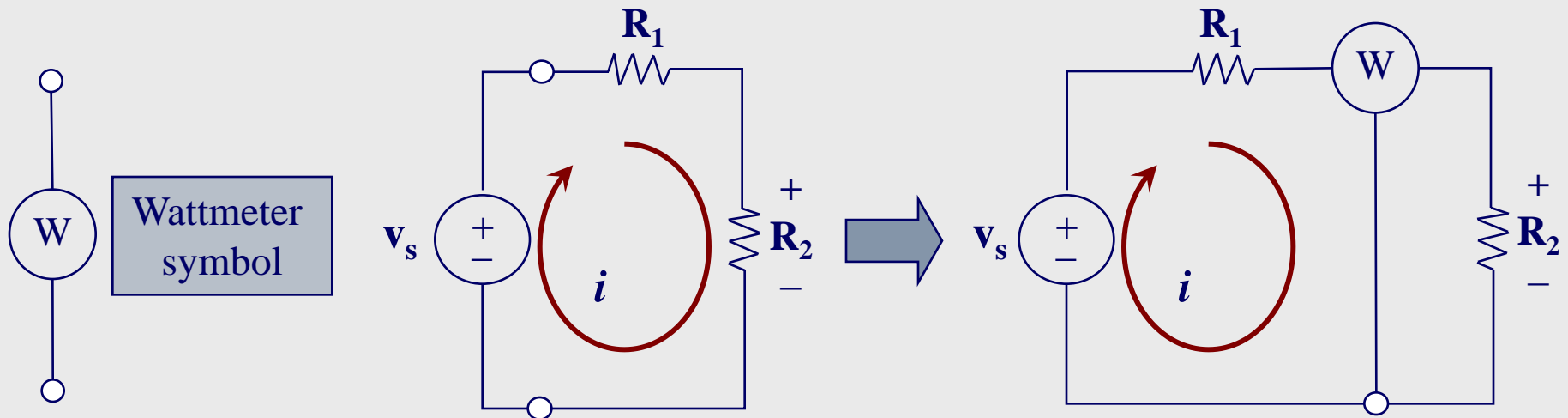NB: 1. the wattmeter must be connected in **parallel** with the circuit element, but also in **series** with the circuit.
– a wattmeter is simply the combination of a voltmeter and an ammeter



Practical Voltmeters and Ammeters

- ◆ In reality, voltmeters and ammeters have internal resistances
 - ▶ Practical ammeters will always add some resistance
 - ▶ Practical voltmeters will always draw some current

